
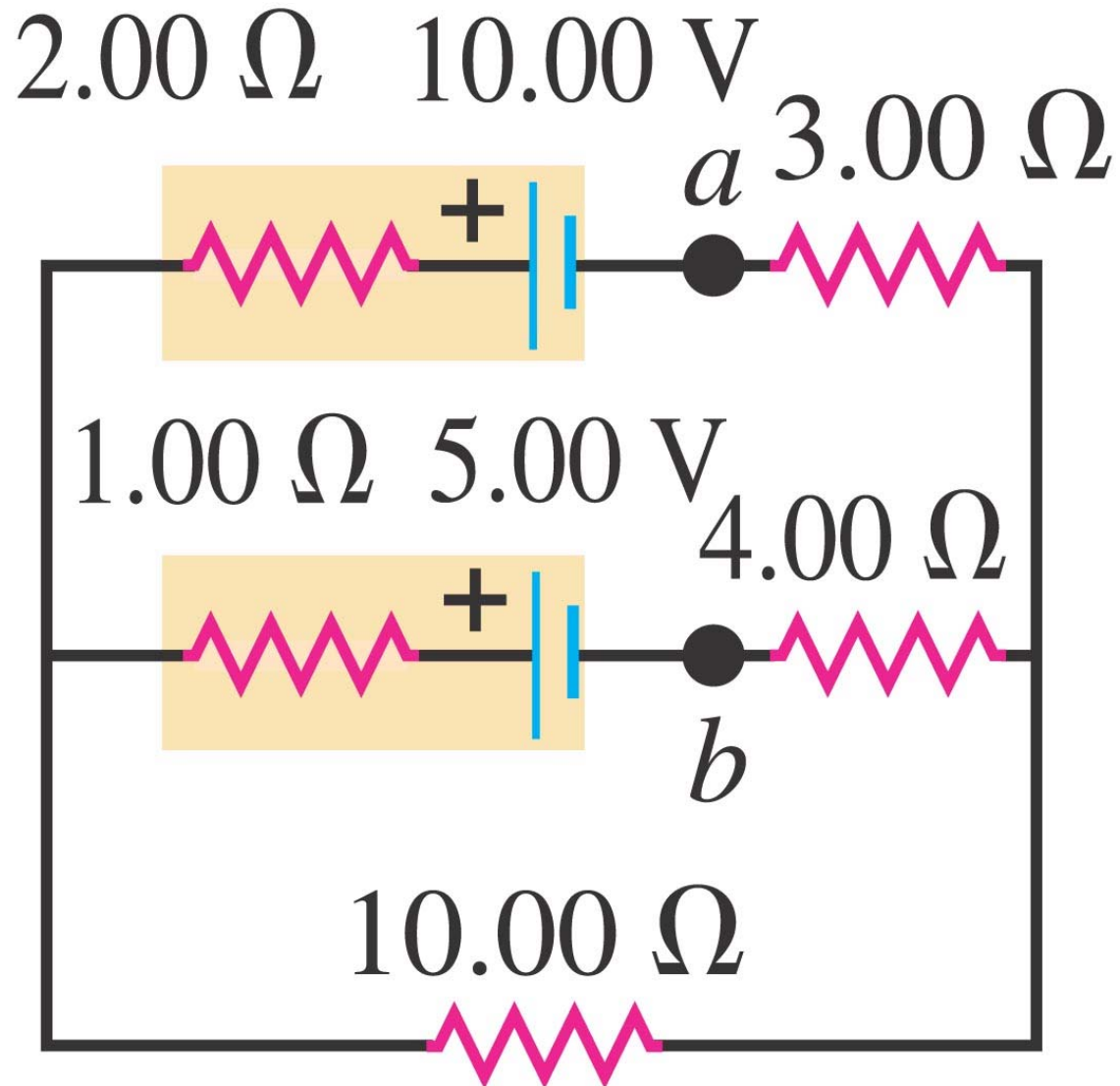


What is  $V_{ab}$ ?

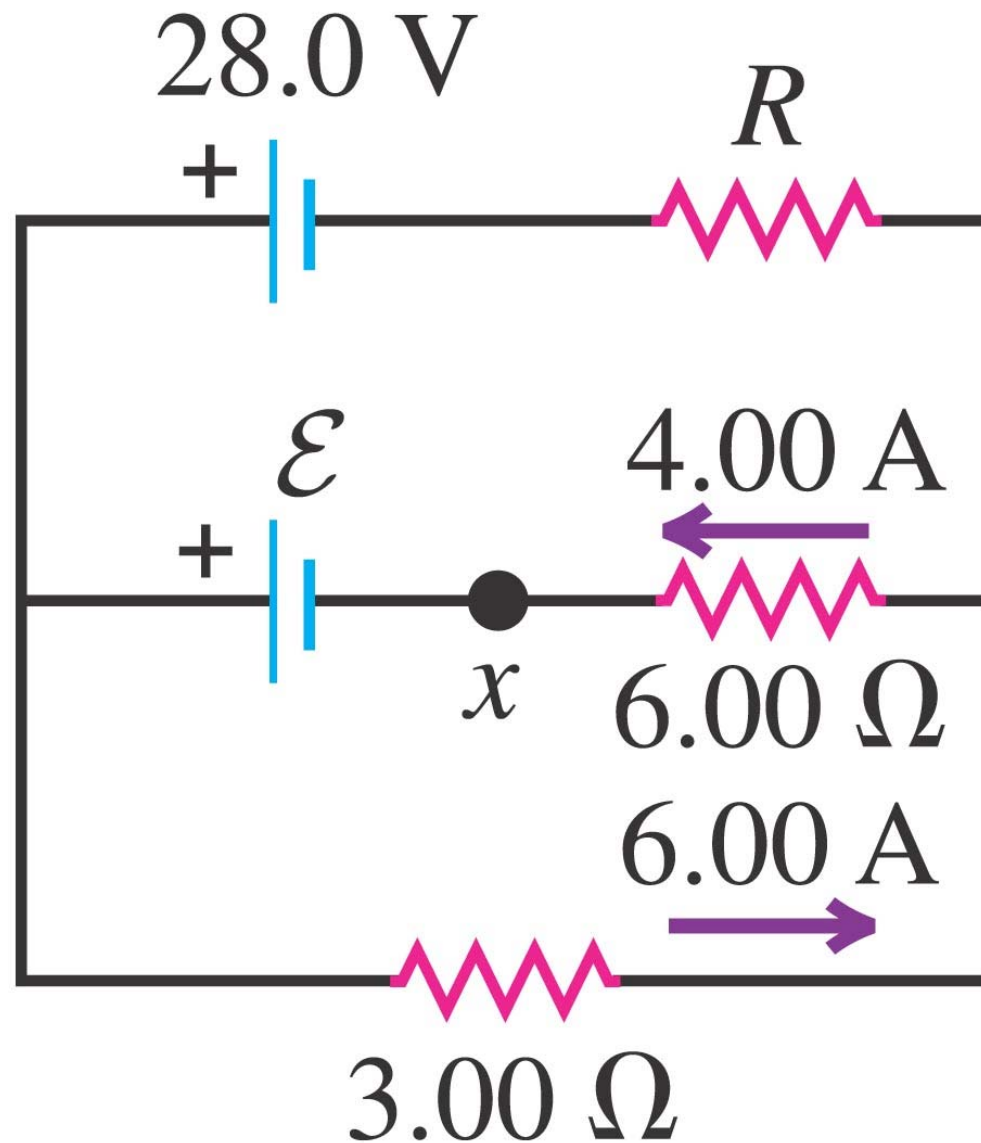

Solve for  $\varepsilon$ ,  $R$



What is Power dissipated in  $4\ \Omega$  Resistor?

