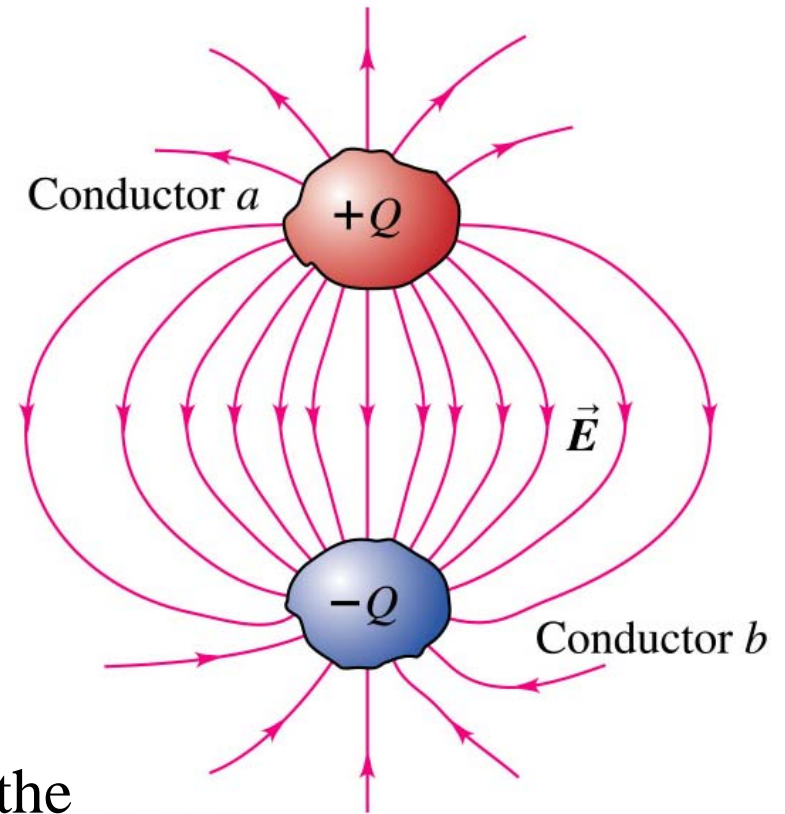


# CAPACITORS

- C - Capacitance

$V = V_a - V_b$  - voltage difference

$$C = \frac{Q}{V}$$



ication, Inc., publishing as Addison Wesley.


- Capacitance, depends on the geometry of the two conductors (size, shape, separation) and capacitance is always a positive quantity by its definition (voltage difference and charge of + conductor)
- UNITS: Coulomb/Volts or Farads, after Michael Faraday

# Capacitor Summary

- A Capacitor is an object with two spatially separated conducting surfaces.
- The definition of the capacitance of such an object is:


$$C \equiv \frac{Q}{V}$$

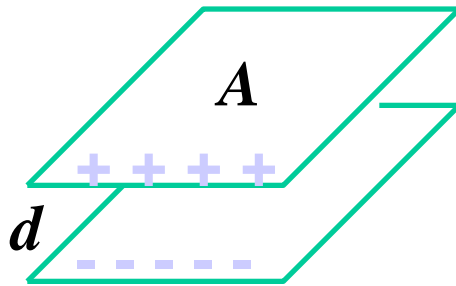- The capacitance depends on the geometry :




**Parallel Plates**

$$C = \frac{A\epsilon_0}{d}$$

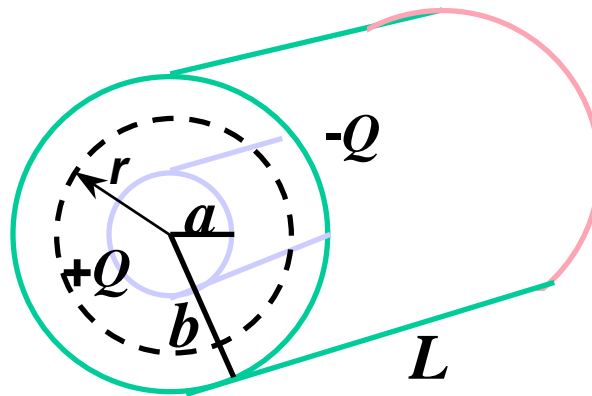

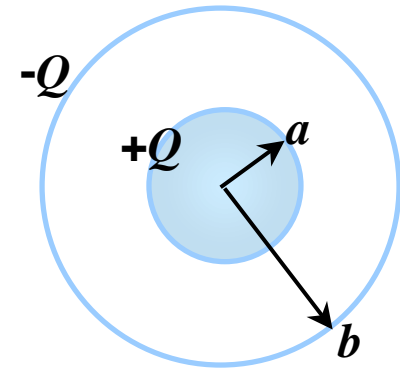**Cylindrical**

$$C = \frac{2\pi\epsilon_0 L}{\ln\left(\frac{b}{a}\right)}$$



**Spherical**


$$C = \frac{4\pi\epsilon_0 ab}{b - a}$$

# CAPACITORS in parallel

Want to find the equivalent capacitance  $C_{eq}$ :

- Voltage is same across each capacitor
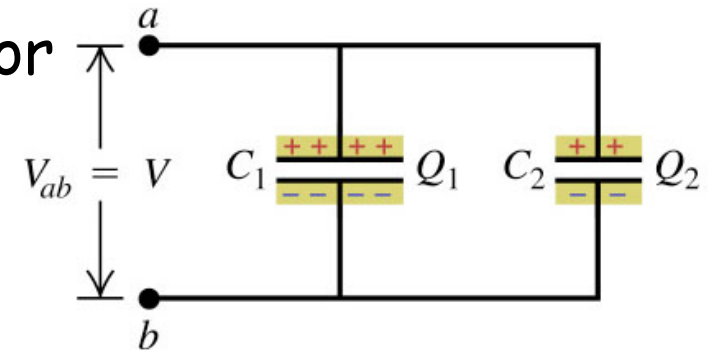
$$V_{ab} = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}; \quad C_1 = \frac{Q_1}{V_{ab}}; \quad C_2 = \frac{Q_2}{V_{ab}}$$




(a)

- Total charge and voltage ratios for parallel capacitor,

$$\frac{Q_1 + Q_2}{V_{ab}} = C_{parallel} = C_1 + C_2$$

For more parallel capacitors:

$$C_{parallel} = \sum_i C_i$$

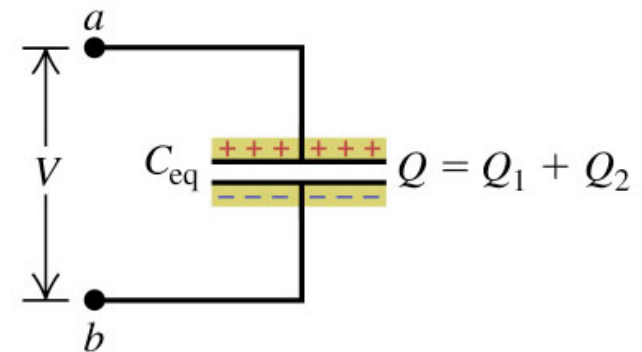


(b)

ublishing as Addison Wesley.

Note; 2 parallel capacitors  $C$ , doubles capacitance.
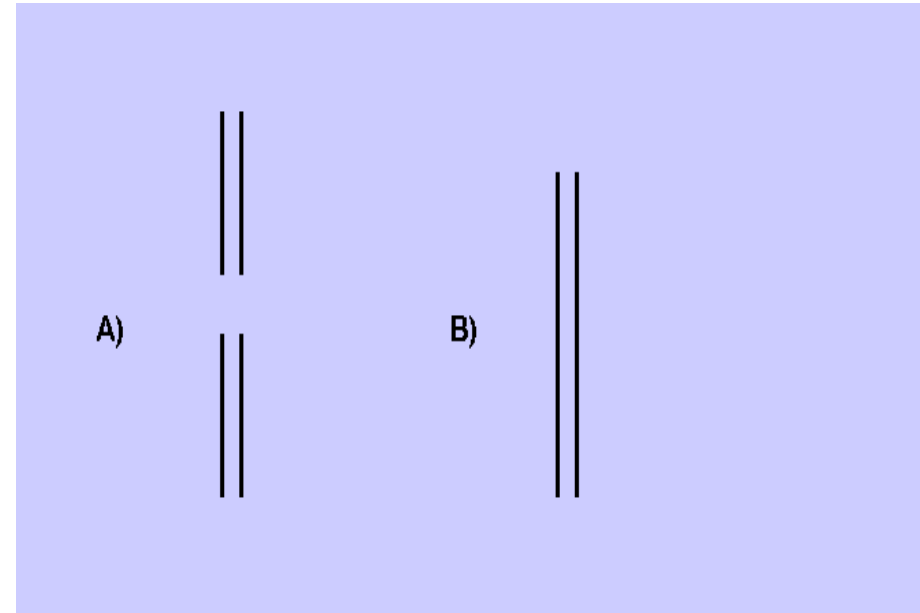
## Example 1:

Two identical parallel plate capacitors are shown in an end-view in A) of the figure. Each has a capacitance of  $C$ .




4) If the two are joined together as shown in B), forming a single capacitor, what will be the final capacitance?

a)  $C/2$


b)  $C$

c)  $2C$

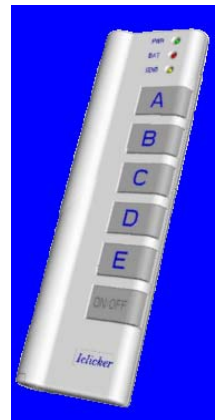
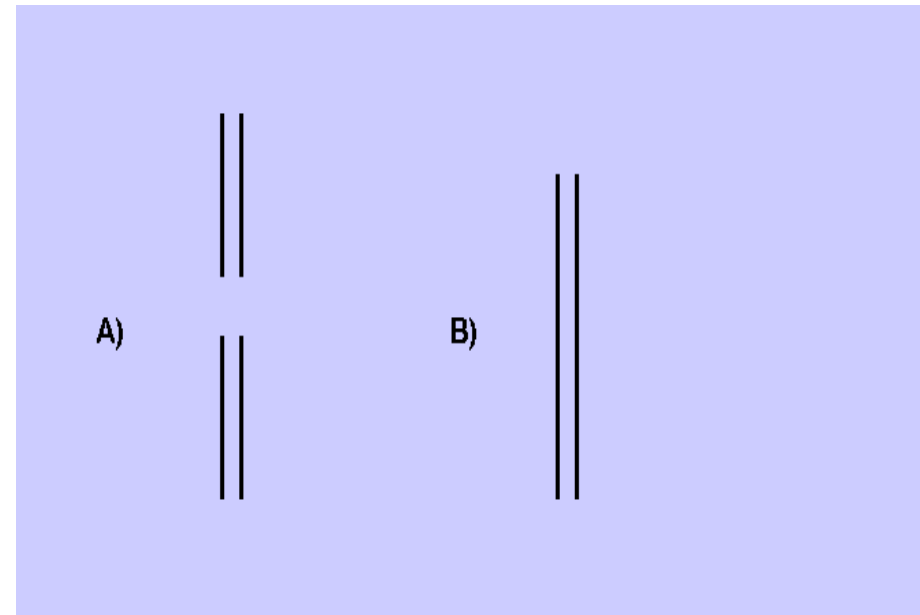
### Example 1:

Two identical parallel plate capacitors are shown in an end-view in A) of the figure. Each has a capacitance of  $C$ .



4) If the two are joined together as shown in B), forming a single capacitor, what will be the final capacitance?

a)  $C/2$


b)  $C$

c)  $2C$
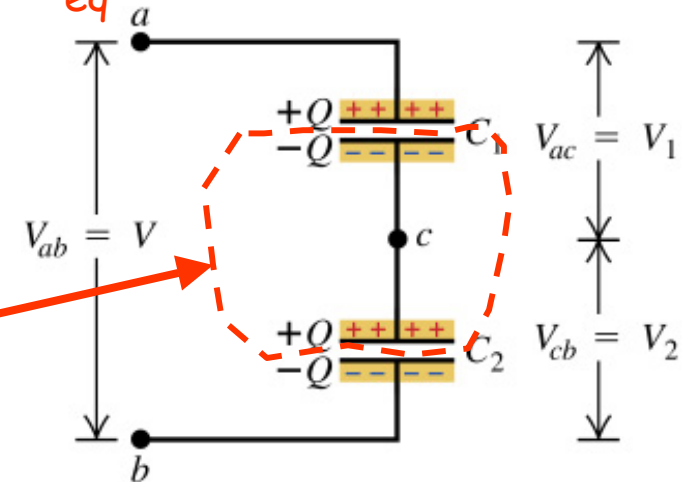
# CAPACITORS in series

Want to find the equivalent capacitance  $C_{eq}$ :

- If a voltage is applied across a and b, then a  $+Q$  appears on upper plate and  $-Q$  on lower plate.
- A  $-Q$  charge is induced on lower plate of  $C_1$  and a  $+Q$  charge is induced on upper plate of  $C_2$ . The total charge in circuit c is neutral.




(a)

$$V_1 = \frac{Q}{C_1} ; \quad V_2 = \frac{Q}{C_2}$$

$$V = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2}$$
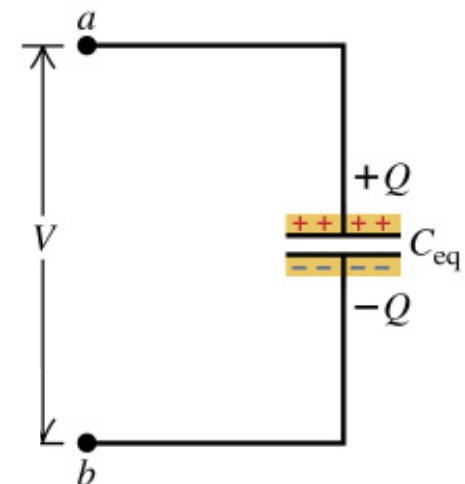
$$\frac{V}{Q} = \frac{1}{C_{series}} = \frac{1}{C_1} + \frac{1}{C_2}$$




(b)

Note; 2 series capacitors C, halves capacitance.

# Examples:


## Combinations of Capacitors

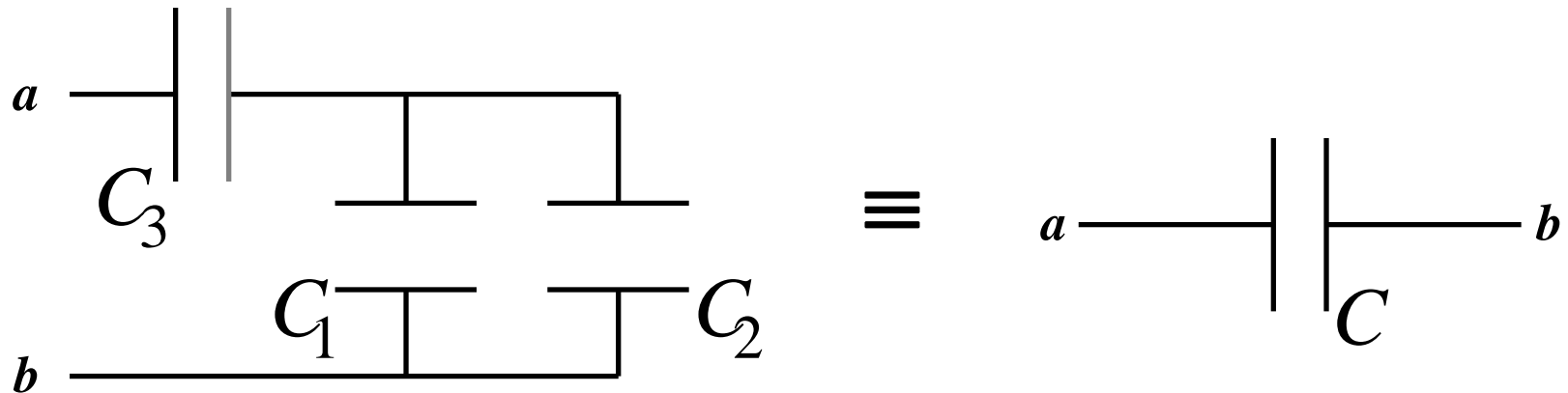


- How do we start??
- Recognize  $C_3$  is in series with the parallel combination on  $C_1$  and  $C_2$ . i.e.,

$$\frac{1}{C} = \frac{1}{C_3} + \frac{1}{C_1 + C_2} \quad \Rightarrow \quad \boxed{C = \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3}}$$


## Example 2:

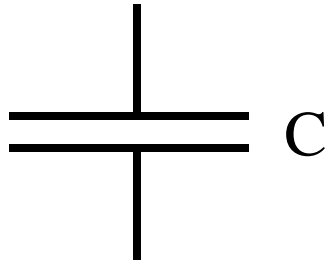

Configuration A

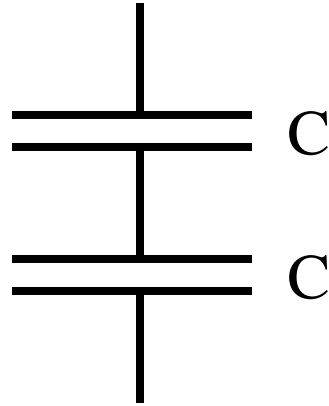

Configuration B

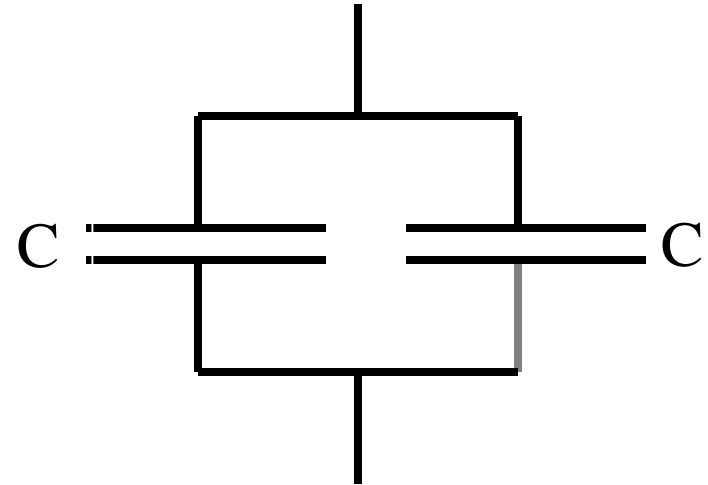


Configuration C

Three configurations are constructed using identical capacitors


→ Which of these configurations has the lowest overall capacitance?

- a) Configuration A
- b) Configuration B
- c) Configuration C

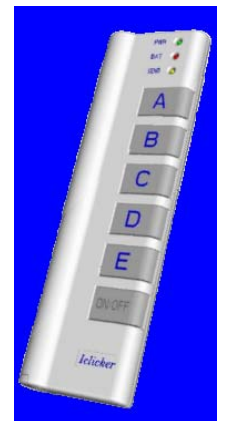





Example 2:

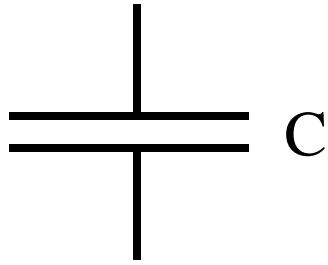

Configuration A

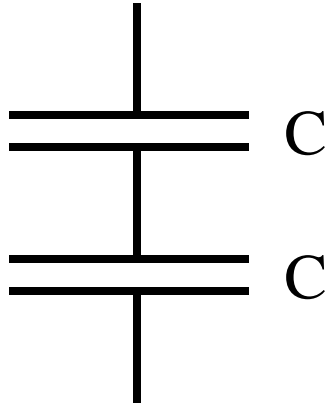

Configuration B

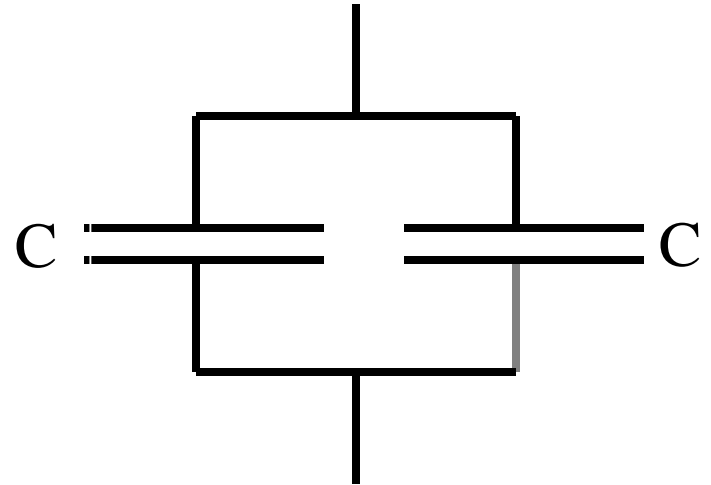

Configuration C

Three configurations are constructed using identical capacitors

→ Which of these configurations has the lowest overall capacitance?


a) Configuration A

b) Configuration B

c) Configuration C
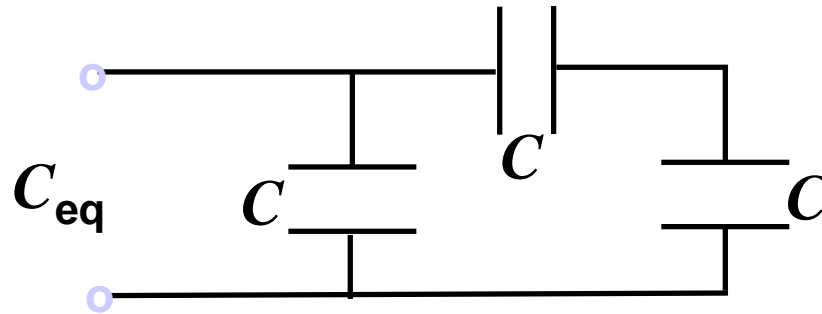
## Example 4


- What is the equivalent capacitance,  $C_{eq}$ , of the combination shown?



(a)  $C_{eq} = (3/2)C$


(b)  $C_{eq} = (2/3)C$

(c)  $C_{eq} = 3C$

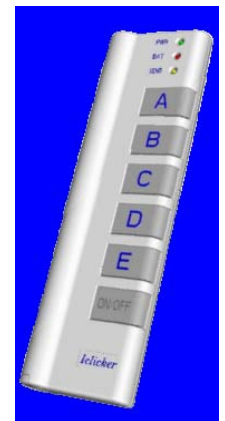
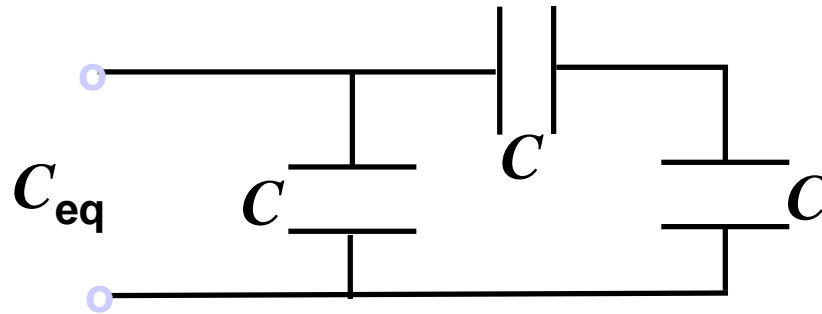
# Example 4


- What is the equivalent capacitance,  $C_{eq}$ , of the combination shown?



(a)  $C_{eq} = (3/2)C$

(b)  $C_{eq} = (2/3)C$


(c)  $C_{eq} = 3C$

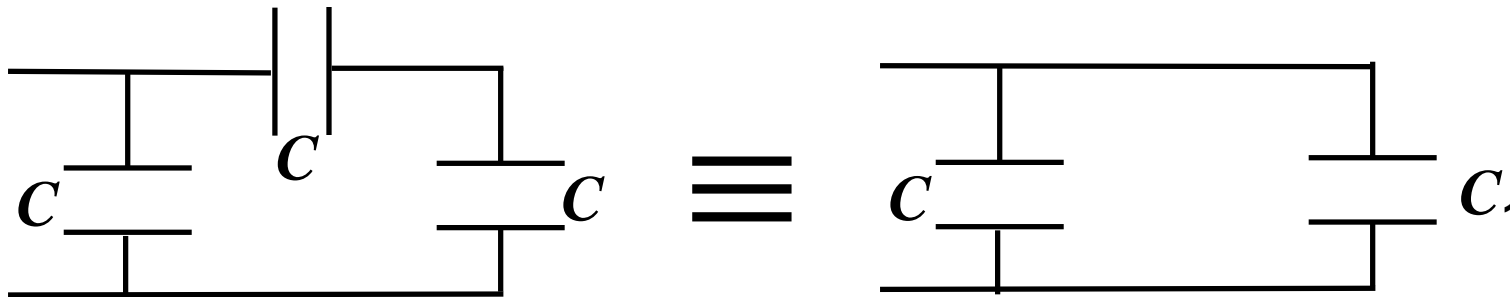

$$\frac{1}{C_1} = \frac{1}{C} + \frac{1}{C} \Rightarrow C_1 = \frac{C}{2} \Rightarrow C_{eq} = C + \frac{C}{2} = \frac{3}{2}C$$
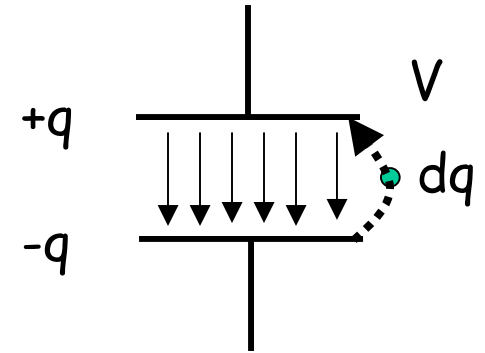
# Energy storage in CAPACITORS

Charge capacitor by transferring bits of charge  $dq$  at a time from bottom to top plate. Can use a battery to do this. Battery does work which increase potential energy of capacitor.



$q$  is magnitude of charge on plates

$V = q/C$        $V$  across plates

$dU = V dq$       increase in potential energy


$$U = \int_0^U dU = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C} = \frac{(CV)^2}{2C} = \frac{1}{2} CV^2$$

Y&F, eqn. 24.9

two ways to write
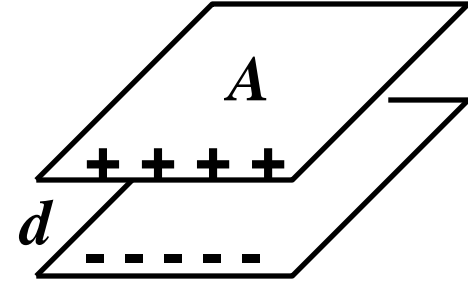
# Question!

- Suppose the capacitor shown here is charged to  $Q$  and then the battery is *disconnected*.
- Now suppose I pull the plates further apart so that the final separation is  $d_1$ .
- How do the quantities  $Q, C, E, V, U$  change?
- $Q$ : remains the same.. no way for charge to leave.
- $C$ : decreases.. since capacitance depends on geometry
- $E$ : remains the same... depends only on charge density
- $V$ : increases.. since  $C \downarrow$ , but  $Q$  remains same (or  $d \uparrow$  but  $E$  the same)
- $U$ : increases.. add energy to system by separating
- How much do these quantities change?.. exercise for student!!



Answers:


$$C_1 = \frac{d}{d_1} C$$

$$V_1 = \frac{d_1}{d} V$$

$$U_1 = \frac{d_1}{d} U$$
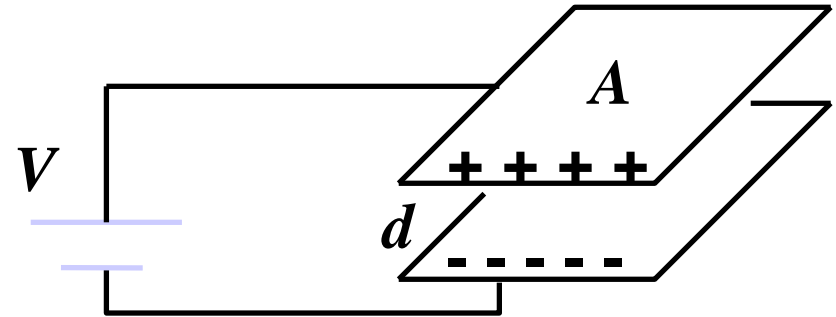
# Related Question

- Suppose the battery ( $V$ ) is kept attached to the capacitor.
- Again pull the plates apart from  $d$  to  $d_1$ .
- Now what changes?



- $C$ : decreases (capacitance depends only on geometry)
- $V$ : must stay the same - the battery forces it to be  $V$
- $Q$ : must decrease,  $Q=CV$  charge flows off the plate
- $E$ : must decrease ( $E = \frac{V}{D}$ ,  $E = \frac{\sigma}{E_0}$ )
- $U$ : must decrease ( $U = \frac{1}{2}CV^2$ )
- How much do these quantities change?


Answers:

$$C_1 = \frac{d}{d_1} C$$

$$E_1 = \frac{d}{d_1} E$$

$$U_1 = \frac{d}{d_1} U$$

Example 5:

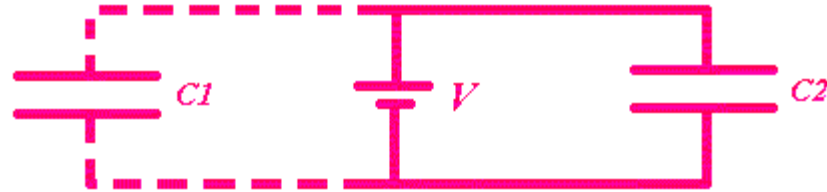


Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both capacitors is doubled.

→ What is the relation between the charges on the two capacitors ?


a)  $Q_1 > Q_2$

b)  $Q_1 = Q_2$

c)  $Q_1 < Q_2$

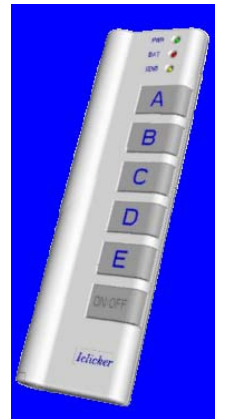

Example 5:

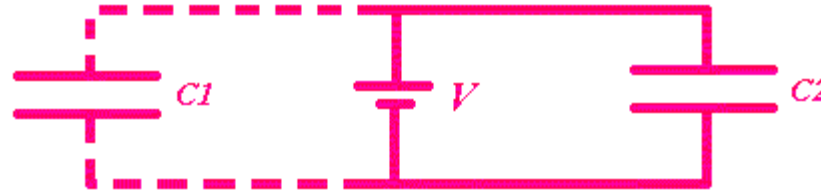

Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both capacitors is doubled.

→ What is the relation between the charges on the two capacitors ?


a)  $Q_1 > Q_2$

b)  $Q_1 = Q_2$

c)  $Q_1 < Q_2$



Example 6:

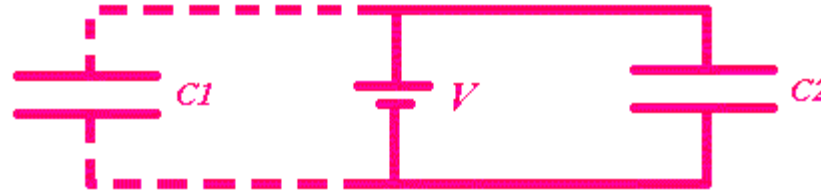


Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both capacitors is doubled.

→ How does the electric field between the plates of  $C_2$  change as separation between the plates is increased ? The electric field:


a) increases

b) decreases

c) doesn't change

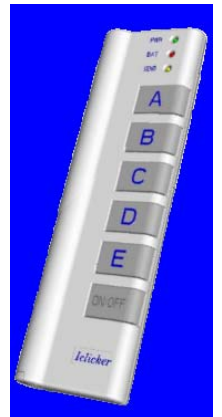

Example 6:

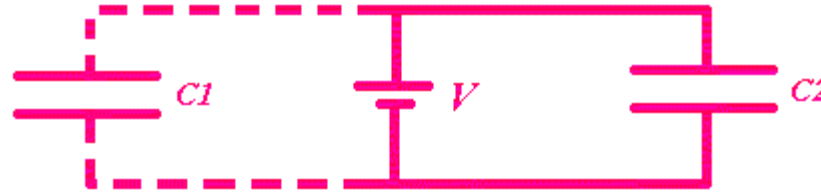

Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both capacitors is doubled.


→ How does the electric field between the plates of  $C_2$  change as separation between the plates is increased ? The electric field:

a) increases

b) decreases

c) doesn't change

Example 7:

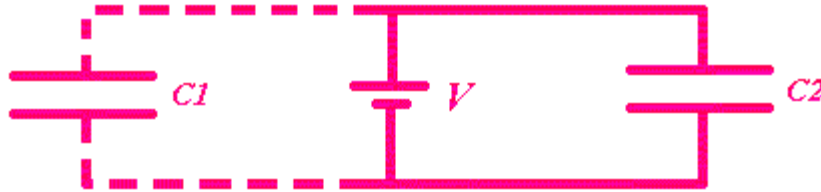


Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both caps is doubled.

→ What is the relation between the voltages on the two capacitors?


a)  $V_1 > V_2$

b)  $V_1 = V_2$

c)  $V_1 < V_2$

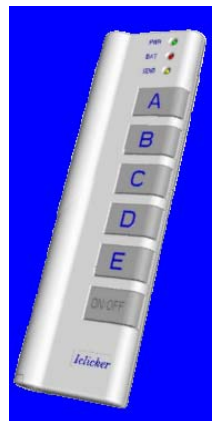

Example 7:

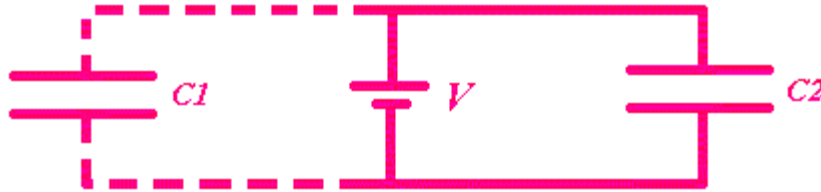

Two identical parallel plate capacitors are connected to a battery, as shown in the figure.  $C_1$  is then disconnected from the battery, and the separation between the plates of both caps is doubled.

→ What is the relation between the voltages on the two capacitors?


a)  $V_1 > V_2$

b)  $V_1 = V_2$

c)  $V_1 < V_2$
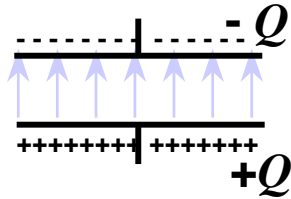
# Where is the Energy Stored?

- **Claim:** energy is stored in the electric field itself. Think of the energy needed to charge the capacitor as being the energy needed to create the field.
- To calculate the energy density in the field, first consider the constant field generated by a parallel plate capacitor, where



$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{Q^2}{(A\epsilon_0 / d)}$$

- The electric field is given by:

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A} \quad \Rightarrow \quad U = \frac{1}{2} \epsilon_0 E^2 A d$$

- The energy density  $u$  in the field is given by:

$$u = \frac{U}{\text{volume}} = \frac{U}{Ad} = \frac{1}{2} \epsilon_0 E^2$$

This is the energy density,  $u$ , of the electric field....

Units:  $\frac{\text{J}}{\text{m}^3}$

# Energy Density

**Claim:** the expression for the energy density of the electrostatic field

$$u = \frac{1}{2} \epsilon_0 E^2$$

is general and is not restricted to the special case of the constant field in a parallel plate capacitor.

- **Example** (and another exercise for the student!)
  - Consider  $E$ - field between surfaces of cylindrical capacitor:
  - Calculate the energy in the field of the capacitor by integrating the above energy density over the volume of the space between cylinders.

$$U = \frac{1}{2} \epsilon_0 \int E^2 dV = \frac{1}{2} \epsilon_0 \int \int E^2 \pi r dr dl = \text{etc.}$$

- Compare this value with what you expect from the general expression:

$$W = \frac{1}{2} C V^2$$

# For next time

- HW #3 → turn in if haven't
- HW #4 → available
- Office Hours immediately after this class (9:30 – 10:00) in WAT214 [M 1:30-2; WF 1-1:30]
- Don't fall behind – 2<sup>nd</sup> Quiz Friday

