

# Course Updates

<http://www.phys.hawaii.edu/~varner/PHYS272-Spr10/physics272.html>

Notes for today:

- 1) Review of Quiz 2 (at end)
- 2) Assignment 5 (Mastering Physics) online and separate, written problems due **Wednesday**
- 3) **Review all of Chap 21-24 for Midterm**
- 4) Schedule for next week:
  - 1) Monday: **holiday**
  - 2) Wednesday: **review**
  - 3) Friday: **Midterm #1**

# Last Time

## Resistors in series:

Current through is same.

Voltage drop across is  $IR_i$




$$R_{\text{effective}} = R_1 + R_2 + R_3 + \dots$$

## Resistors in parallel:


Voltage drop across is same.

Current through is  $V/R_i$

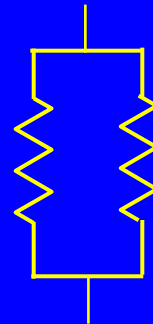


$$\frac{1}{R_{\text{effective}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



## Solved Circuits

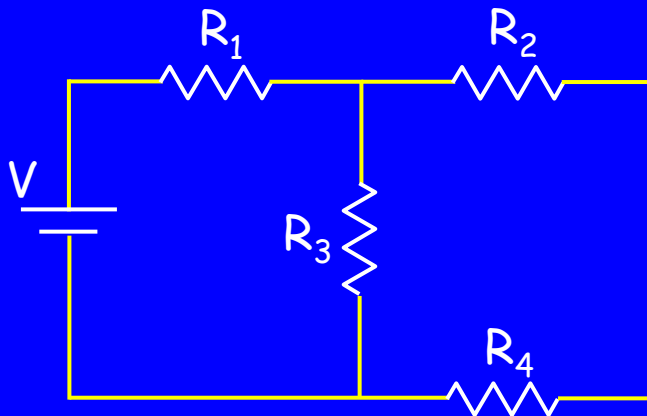

=

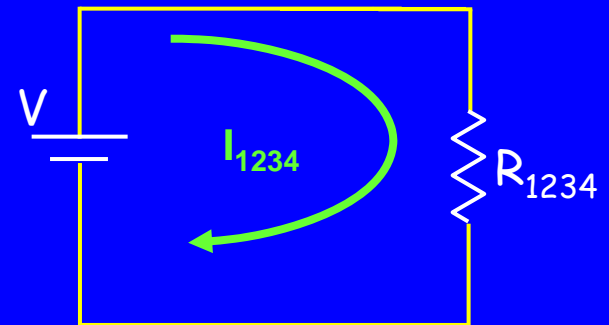

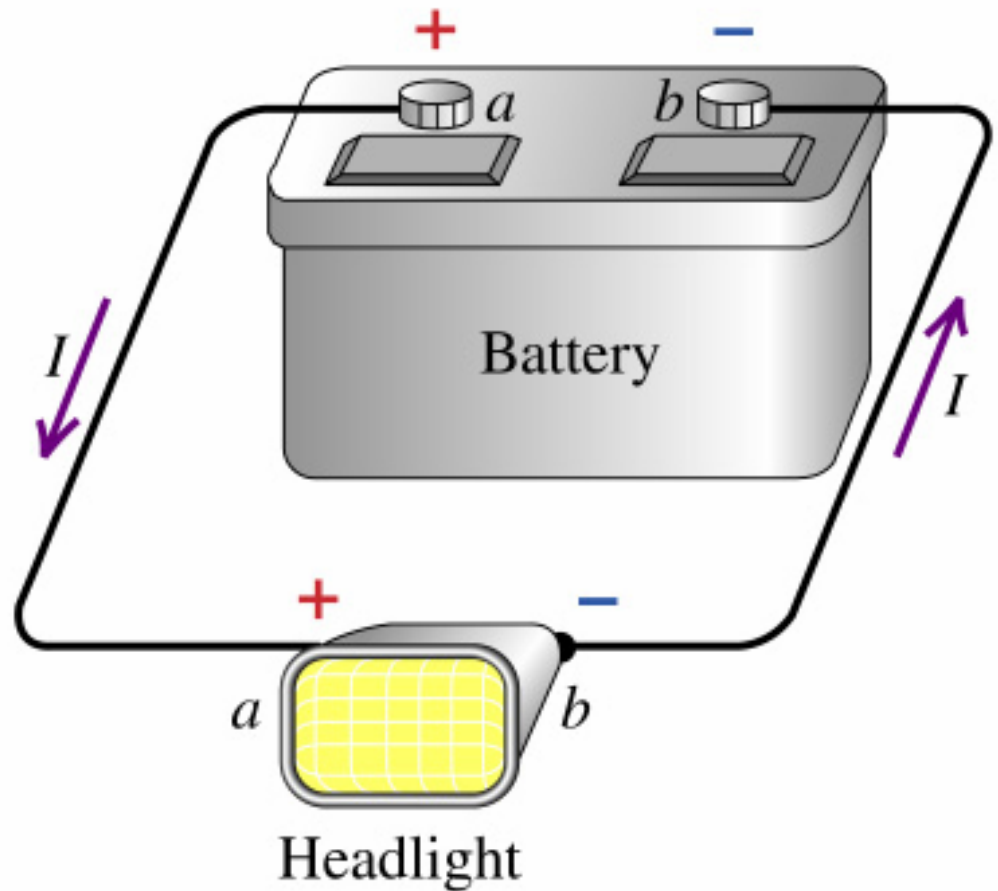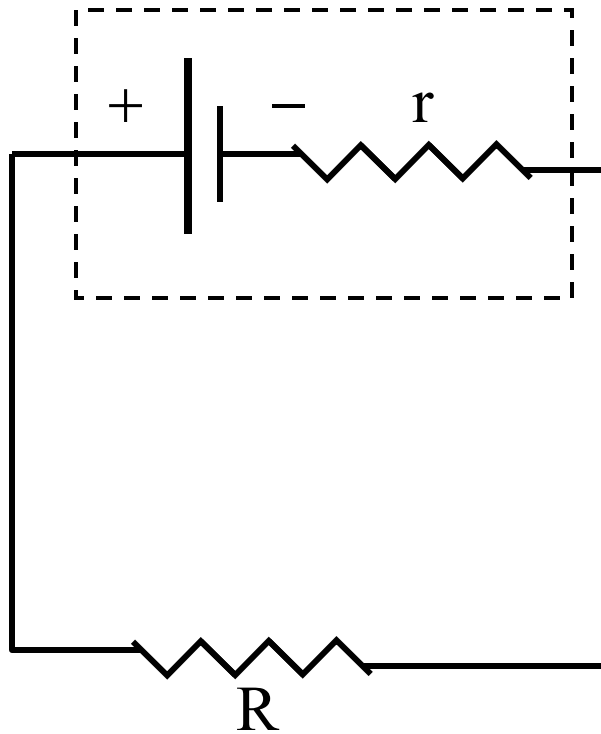Real life example of previous circuit is a car battery and a headlamp



$R$  = resistance in headlight  
 $r$  = internal resistance in battery


Real Battery with 12volts and an internal resistance of 2 ohms in a circuit with a resistor of 4 ohms

$$\mathcal{E} - Ir = IR$$

Rearranging:

$$\mathcal{E} - Ir - IR = 0$$

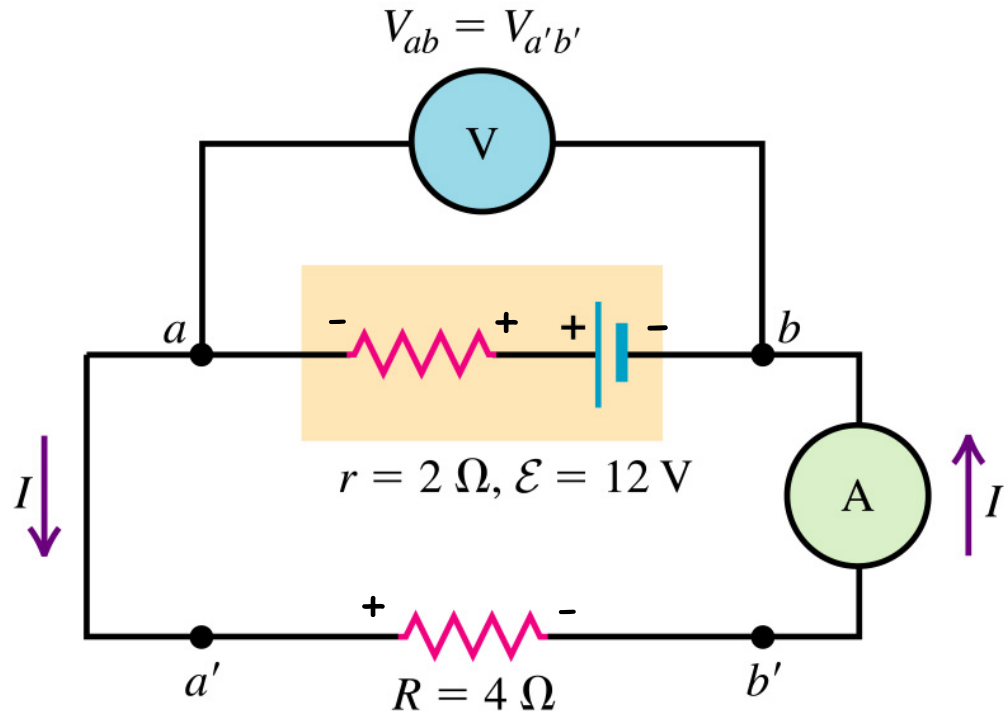Can interpret this as  
the sum of all potential  
differences around a  
closed loop must add to  
zero.



Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

Kirchoff's voltage law or loop rule.


Can define a voltage rise as positive OR a voltage fall as positive.

# Electric Potential/Voltage Diagram of the circuit

Voltage drop across 2 Ohms is 4 volts

Voltage drop across 4 Ohms is 8 volts

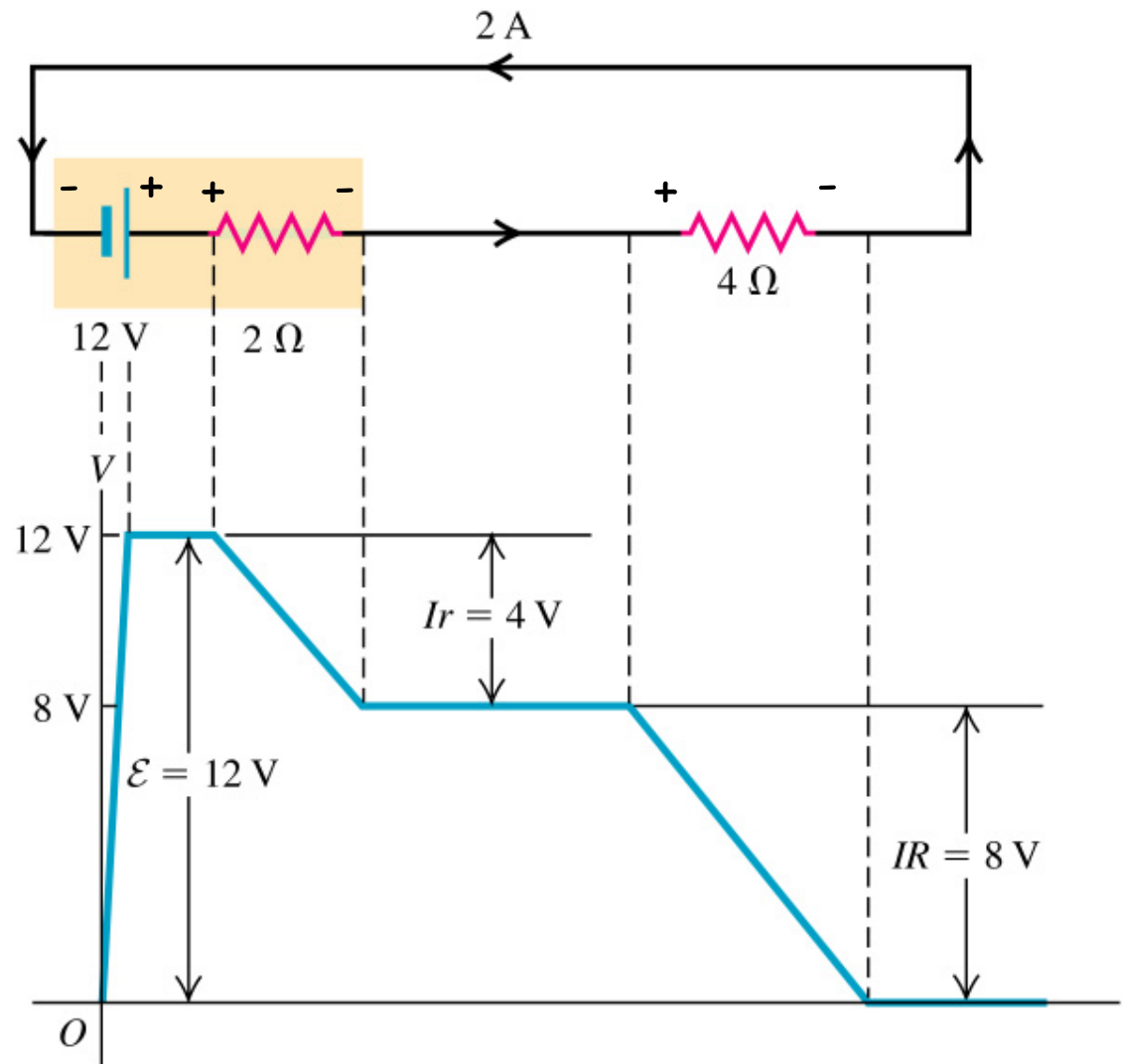NOTE  $4\Omega$  resistor has only 8 of the 12 volts.





## Warm up Exercise

In the circuit shown, the voltage across the  $2\ \Omega$  resistor is 12 volts .

A) What is the emf of the battery?

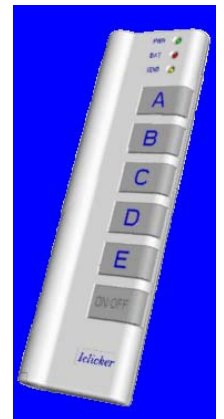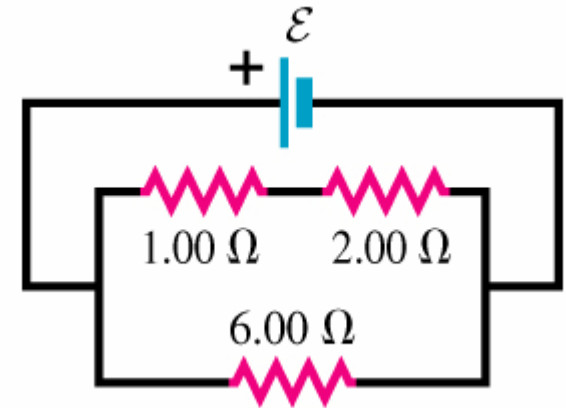- A) 6V
- B) 12V
- C) 18V
- D) 24V
- E) 120V



## Warm up Exercise

In the circuit shown, the voltage across the  $2\ \Omega$  resistor is 12 volts .

A) What is the emf of the battery?


A) 6V

B) 12V

C) 18V

D) 24V

E) 120V

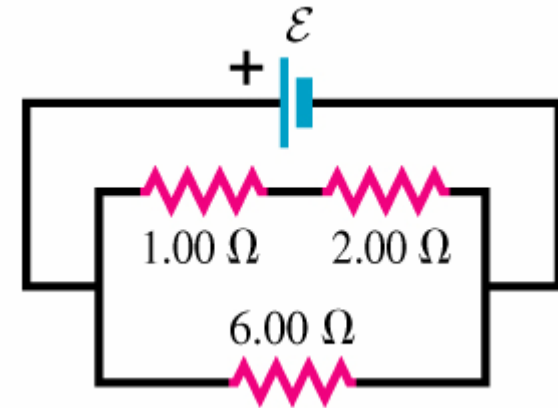


$$I_2 = \frac{V_2}{R_2} = \frac{12V}{2\ \Omega} = 6A$$

$$V_1 = I_1 R_1 = (6A)(1\ \Omega) = 6V$$

$$\mathcal{E} = V_1 + V_2 = 18V$$

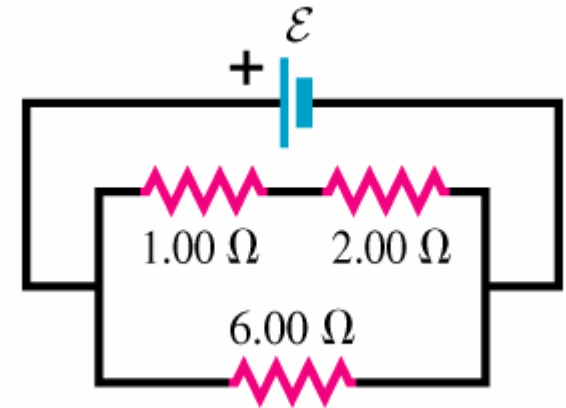
## Warm up Exercise

In the circuit shown, the voltage across the  $2\ \Omega$  resistor is 12 volts .



B) What is the current through the  $6.00\ \text{ohm}$  resistor?

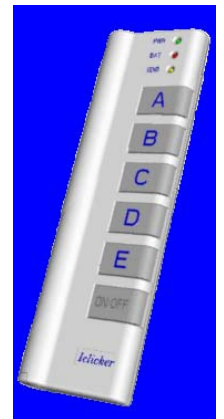
- A)  $2\text{ A}$
- B)  $3\text{ A}$
- C)  $4\text{ A}$
- D)  $8\text{ A}$
- E)  $12\text{ A}$




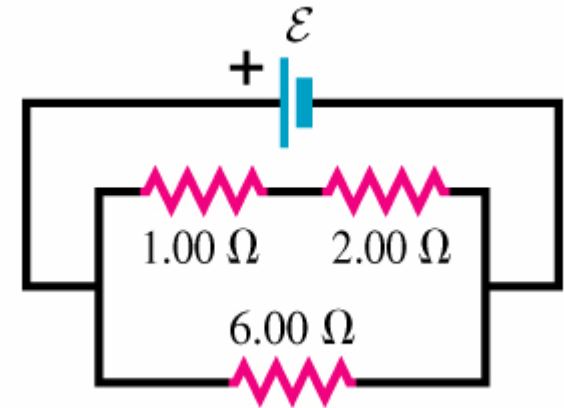
## Warm up Exercise

In the circuit shown, the voltage across the  $2\ \Omega$  resistor is 12 volts .



B) What is the current through the  $6.00\ \text{ohm}$  resistor?

A)  $2\ \text{A}$

B)  $3\ \text{A}$


C)  $4\ \text{A}$

D)  $8\ \text{A}$

E)  $12\ \text{A}$

$$I_6 = \frac{\mathcal{E}}{R_6} = \frac{18\text{V}}{6\ \Omega} = 3\text{A}$$

## Calculation 3

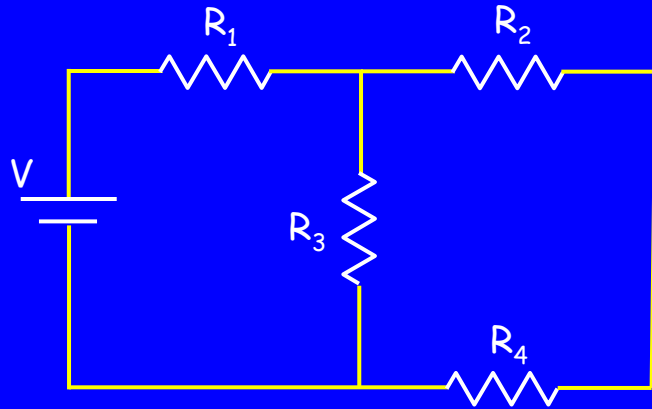


In the circuit shown:  $V = 18\text{V}$ ,  
 $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ , and  $R_4 = 4\Omega$ .

What is  $V_2$ , the voltage across  $R_2$ ?


- Combine Resistances:

$R_2$  and  $R_4$  are connected in series =  $R_{24} = 2 + 4 = 6\Omega$

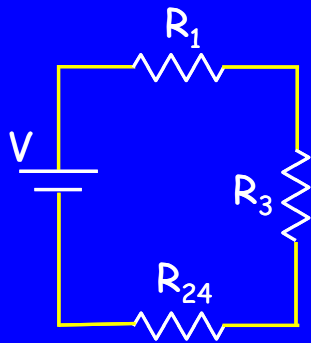
Redraw the circuit using the equivalent resistor  $R_{24}$  = series combination of  $R_2$  and  $R_4$ .



(A)

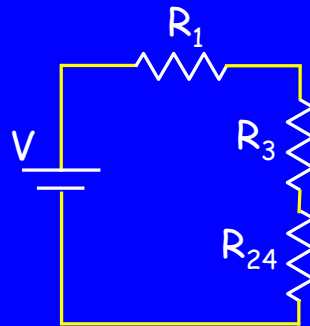


(B)

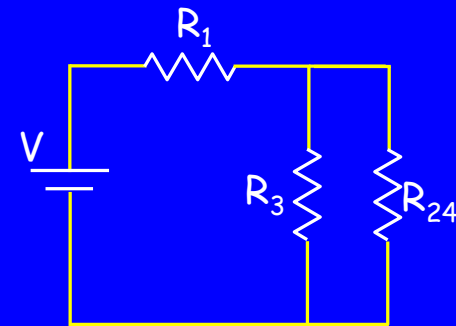

(C)
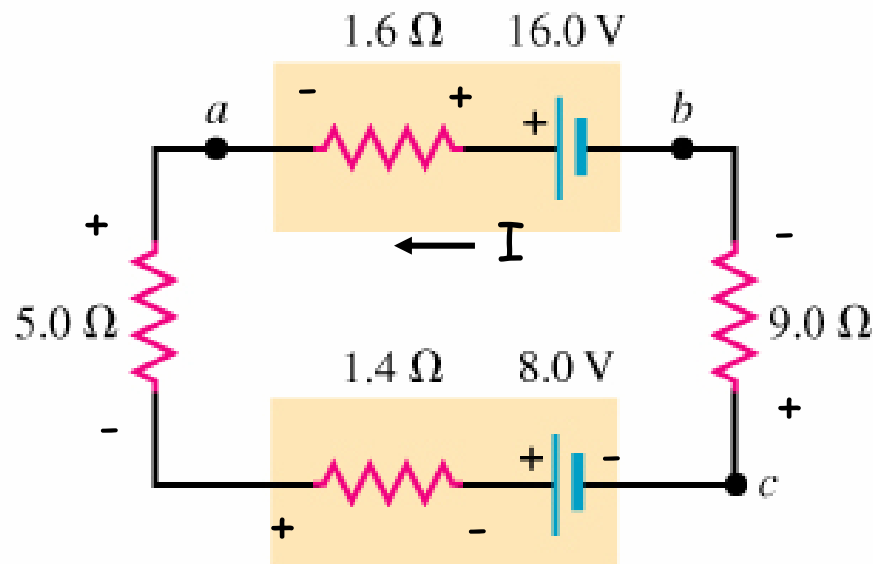
# Loopy-ness

Kirchoff's Voltage loop law: **sum of voltages = 0**



Need to determine  $I$

How to know which direction to go around loop?

$$\sum_i V_i = V_{eq}$$

$$\sum_i R_i = R_{eq}$$

$$I = \frac{V_{eq}}{R_{eq}}$$


Doesn't matter, because **sign of  $I$  will tell**

**Warning!!** need Thevenin Equivalence to make General
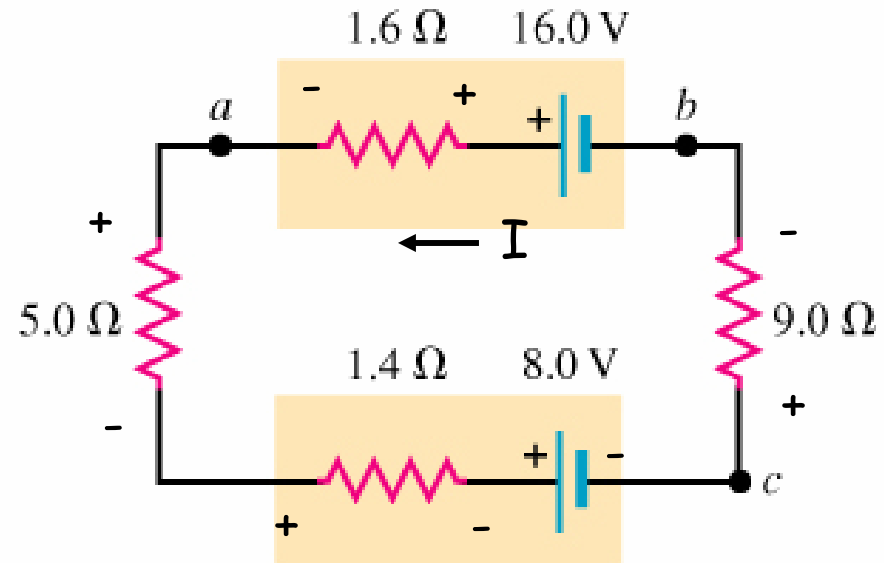
## Y&F 25.36

The circuit shown in the figure contains two batteries, each with an emf and an internal resistance, and two resistors.

- Find the direction and magnitude of the current in the circuit
- Find the terminal voltage  $V_{ab}$  of the 16.0-V battery.
- Find the potential difference  $V_{bc}$  of point b with respect to point c.



A.) Use Kirchhoff's loop law:

$$16V - 1.6\Omega I - 5.0\Omega I - 1.4\Omega I - 8V - 9.0\Omega I = 0$$

$$8V - 17\Omega I = 0$$

$$I = \frac{8}{17} A = 0.471 A$$


B.)  $V_{ab} = 16V - I(1.6\Omega) = 16V - (0.471 A)(1.6\Omega) = 15.2 V$

C.)  $V_{bc} = -I(9.0\Omega) = -(0.471 A)(9.0\Omega) = -4.24 V$
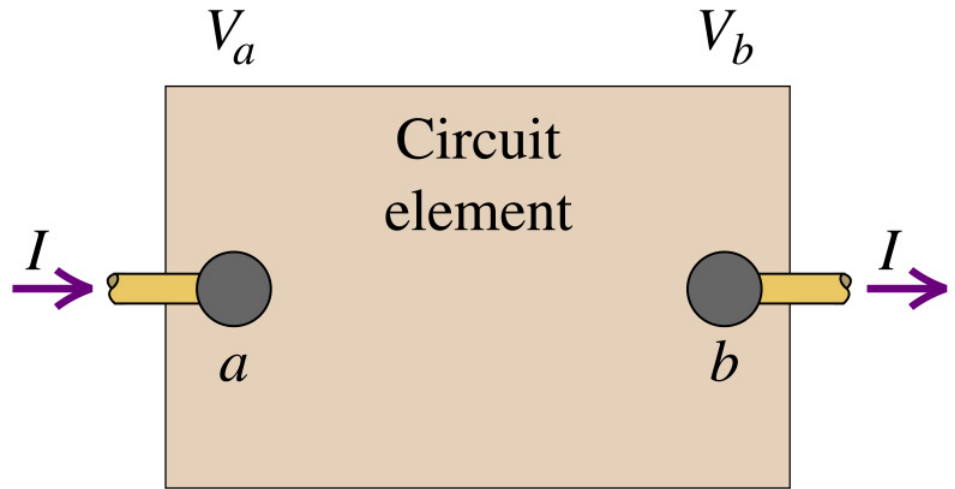
# Power

Very important use of electricity.

Suppose we have a circuit element that has a voltage drop of  $V_{ab} = V_a - V_b$  and a current flow of  $I$ .



What is the change in potential energy in this circuit element?

$$dU = (V_{ab}) dq$$

What is the time rate change in potential energy in this circuit element?


$$P = \frac{dU}{dt} = (V_{ab}) \frac{dq}{dt} = (V_{ab}) I$$

Power,  $P$ , is the time rate change in energy and equals voltage  $\times$  current

$$P = (V_{ab}) I \quad \text{Units = voltage-amps = Watts}$$

## Power


Resistor

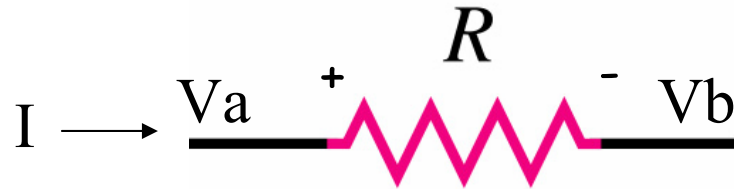

$$\text{Power } P = I (V_a - V_b) = IV = I (IR) = I^2 R = V^2/R$$

Electrical power converted to Joule heat.

EMF

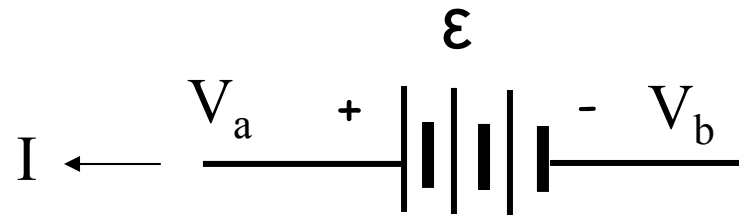

$$\text{Power } P = I (V_a - V_b) = I \varepsilon$$

Electrical power can be + or -  
depending on direction of  $I$ .

## Power Example of Battery and resistor

What is the power in resistor R?

$$I^2 R = 2 * 2 * 4 = 16 \text{ W}$$


What is the power in internal resistance r?

$$I^2 r = 2 * 2 * 2 = 8 \text{ W}$$

What is the rate of energy conversion of the battery?

$$\mathcal{E} I = 12 * 2 = 24 \text{ W}$$

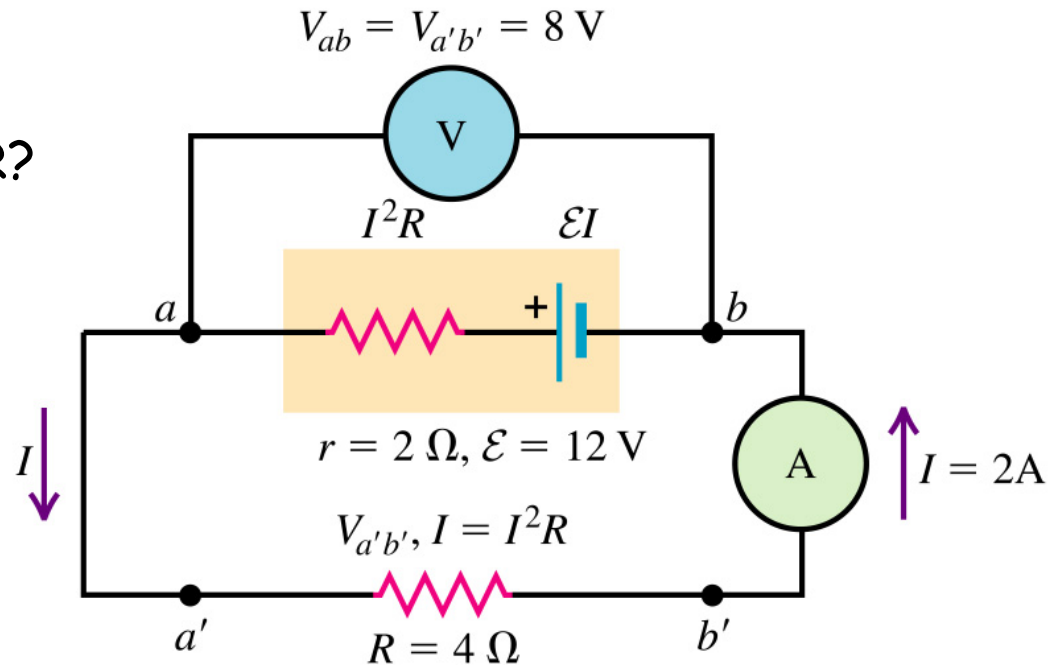=> Energy conversion rate equals sum of power in both R and r



Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

## Y&F Problem 25.47

The capacity of a storage battery in your car is rated in amp-hours. A 12 volt battery rated at  $50 \cdot A \cdot h$ , can supply a 50 amps for 1 hour at 12 volts or 25 amps for 2 hours etc.

A.) What is the total energy supplied by this battery?

$$P = \frac{dU}{dt} = IV = (50A)(12V) = 600W$$

$$U = Pt = (600W)(1hr)(3600s/hr) = 2.16MJ$$

B.) if a electric battery charger supplies 0.45 kW, how long does it take to fully charge a dead battery?


$$U = Pt$$

$$t = U / P = (2.16MJ) / 0.45kW)$$

$$= 4680s = 78m$$



# Gauss' Law

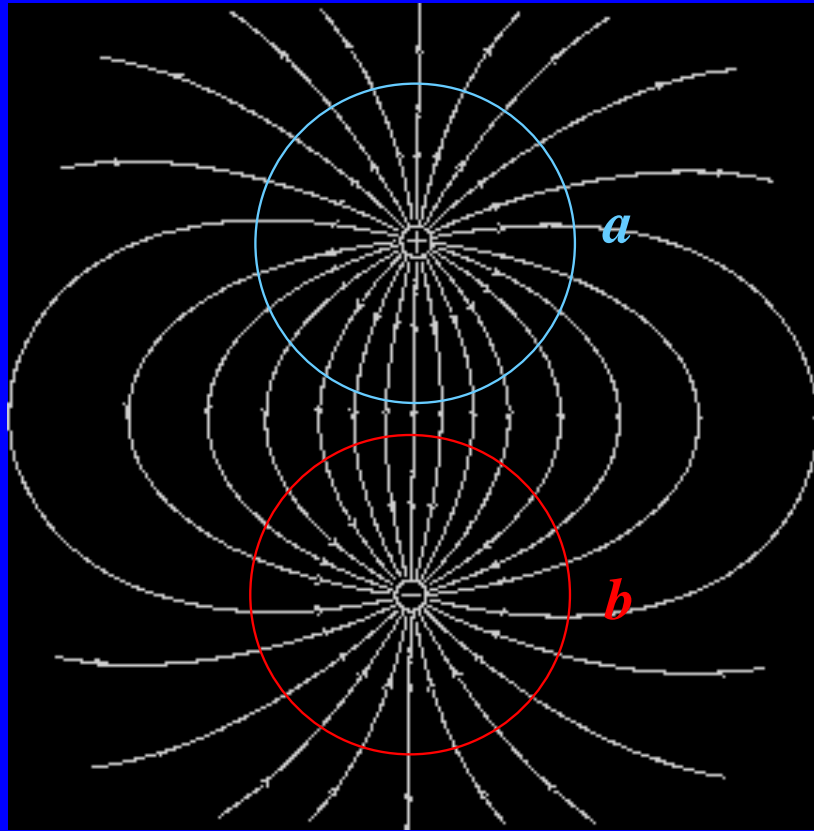

$$\oint \vec{E} \cdot d\vec{A} = \Phi_E = \frac{q_{\text{enclosed}}}{\epsilon_0}$$

# Gauss $\Rightarrow$ Coulomb

- We now illustrate this for the field of the point charge and prove that Gauss' Law implies Coulomb's Law.

- Symmetry  $\Rightarrow$   $E$ -field of point charge is radial and spherically symmetric
- Draw a sphere of radius  $R$  centered on the charge.

- Why?


$E$  normal to every point on the surface

$$\Rightarrow \vec{E} \cdot d\vec{A} = E dA$$

$E$  has same value at every point on the surface


$\Rightarrow$  can take  $E$  outside of the integral!

- Therefore,  $\oint \vec{E} \cdot d\vec{A} = \oint E dA = E \oint dA = 4\pi R^2 E$  !

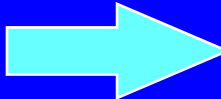– Gauss' Law  $\epsilon_0 4\pi R^2 E = Q$  


$$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{R^2}$$

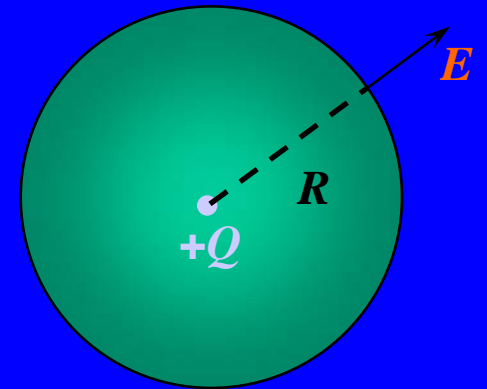- We are free to choose the surface in such problems... we call this a "Gaussian" surface


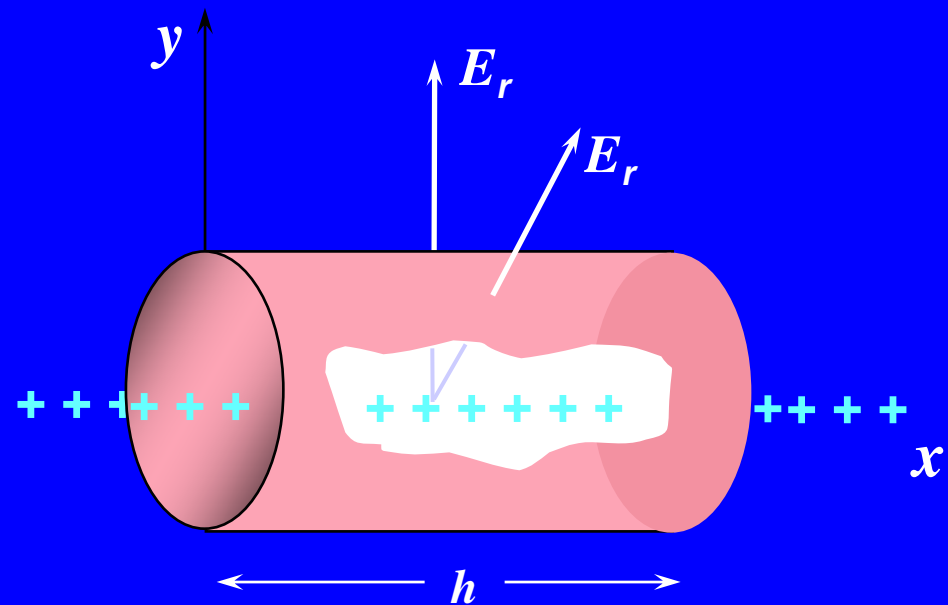
# Infinite Line of Charge

- Symmetry  $\Rightarrow$   $E$ -field must be  $\perp$  to line and can only depend on distance from line
- Therefore, CHOOSE Gaussian surface to be a cylinder of radius  $r$  and length  $h$  aligned with the  $x$ -axis.



## • Apply Gauss' Law:

- On the ends,  $\vec{E} \bullet d\vec{A} = 0$
- On the barrel,  $\oint \vec{E} \bullet d\vec{A} = 2\pi r h E$  AND  $q = \lambda h \Rightarrow$

$$E = \frac{\lambda}{2\pi\epsilon_0 r}$$

**NOTE:** we have obtained here the same result as we did last lecture using Coulomb's Law. The symmetry makes today's derivation easier.

# Gauss' Law: Help for the Homework Problems

Midterm

- Gauss' Law is ALWAYS VALID!

$$\epsilon_0 \oint \vec{E} \cdot d\vec{A} = q_{\text{enclosed}}$$

- What Can You Do With This?

If you have (a) spherical, (b) cylindrical, or (c) planar symmetry  
AND:

- If you know the charge (RHS), you can calculate the electric field (LHS)
- If you know the field (LHS, usually because  $E=0$  inside conductor), you can calculate the charge (RHS).

- **Spherical Symmetry:** Gaussian surface = sphere of radius  $r$

**LHS:**  $\epsilon_0 \oint \vec{E} \cdot d\vec{A} = 4\pi\epsilon_0 r^2 E$

**RHS:**  $q = \text{ALL charge inside radius } r$

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2}$$

- **Cylindrical symmetry:** Gaussian surface = cylinder of radius  $r$

**LHS:**  $\epsilon_0 \oint \vec{E} \cdot d\vec{A} = \epsilon_0 2\pi r L E$

**RHS:**  $q = \text{ALL charge inside radius } r, \text{ length } L$

$$E = \frac{\lambda}{2\pi\epsilon_0 r}$$

- **Planar Symmetry:** Gaussian surface = cylinder of area  $A$

**LHS:**  $\epsilon_0 \oint \vec{E} \cdot d\vec{A} = \epsilon_0 2 A E$

**RHS:**  $q = \text{ALL charge inside cylinder} = \sigma A$

$$E = \frac{\sigma}{2\epsilon_0}$$

# Prez Day Weekend Fun

- HW #5 → due next Wednesday
- Now is time to resolve any questions you may have about previous HW, Quiz
- Office Hours usually after this class (9:30 – 10:00) in WAT214 – today (1-1:30pm)

