

Course Updates

<http://www.phys.hawaii.edu/~varner/PHYS272-Spr10/physics272.html>

Notes for today:

- 1) Complete Chap 26, Problem session Friday
- 2) Assignment 6 (Mastering Physics) online and separate, written problems due **Monday**
- 3) **Quiz 3 on Friday**
- 4) Review Midterm 1


Kirchhoff's Rules

Kirchhoff's rules are statements used to solve for currents and voltages in complicated circuits. The rules are

Rule I. Sum of currents into any junction is zero.

$$\sum_i I_i = 0$$

Why? Since charge is conserved.

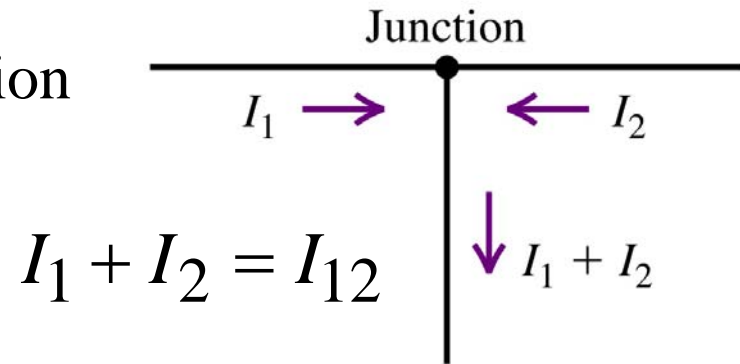


Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

Rule II. Sum of potential differences in any loop is zero. (This includes emfs)





$$\sum_i V_i = 0$$

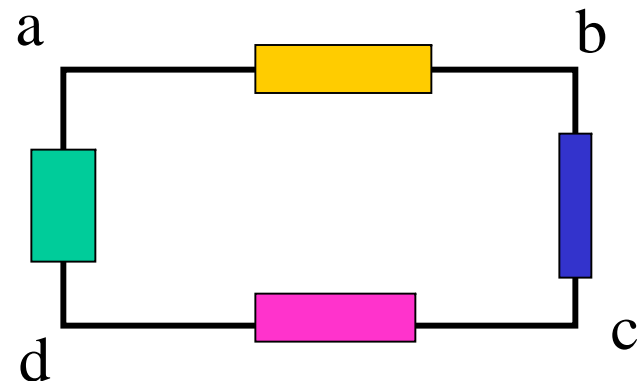Why? Since potential (energy) is conserved



$$V_{ab} + V_{bc} + V_{cd} + V_{da} = 0$$

RC Circuits

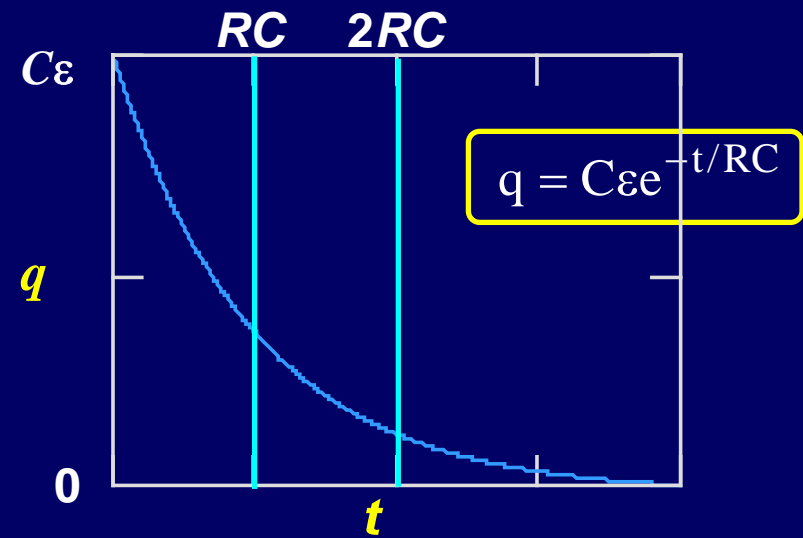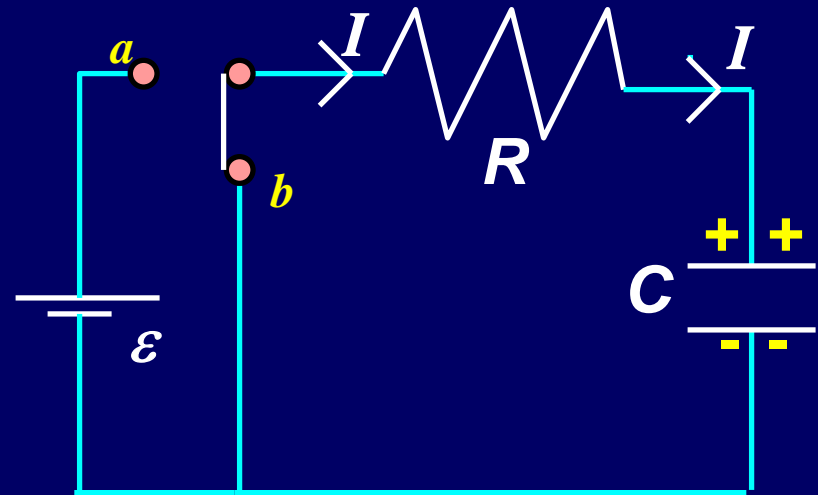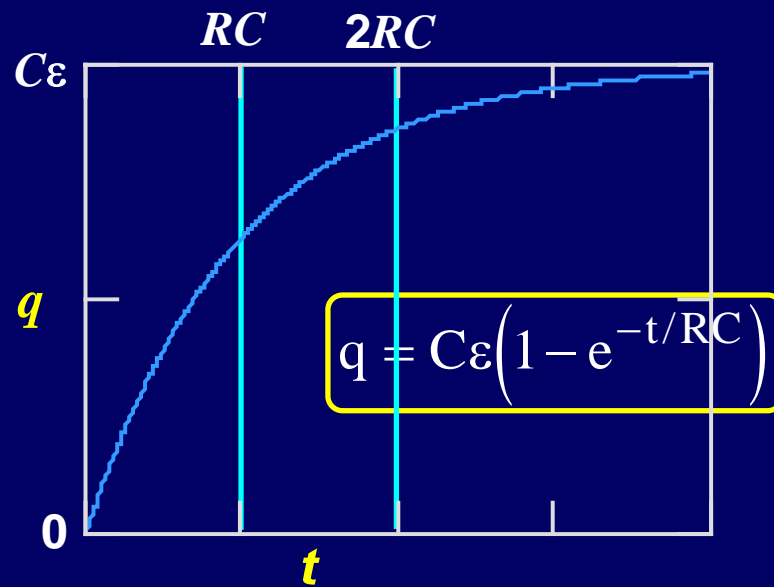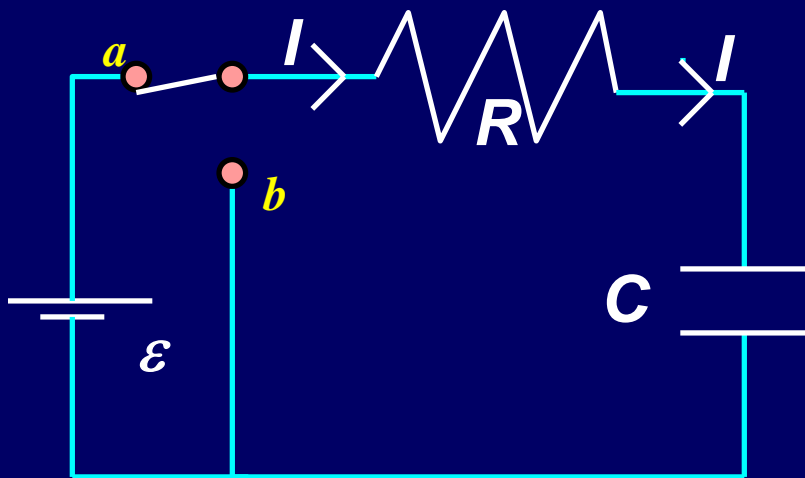


RC Circuits

(Time-varying currents, charging)

- Charge capacitor:

C initially uncharged;
connect switch to a at $t=0$

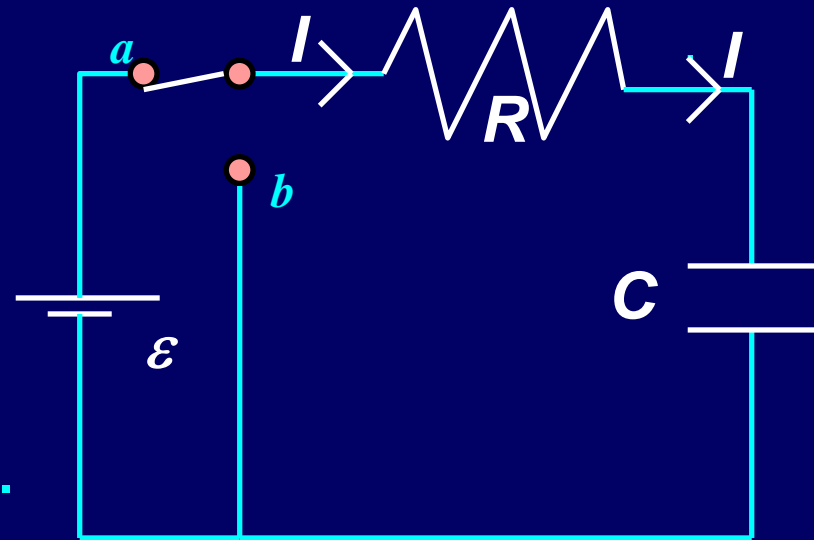Calculate current and
charge as function of time.



- Loop theorem $\Rightarrow \mathcal{E} - IR - \frac{Q}{C} = 0$

Would it matter where R
is placed in the loop??

- Convert to differential equation for Q :

$$I = \frac{dQ}{dt} \Rightarrow \boxed{\mathcal{E} = R \frac{dQ}{dt} + \frac{Q}{C}}$$

No!

Charging Capacitor

- **Charge capacitor:**

$$\varepsilon = R \frac{dQ}{dt} + \frac{Q}{C}$$


- **Guess solution:**

$$Q = C\varepsilon(1 - e^{-t/RC})$$

- **Check that it is a solution:**

$$\frac{dQ}{dt} = C\varepsilon e^{-t/RC} \left(-\frac{1}{RC} \right)$$
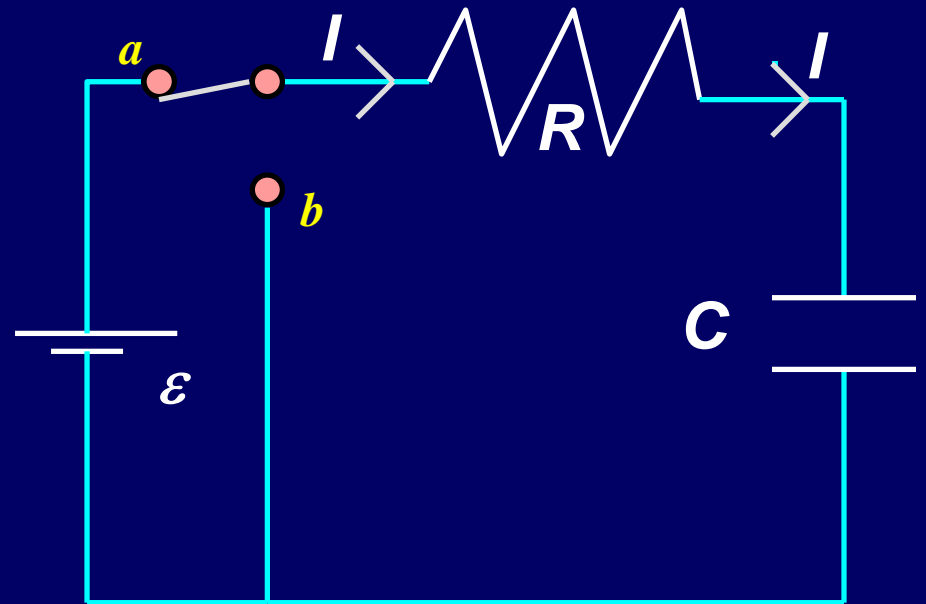
$$\Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = -\varepsilon e^{-t/RC} + \varepsilon(1 - e^{-t/RC}) = \varepsilon \quad !$$



Note that this “guess” fits the boundary conditions:

$$t = 0 \Rightarrow Q = 0$$

$$t = \infty \Rightarrow Q = C\varepsilon$$

Charging Capacitor

- Charge capacitor:

$$Q = C\varepsilon(1 - e^{-t/RC})$$


- Current is found from differentiation:


$$I = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$



Conclusion:

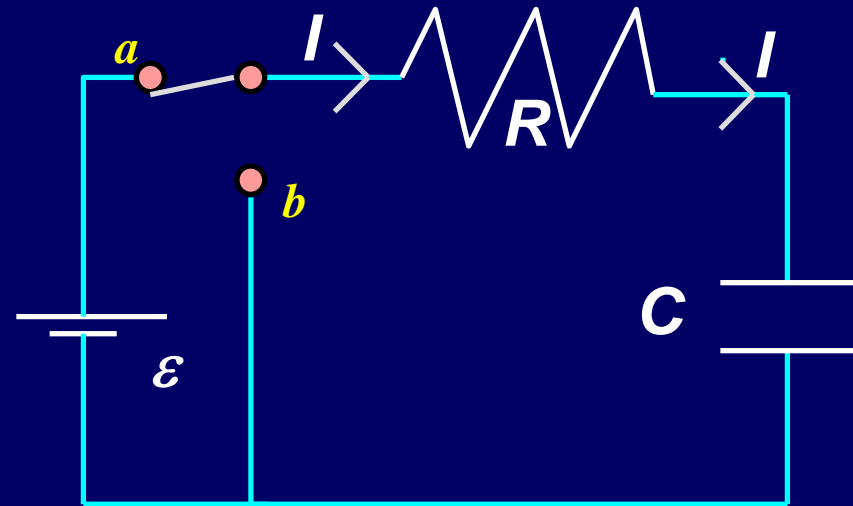- Capacitor reaches its final charge ($Q = C\varepsilon$) exponentially with time constant $\tau = RC$.
- Current decays from max ($= \varepsilon/R$) with same time constant.



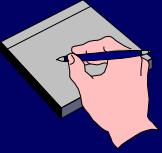

Charging Capacitor

Charge on C

$$Q = C\varepsilon(1 - e^{-t/RC})$$

$$\text{Max} = C\varepsilon$$


$$63\% \text{ Max at } t = RC$$

Current

$$I = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$

$$\text{Max} = \varepsilon/R$$

$$37\% \text{ Max at } t = RC$$

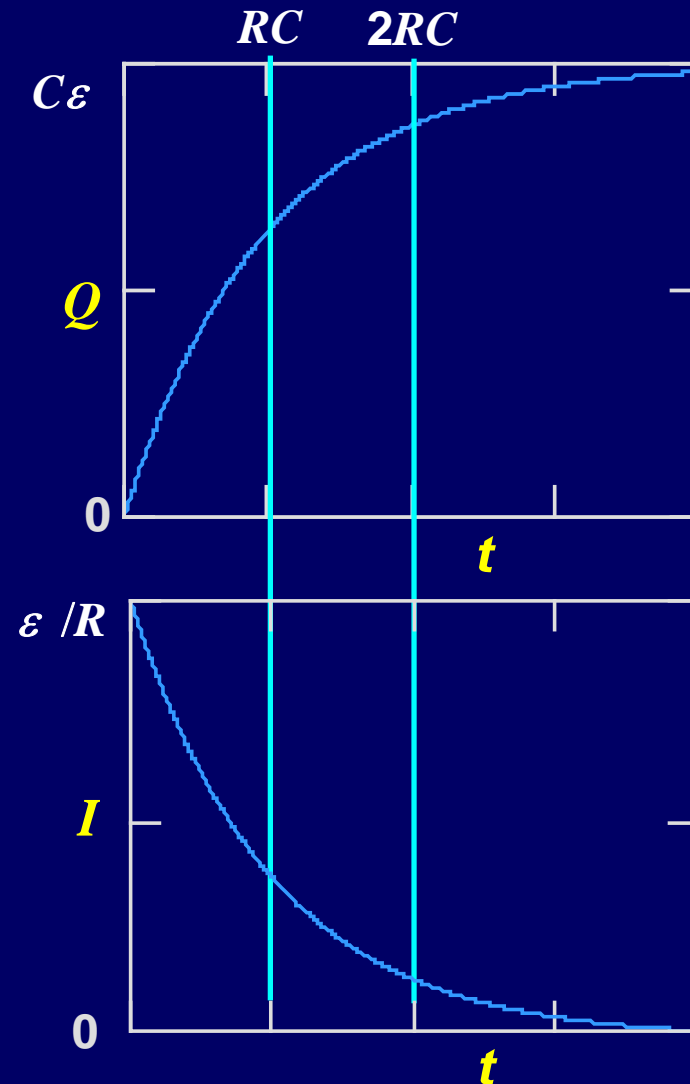

Discharging Capacitor

$$R \frac{dQ}{dt} + \frac{Q}{C} = 0$$


- **Guess solution:**

$$Q = Q_0 e^{-t/\tau} = C \varepsilon e^{-t/RC}$$

- **Check that it is a solution:**

$$\frac{dQ}{dt} = C \varepsilon e^{-t/RC} \left(-\frac{1}{RC} \right)$$
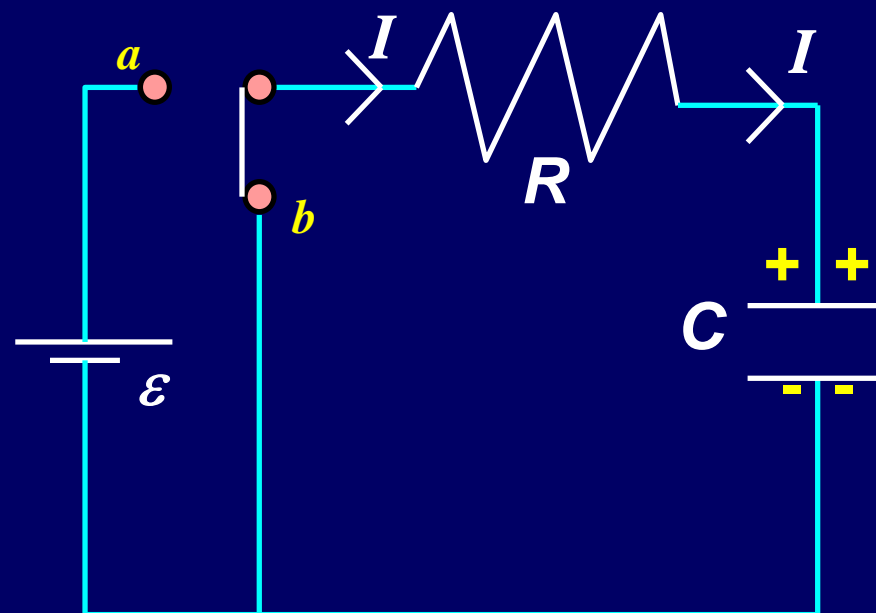
$$\Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = -\varepsilon e^{-t/RC} + \varepsilon e^{-t/RC} = 0 !$$



Note that this “guess” fits the boundary conditions:

$$t = 0 \Rightarrow Q = C \varepsilon$$

$$t = \infty \Rightarrow Q = 0$$

Discharging Capacitor


- Discharge capacitor:

$$Q = Q_0 e^{-t/\tau} = C \varepsilon e^{-t/RC}$$

- Current is found from differentiation:


$$I = \frac{dQ}{dt} = -\frac{\varepsilon}{R} e^{-t/RC}$$

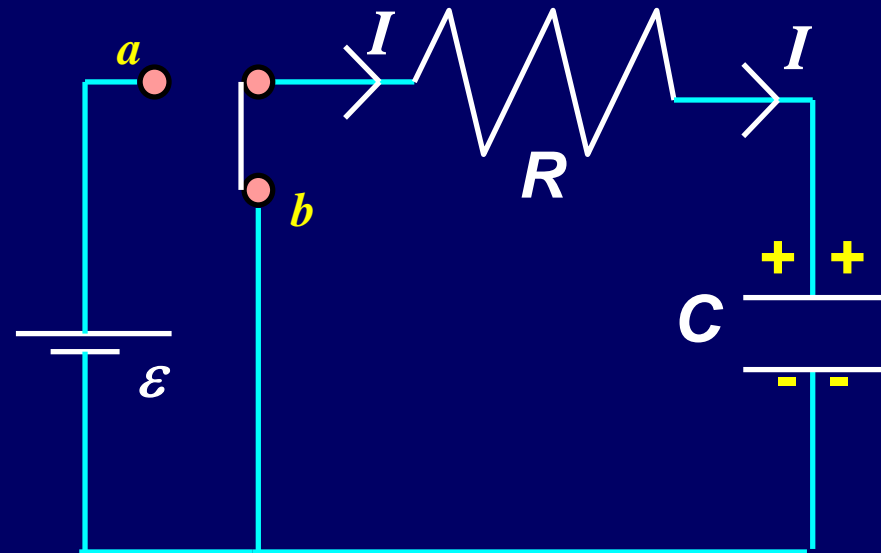Minus sign:
Current is opposite to
original definition,
i.e., charges flow
away from capacitor.



Conclusion:

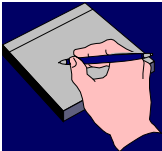- Capacitor discharges exponentially with time constant $\tau = RC$
- Current decays from initial max value ($= -\varepsilon/R$) with same time constant



Discharging Capacitor

Charge on C

$$Q = C\varepsilon e^{-t/RC}$$

$$\text{Max} = C\varepsilon$$


$$37\% \text{ Max at } t = RC$$

Current


$$I = \frac{dQ}{dt} = -\frac{\varepsilon}{R} e^{-t/RC}$$

$$\text{"Max"} = -\varepsilon/R$$

$$37\% \text{ Max at } t = RC$$

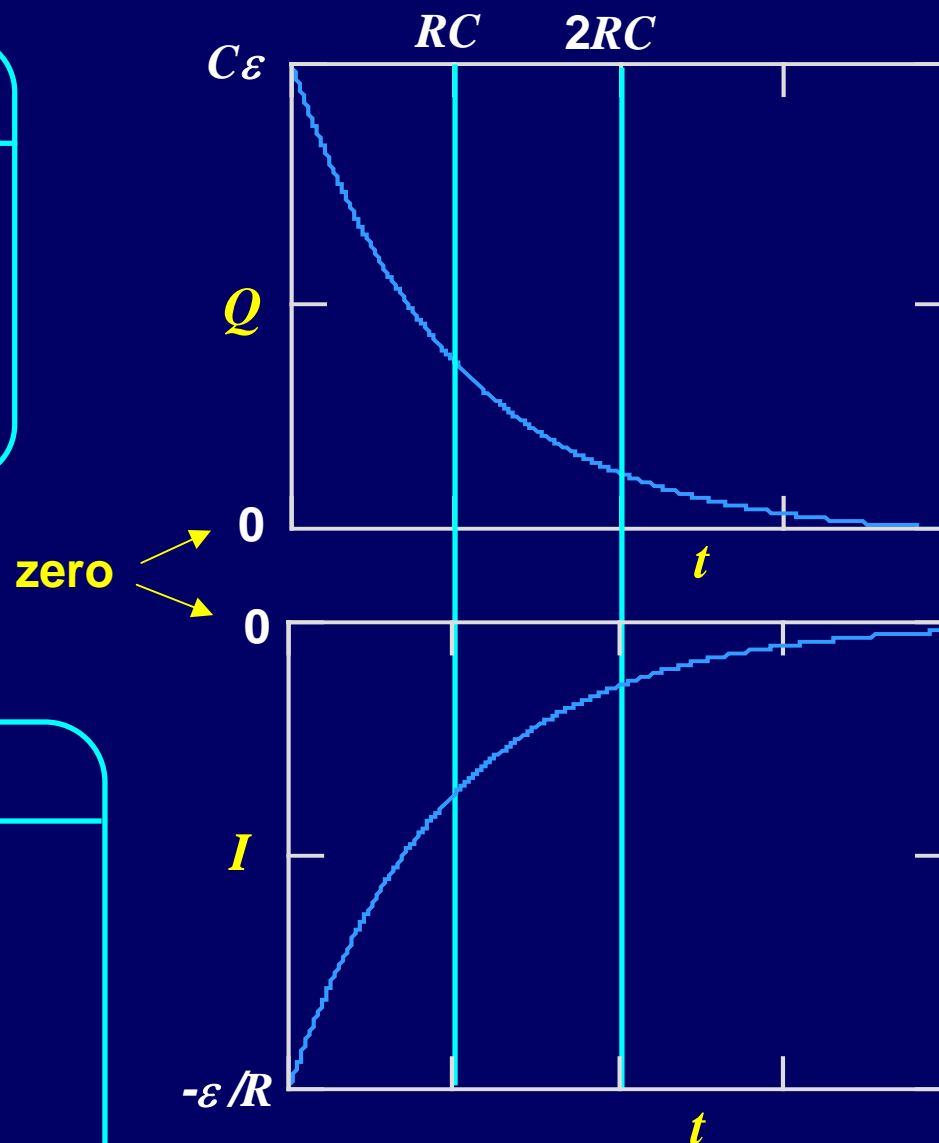


Midterm 1 statistics

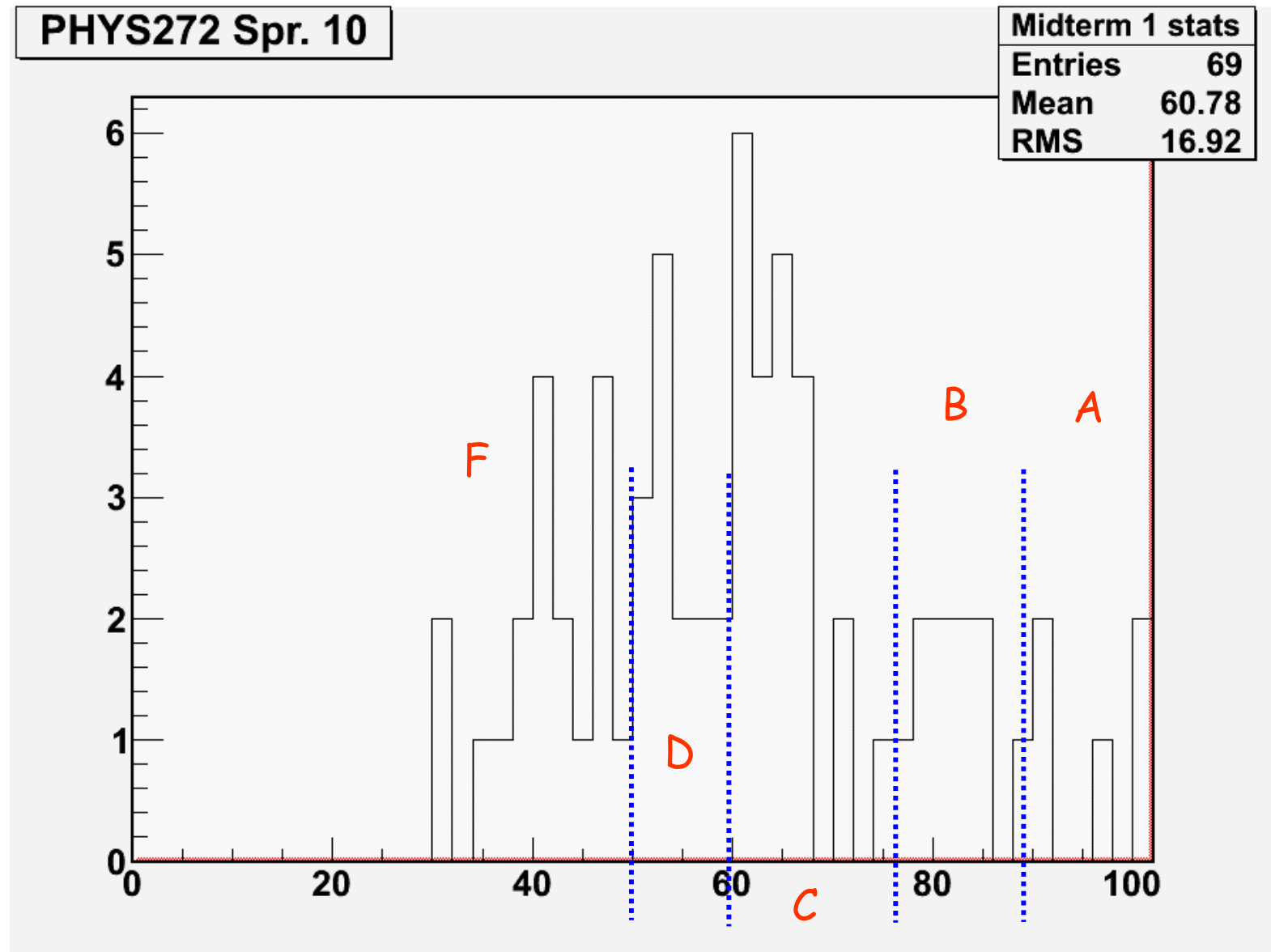

Cumulative statistics

PHYS272 Spr. 10

| Midterm 1 stats | |
|-----------------|-------|
| Entries | 69 |
| Mean | 791 |
| RMS | 173.2 |

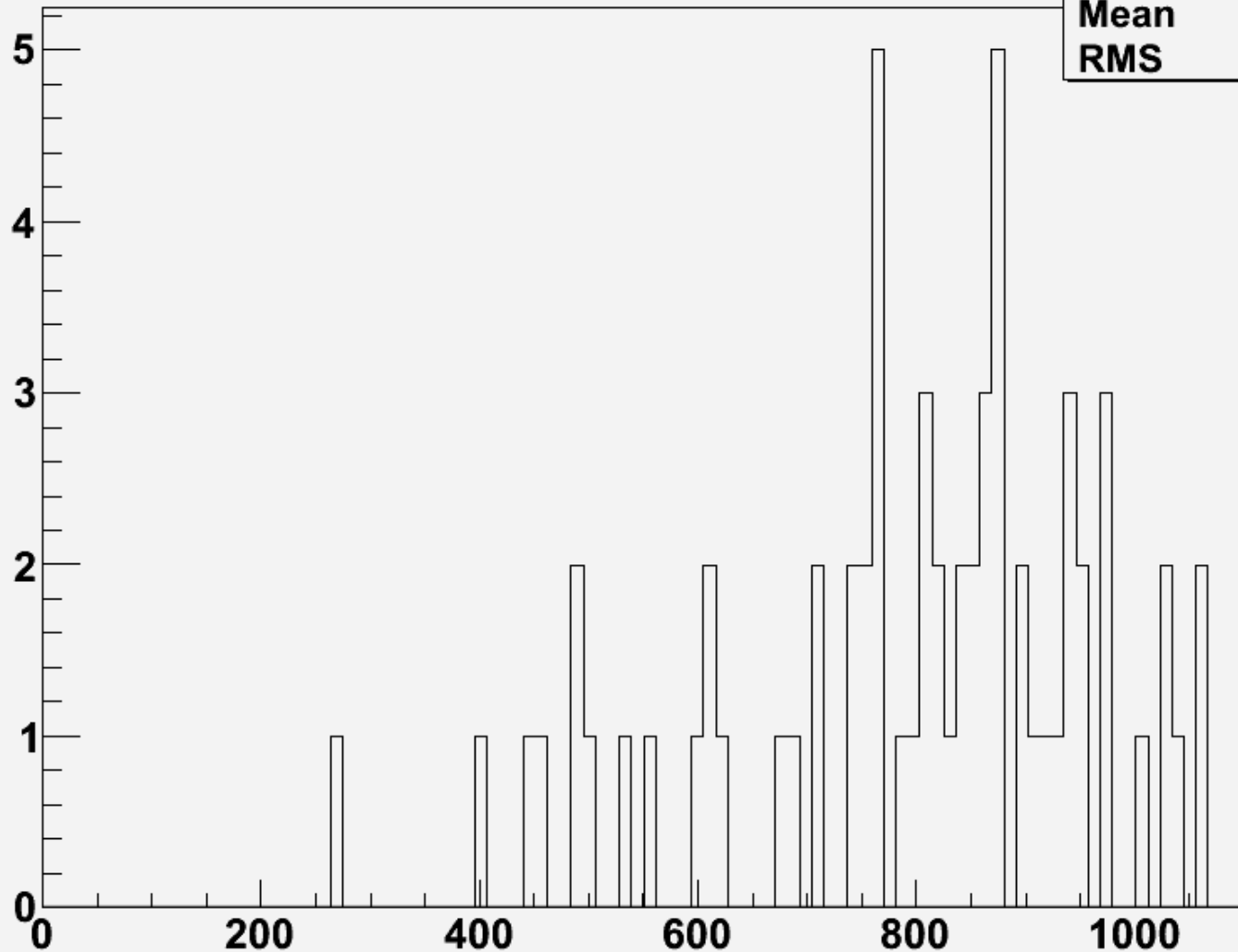

Midterm Review

- Not many systematic, consistent problems
- However, some recurrent themes:
 - Electric Potential (V) vs. Potential Energy (U)
 - Electric field sums as vector quantity
 - Potential field (V) sums as a scalar
 - Area of a circle is πr^2
- Detailed points breakdown (by roster ID) linked from course webpage
- Will go over in outline form problems next...

For next time

- HW #6 Assigned → due next Monday
- Quiz #3 on Friday
- Problem session Friday prior to quiz

