

Course Updates

<http://www.phys.hawaii.edu/~varner/PHYS272-Spr10/physics272.html>


Reminders:

- 1) Assignment #10 → due Today
- 2) Quiz # 5 **Friday** (Chap 29, 30)
- 3) Start AC Circuits


Alternating Currents (Chap 31)

In this chapter we study circuits where the battery is replaced by a sinusoidal voltage or current source.

$$v(t) = V_0 \cos(\omega t) \quad \text{or} \quad i(t) = I_0 \cos(\omega t)$$

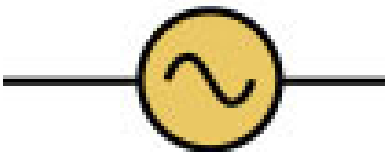The circuit symbol is, 

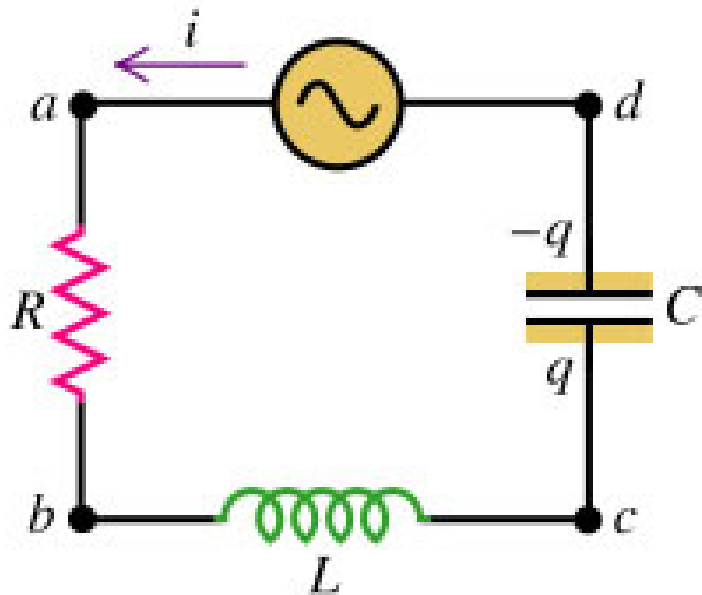An example of an LRC circuit connected to sinusoidal source is,



Important:
I(t) is same throughout - just like DC case.

Alternating Currents

Since the currents & voltages are sinusoidal, their values change over time and the averages are zero.

A more useful description of sinusoidal currents and voltages are given by considering the average of the square of this quantities.

We define the RMS (root mean square), which is the square root of the average of ,

$$i^2(t) = (I_0 \cos(\omega t))^2$$

$$\langle i^2(t) \rangle = \langle (I_0 \cos(\omega t))^2 \rangle = I_0^2 \frac{1}{2} (1 + \langle \cos(2\omega t) \rangle) = \frac{I_0^2}{2}$$


$$I_{RMS} = \sqrt{\langle i^2(t) \rangle} = \frac{I_0}{\sqrt{2}}$$

Alternating Currents ; Phasors

A convenient method to describe currents and voltages in AC circuits is "Phasors". Since currents and voltages in circuits with capacitors & inductors have different phase relations, we introduce a phasor diagram. For a current, $i = I \cos(\omega t)$

We can represent this by a vector rotating about the origin. The angle of the vector is given by ωt and the magnitude of the current is its projection on the X-axis.

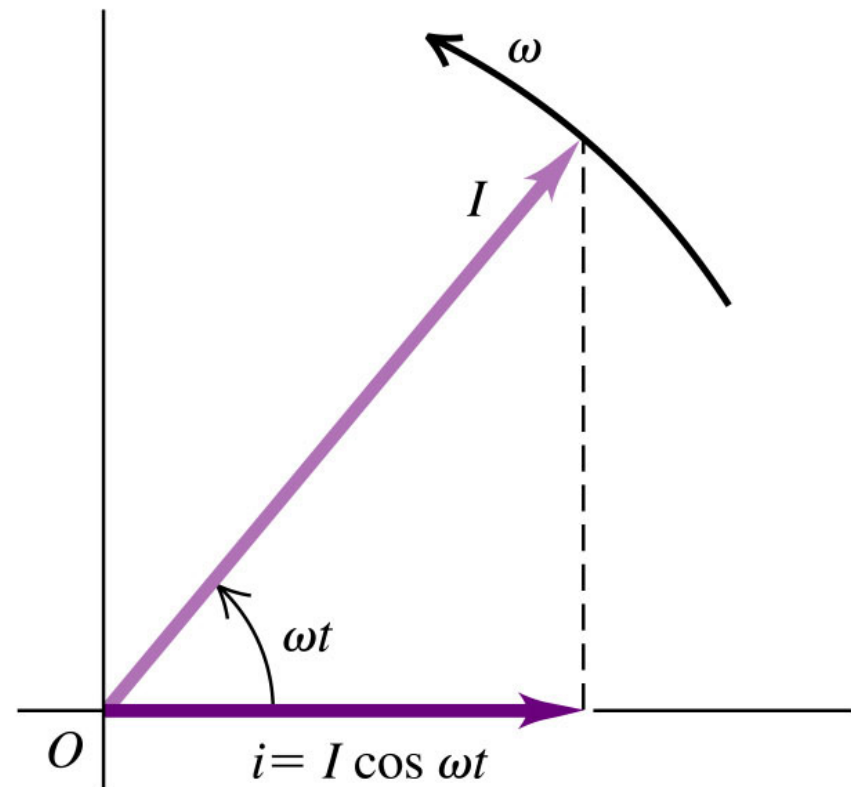If we plot simultaneously currents & voltages of different components we can display different phases .




© Pearson Education, Inc., publishing as Addison Wesley.

Note this method is equivalent to imaginary numbers approach where we take the real part (x-axis projection) for the magnitude



“Beam me up Scotty –
It ate my phasor!”

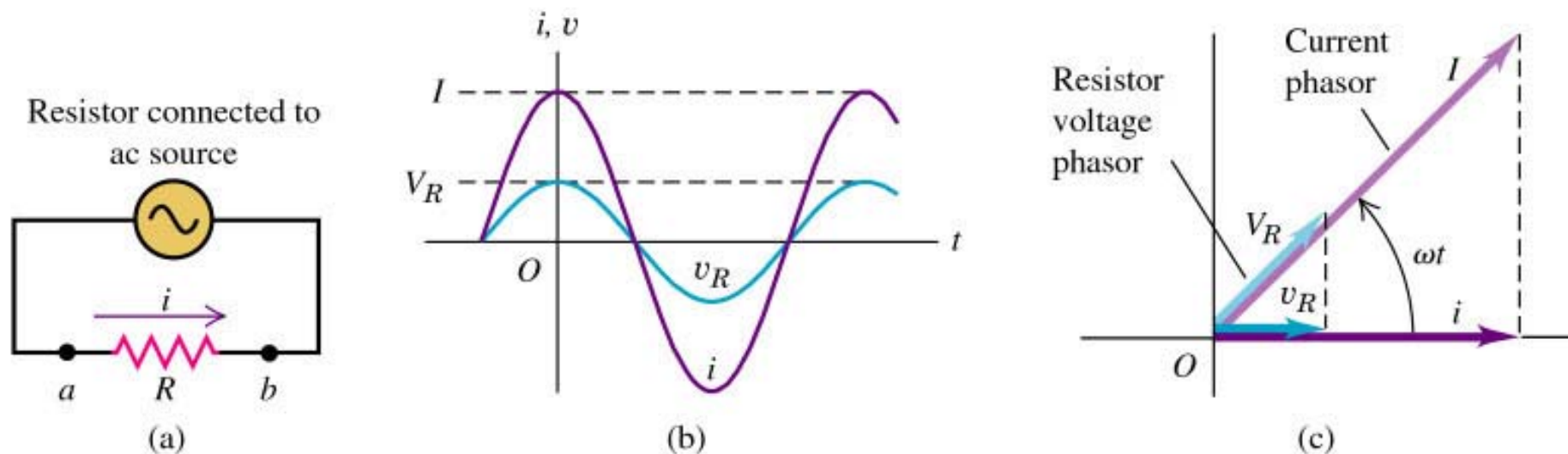Alternating Currents: Resistor in AC circuit




A resistor connected to an AC source will have the voltage, v_R , and the current across the resistor has the same phase. We can draw the current phasor and the voltage phasor with the same angle.

$$v_R = V_R \cos(\omega t) = iR = I \cos(\omega t)R$$

and $V_R = IR$ (just like DC case)


Phasors are rotating 2 dimensional vectors

Resistor in AC circuit; I & V versus ωt

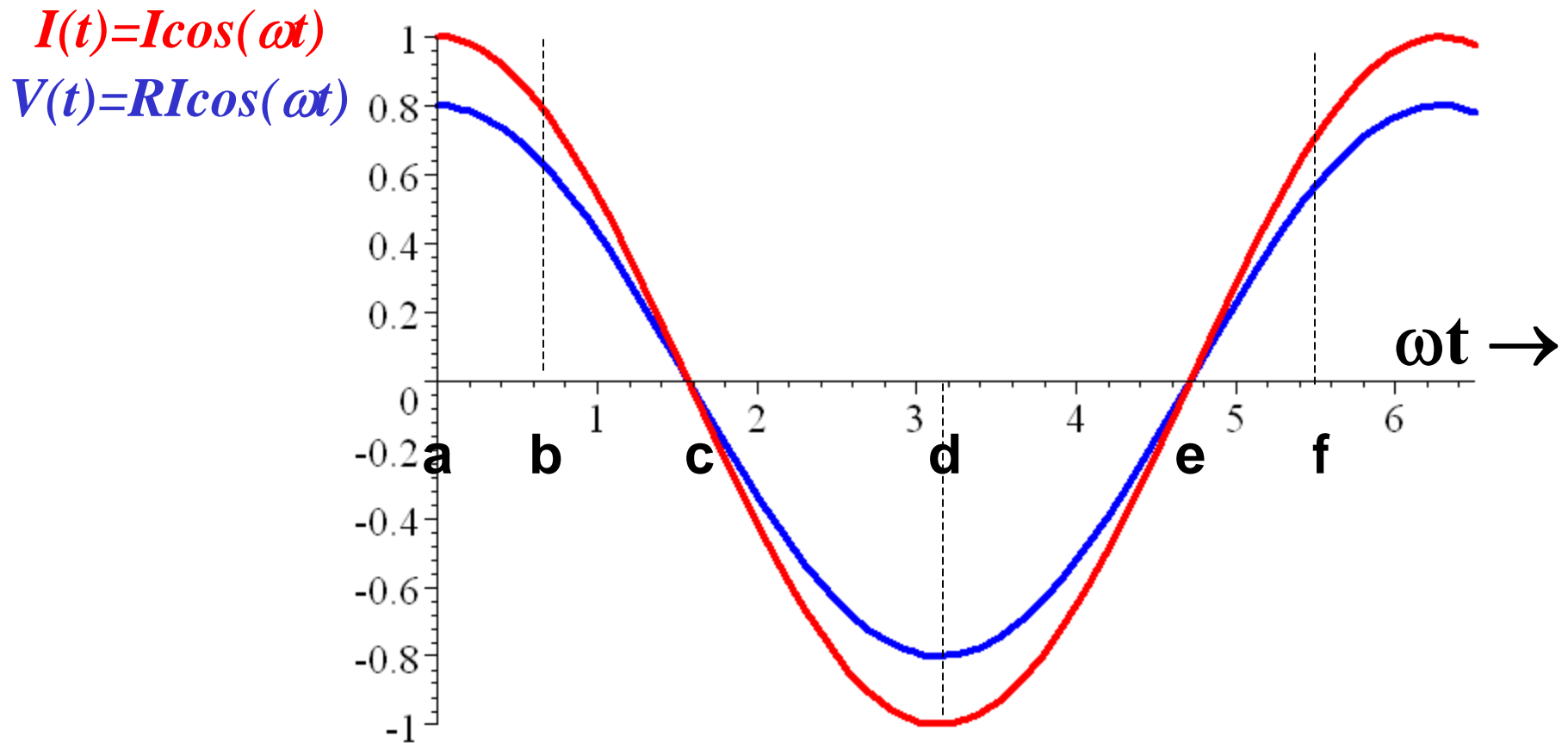

Note: Voltage is in phase with current

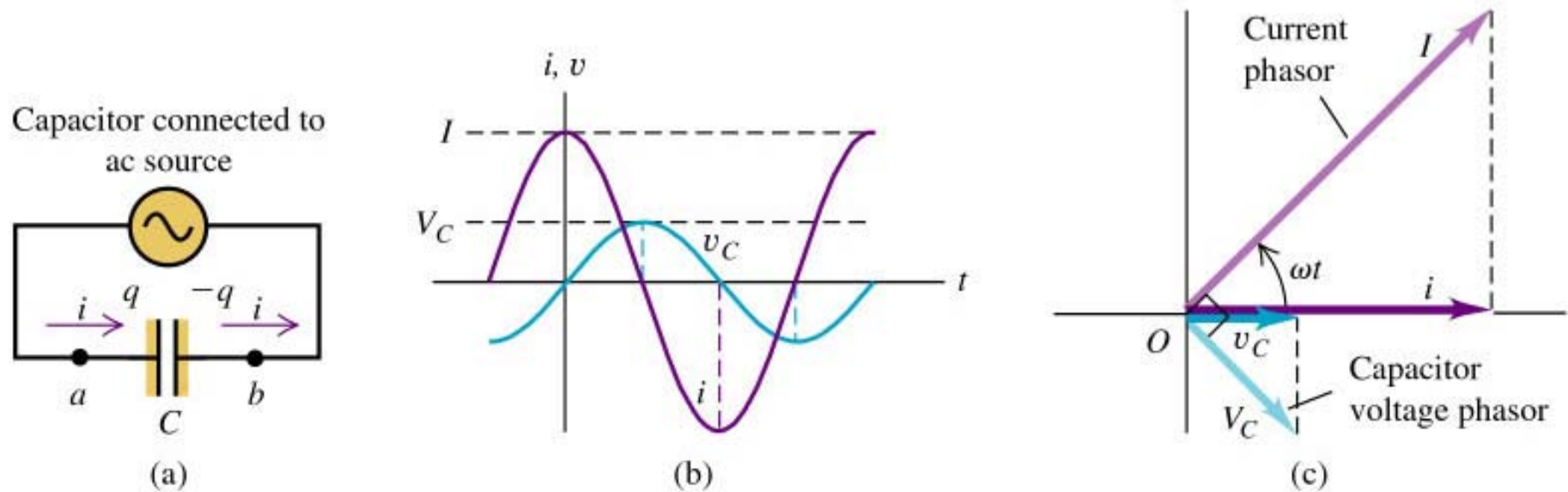Alternating Currents: Capacitor in AC circuit



A capacitor connected to an AC current source will have the voltage lagging behind the current by 90 degrees. We can draw the current phasor and the voltage phasor behind the current by 90 degrees.

$$i = \frac{dq}{dt} = I \cos(\omega t)$$

Find voltage:
$$v = \frac{q}{C} = \frac{1}{C} \int i dt = \frac{I}{\omega C} \sin(\omega t)$$

$$q = \frac{I}{\omega} \sin(\omega t)$$

$$V_{MAX} = I \left(\frac{1}{\omega C} \right)$$

Alternating Currents ; Capacitor in AC circuit

We define the capacitive reactance, X_C , as $X_C = \frac{1}{\omega C}$

$$V_{cap}^{MAX} = \frac{I}{\omega C} = I \left(\frac{1}{\omega C} \right) = I X_C$$

Like: $V_R = IR$


We stated that voltage lags by 90 deg., so equivalent solution is

$$\begin{aligned} v &= \frac{I}{\omega C} \cos(\omega t - 90) = \frac{I}{\omega C} [\cos \omega t \cos 90 + \sin \omega t \sin 90] \\ &= \frac{I}{\omega C} \sin \omega t \end{aligned}$$

Capacitor in AC circuit; I & V versus ωt

$$i(t) = I \cos(\omega t)$$


$$v(t) = (I/\omega C) \sin(\omega t)$$

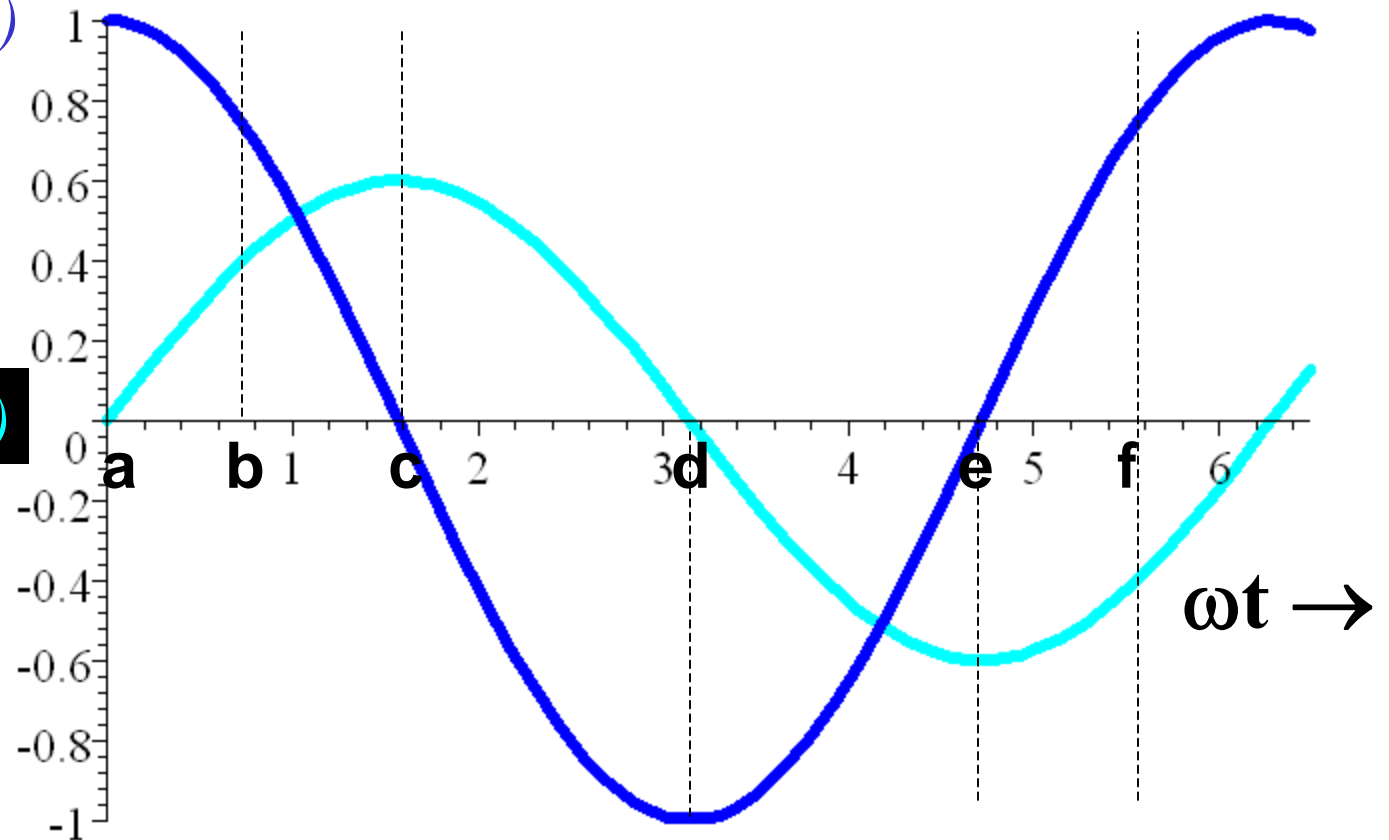

Note voltage lags 90 deg. Behind current

$$V(t) = (I/\omega C) \sin(\omega t) = (I/\omega C) \cos(\omega t - \pi/2)$$

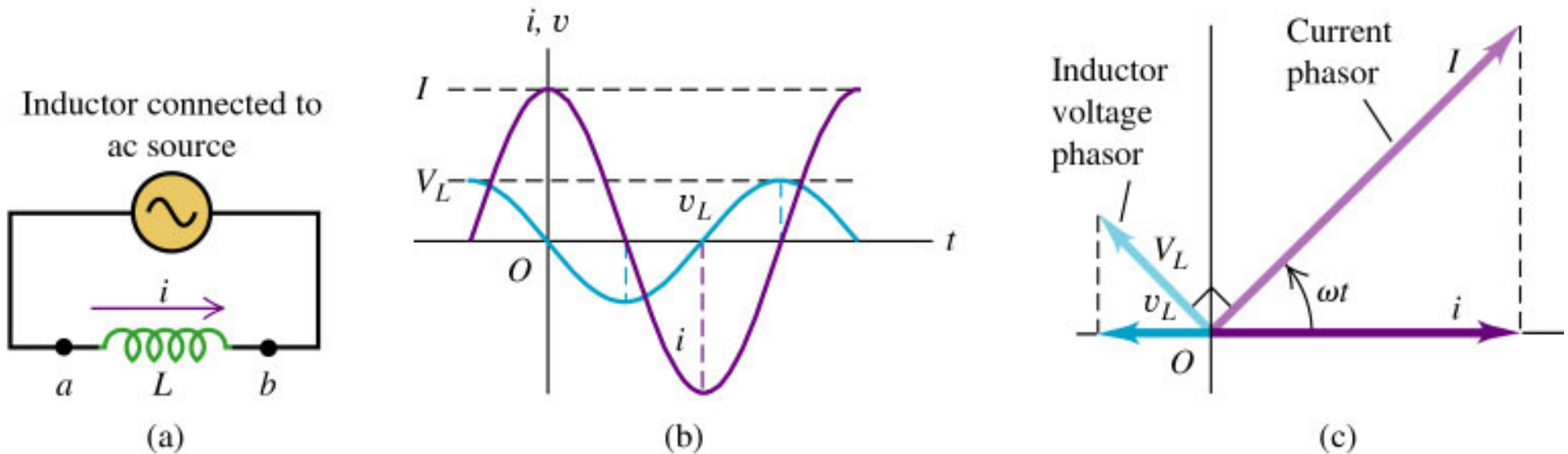Alternating Currents: Inductor in AC circuit



An inductor connected to an AC current source will have the voltage leading (ahead of) the current by 90 degrees. We can draw the current phasor and the voltage phasor ahead the current by 90 degrees.

$$i = I \cos(\omega t) \quad \text{and} \quad V = L \frac{di}{dt} = -IL\omega \sin(\omega t)$$

$$V_{MAX} = IL\omega$$

Define inductive reactance, X_L , as $X_L = \omega L$


$$V_{ind}^{MAX} = I\omega L = I(\omega L) = I X_L$$

Like: $V_R = IR$

Inductor in AC circuit; I & V versus ωt

$$i(t) = I \cos(\omega t)$$

$$v(t) = -IL\omega \sin(\omega t)$$

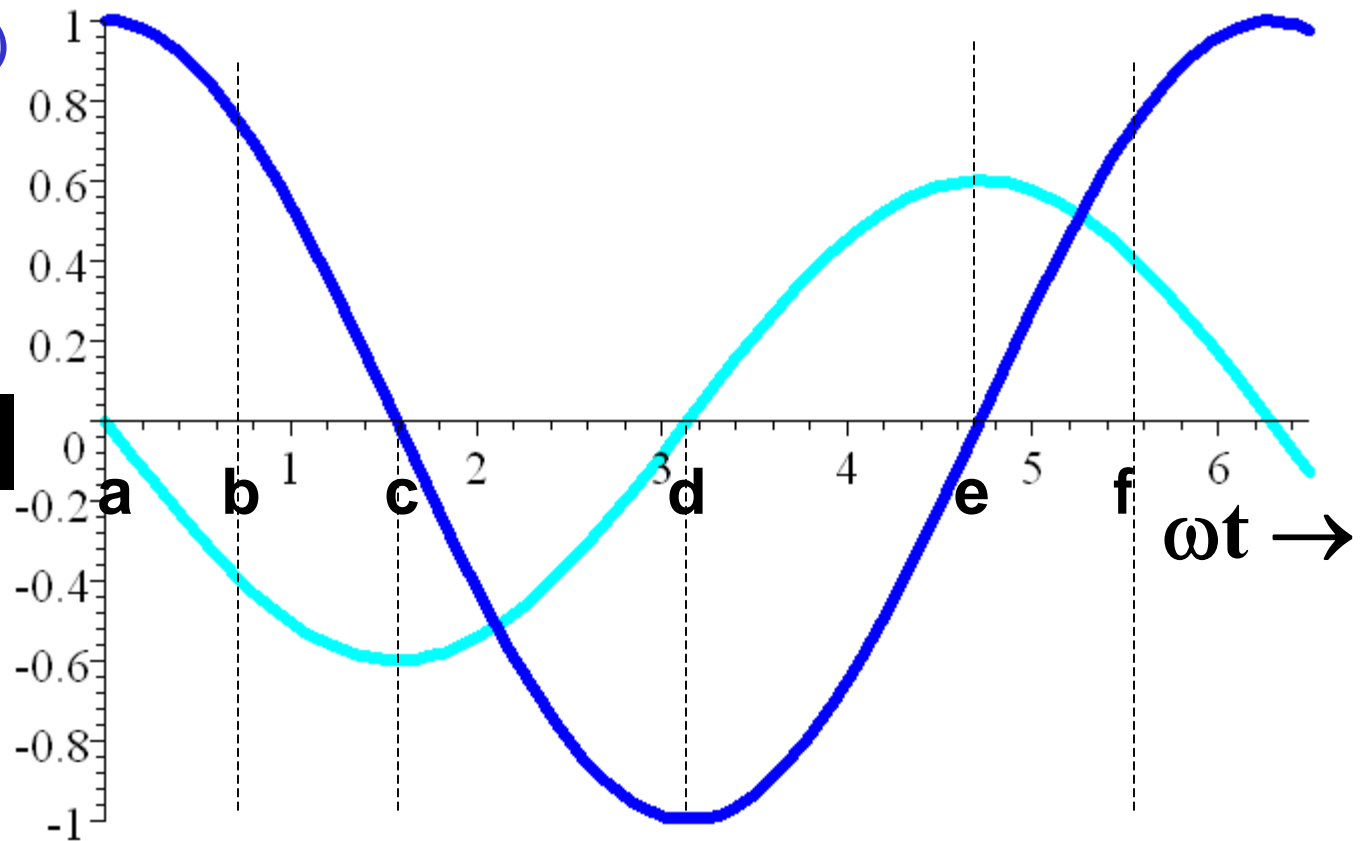

Draw phasor diagram for each point
Note voltage leads 90 deg. ahead current

$$v(t) = IL\omega \sin(\omega t) = IL\omega \cos(\omega t + \pi/2)$$

What is *reactance*?

You can think of it as a frequency-dependent resistance.

$$X_C = \frac{1}{\omega C}$$

For high ω , $X_C \sim 0$

- Capacitor looks like a wire ("short")

For low ω , $X_C \rightarrow \infty$

- Capacitor looks like a break

$$X_L = \omega L$$

For low ω , $X_L \sim 0$

- Inductor looks like a wire ("short")

For high ω , $X_L \rightarrow \infty$


- Inductor looks like a break

(inductors resist change in current)

$$("X_R" = R)$$

Frequency Filtering with inductor circuit

Inductor connected to
ac source

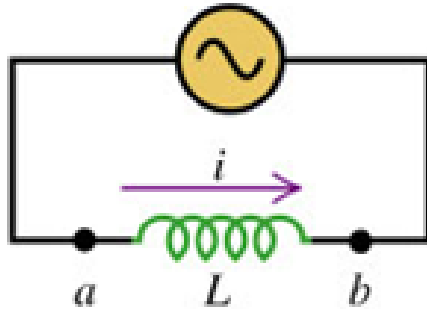


The voltage across the inductor is,

$$V_{ab} = L \frac{di}{dt} = -IL\omega \sin(\omega t)$$

and the magnitude depends on ω . So **LOW** frequencies are reduced or **FILTERED** out.

Frequency Filtering with capacitor circuit

Capacitor connected to
ac source

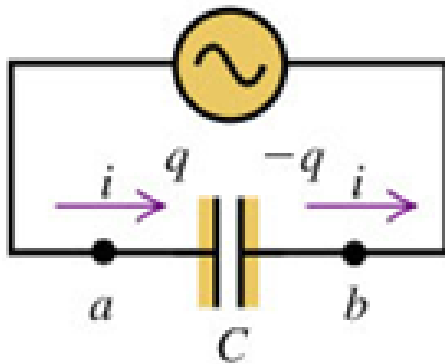


The voltage across the capacitor is,

$$V_{ab} = \frac{I}{\omega C} \sin(\omega t)$$

and the magnitude depends on $(1/\omega)$. So **HIGH** frequencies are reduced or **FILTERED** out.

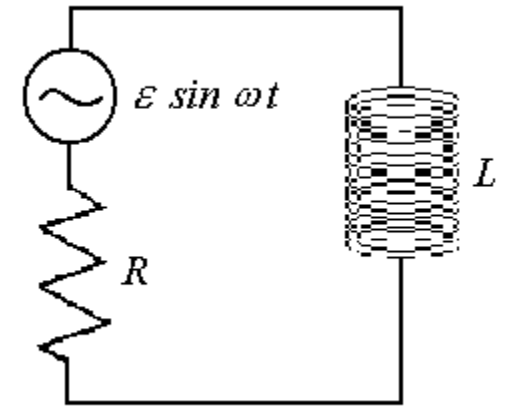
Question 1

An RL circuit is driven by an AC generator as shown in the figure.




For what driving frequency ω of the generator, will the current through the resistor be largest

- a) ω large b) ω small c) ω doesn't matter

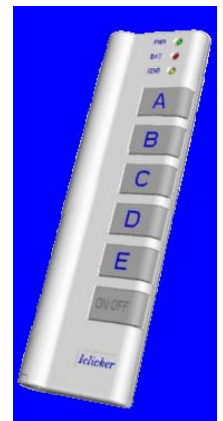

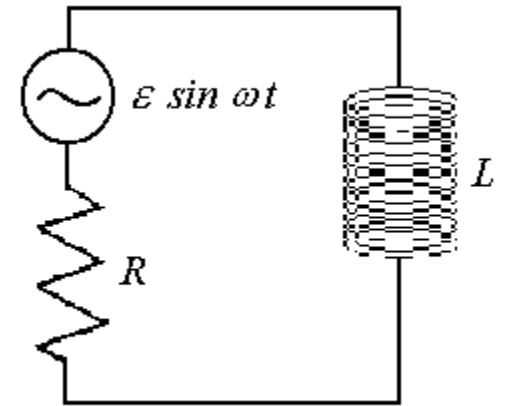Question 1

An RL circuit is driven by an AC generator as shown in the figure.



For what driving frequency ω of the generator, will the current through the resistor be largest

- a) ω large b) ω small c) ω doesn't matter

The current amplitude is inversely proportional to the frequency of the generator.

Alternating Currents: LRC circuit

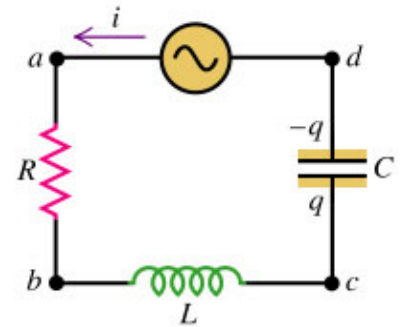
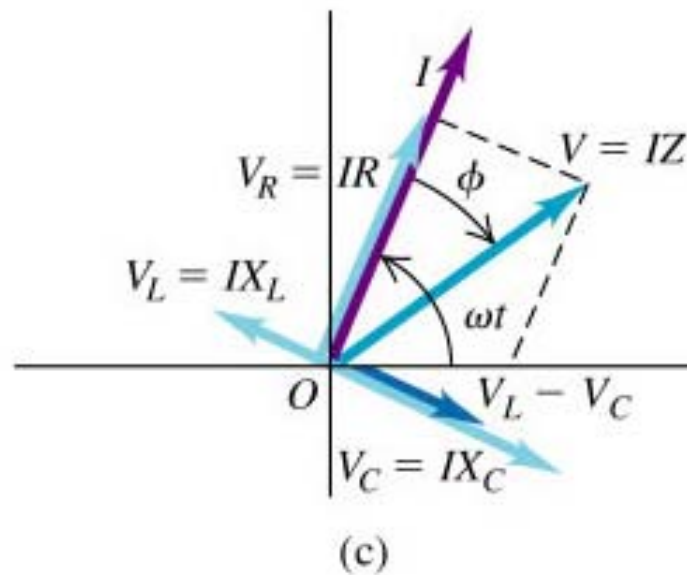
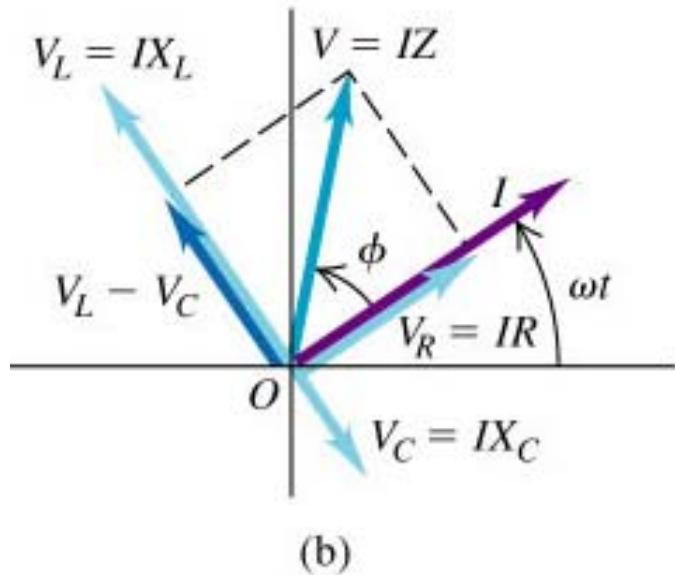


Figure (b) has $X_L > X_C$ and (c) has $X_L < X_C$.


Using Phasors, we can construct the phasor diagram for an LRC Circuit. This is similar to 2-D vector addition. We add the phasors of the resistor, the inductor, and the capacitor. The inductor phasor is +90 and the capacitor phasor is -90 relative to the resistor phasor.

Adding the three phasors vectorially, yields the voltage sum of the resistor, inductor, and capacitor, **which must be the same as the voltage of the AC source.** Kirchhoff's voltage law holds for AC circuits.

Also V_R and I are in phase.

Phasors

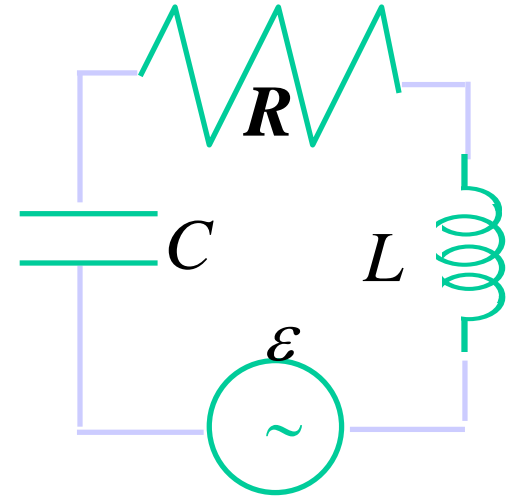Problem: Given $V_{\text{drive}} = \varepsilon_m \sin(\omega t)$,
find V_R , V_L , V_C , I_R , I_L , I_C




Strategy:


We will use Kirchhoff's voltage law that the (phasor) sum of the voltages V_R , V_C , and V_L must equal V_{drive} .

Phasors, cont.

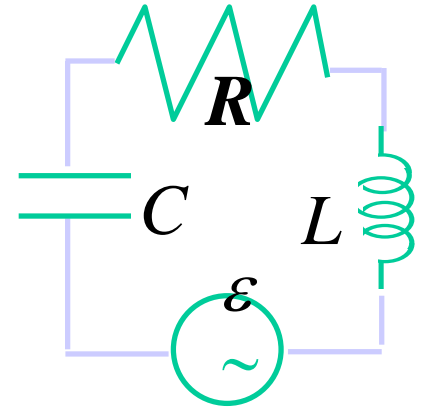Problem: Given $V_{\text{drive}} = \varepsilon_m \sin(\omega t)$,
find V_R , V_L , V_C , I_R , I_L , I_C




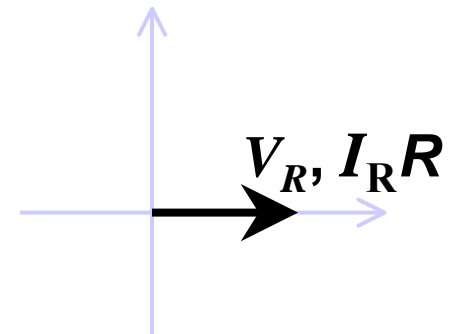1. Draw V_R phasor along x -axis (this direction is chosen for convenience). Note that since $V_R = I_R R$, this is also the direction of the current phasor i_R . Because of Kirchhoff's current law, $I_L = I_C = I_R \equiv I$ (i.e., the same current flows through each element).




Phasors, cont.

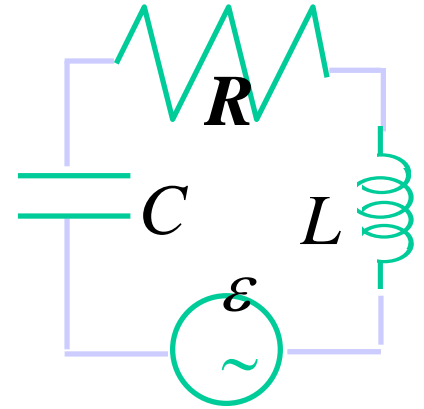Problem: Given $V_{\text{drive}} = \varepsilon_m \sin(\omega t)$,
find V_R , V_L , V_C , I_R , I_L , I_C




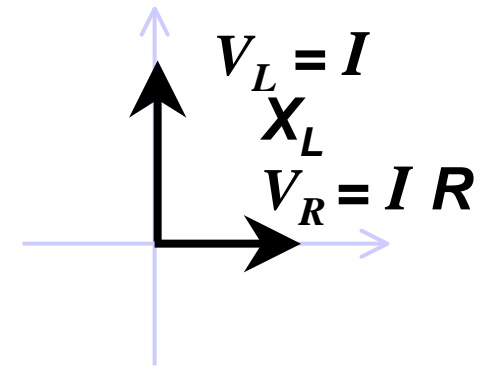2. Next draw the phasor for V_L . Since the inductor current I_L always lags $V_L \rightarrow$ draw V_L 90° further *counterclockwise*. The length of the V_L phasor is $I_L X_L = I \omega L$




Phasors, cont.

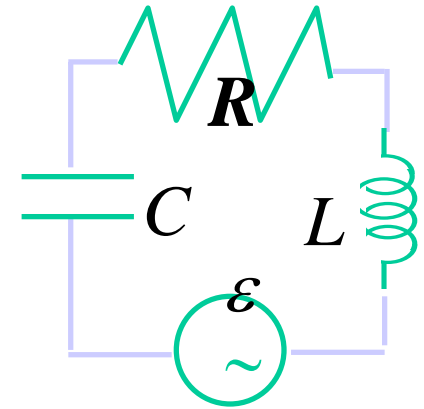Problem: Given $V_{\text{drive}} = \varepsilon_m \sin(\omega t)$,
find V_R , V_L , V_C , I_R , I_L , I_C



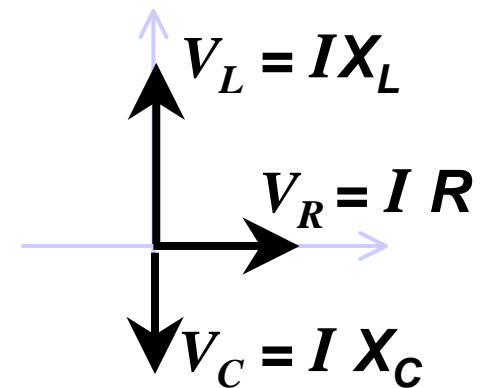
3. The capacitor voltage V_C always lags $I_C \rightarrow$ draw V_C 90° further **clockwise**.
The length of the V_C phasor is $I_C X_C = I / \omega C$




The lengths of the phasors depend on R , L , C , and ω .
The relative orientation of the V_R , V_L , and V_C phasors is always the way we have drawn it. **Memorize it!**

Phasors, cont.

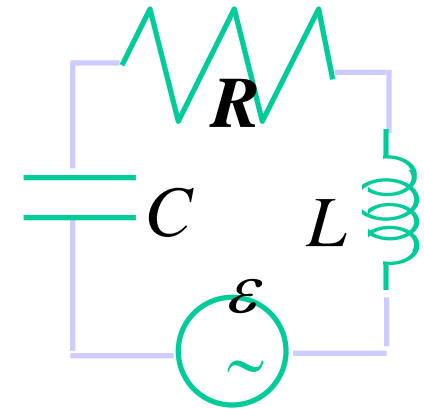Problem: Given $V_{\text{drive}} = \varepsilon_m \sin(\omega t)$,
find V_R , V_L , V_C , I_R , I_L , I_C







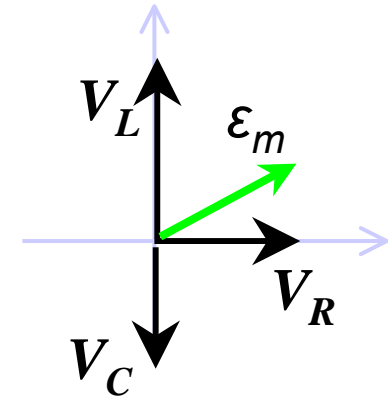
- The phasors for V_R , V_L , and V_C are added like vectors to give the drive voltage $V_R + V_L + V_C = \varepsilon_m$:



- From this diagram we can now easily calculate quantities of interest, like the net current I , the maximum voltage across any of the elements, and the *phase* between the current the drive voltage (and thus the power).





Question 2

A series RC circuit is driven by emf ϵ . Which of the following could be an appropriate phasor diagram?

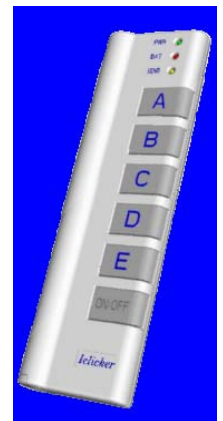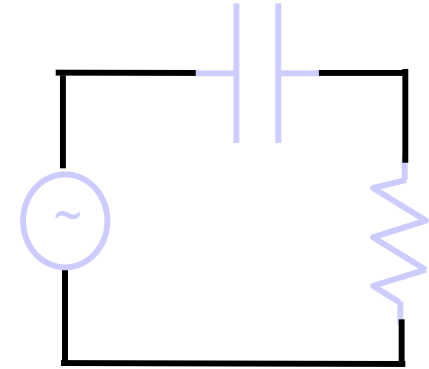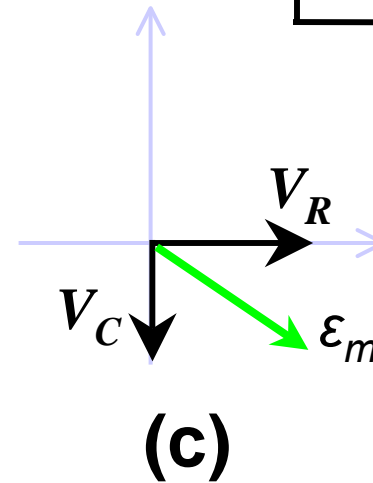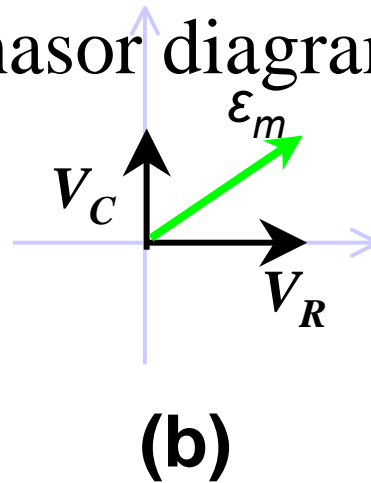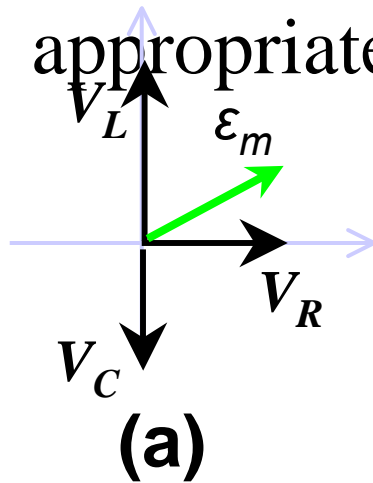

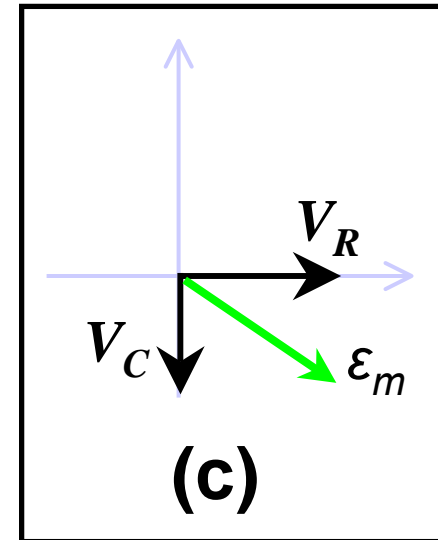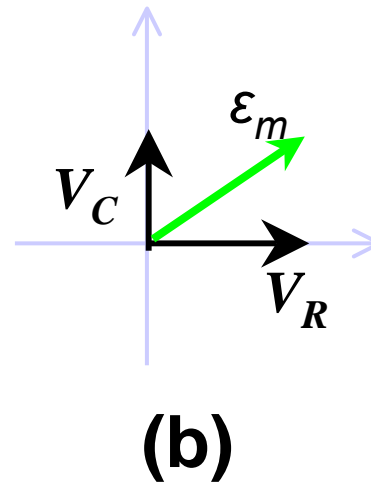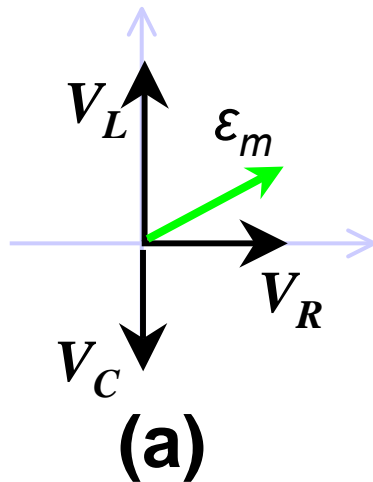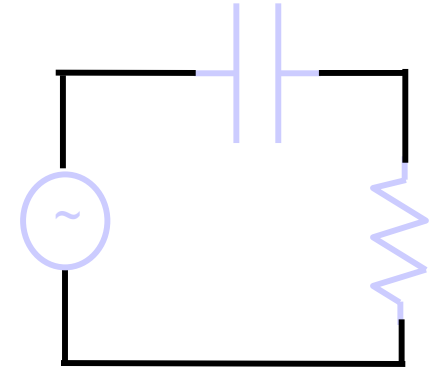Question 2


A series RC circuit is driven by emf ϵ . Which of the following could be an appropriate phasor diagram?



- The phasor diagram for the driven series RLC circuit always has the voltage across the capacitor lagging the current by 90° . The vector sum of the V_C and V_R phasors must equal the generator emf phasor ϵ_m .

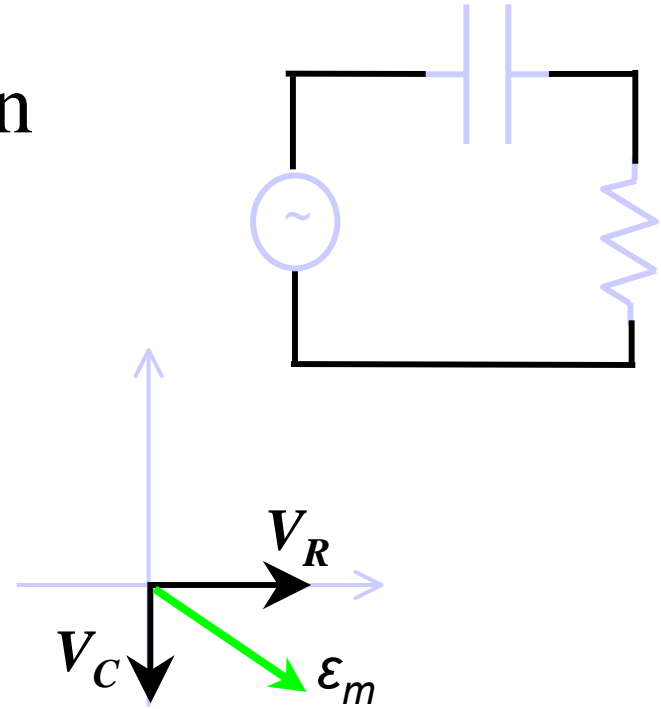
Question 3

A series RC circuit is driven by emf \mathcal{E} .




For this circuit which of the following is true?

- (a) The drive voltage is in phase with the current.
- (b) The drive voltage lags the current.
- (c) The drive voltage leads the current.

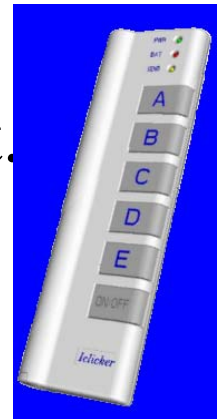

Question 3

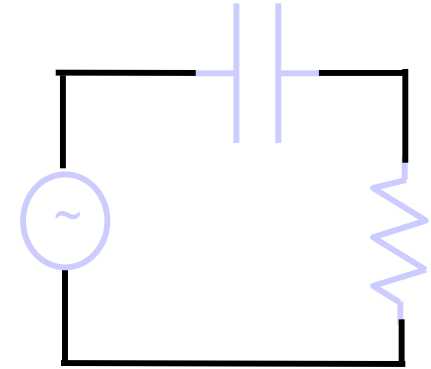


For this circuit which of the following is true?

(a) The drive voltage is in phase with the current.

(b) The drive voltage lags the current.

(c) The drive voltage leads the current.

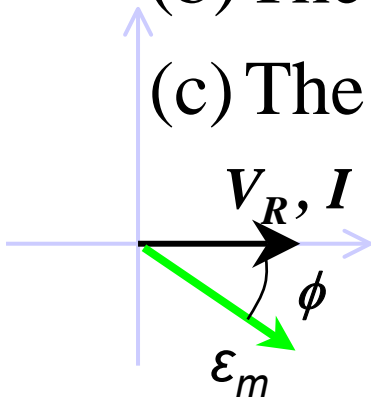

First, remember that the current phasor I is always in the same orientation as the resistor voltage phasor V_R (since the current and voltage are always in phase). From the diagram, we see that the drive phasor ϵ_m is *lagging* (clockwise) I . Just as V_C lags I by 90° , in an AC driven RC circuit, the drive voltage will also lag I by some angle less than 90° . The precise phase lag ϕ depends on the values of R , C and ω .

Voltage $V(t)$ across AC source

$$\begin{aligned}v(t) &= \sqrt{(V_R)^2 + (V_L - V_C)^2} \cos(\omega t + \phi) \\&= \sqrt{(IR)^2 + (IX_L - IX_C)^2} \cos(\omega t + \phi) \\&= I \sqrt{(R)^2 + (X_L - X_C)^2} \cos(\omega t + \phi) = IZ \cos(\omega t + \phi)\end{aligned}$$

$$Z = \sqrt{(R)^2 + (X_L - X_C)^2} \quad Z \text{ is called "impedance"}$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{\omega L - 1/\omega C}{R}$$

Also:


$$V = V^{MAX} = I Z \quad \text{Like: } V_R = IR$$

$$V_{rms} = I_{rms} Z$$

$$i = I \cos \omega t$$


$$v = V \cos(\omega t + \phi)$$
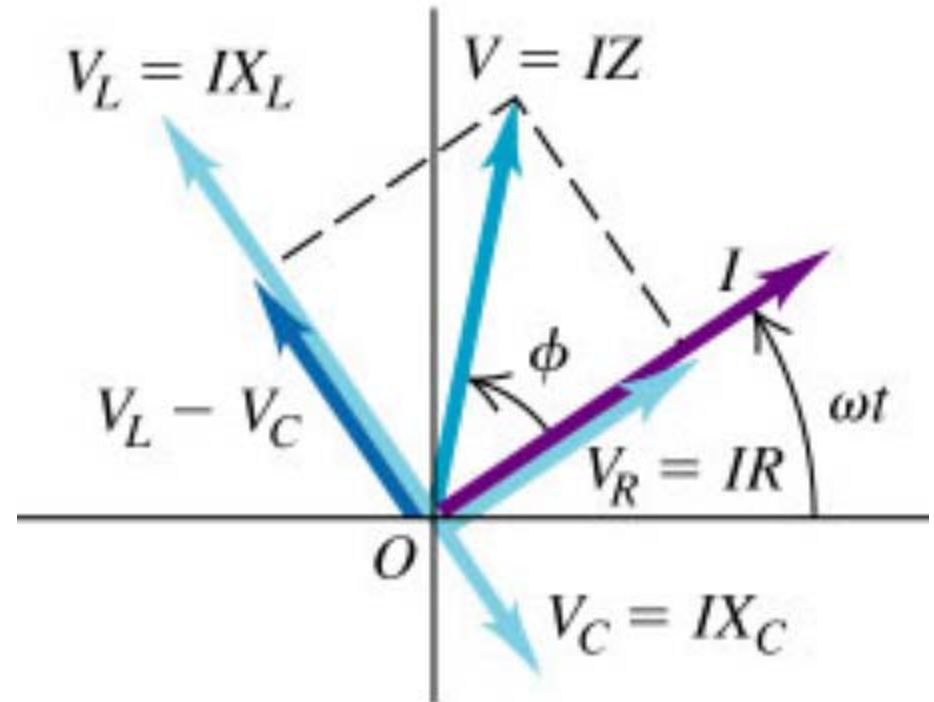
$$\begin{aligned}V_R &= IR \\V_L &= IX_L \\V_C &= IX_C\end{aligned}$$




Alternating Currents: LRC circuit, Fig. 31.11

Y&F Example 31.4

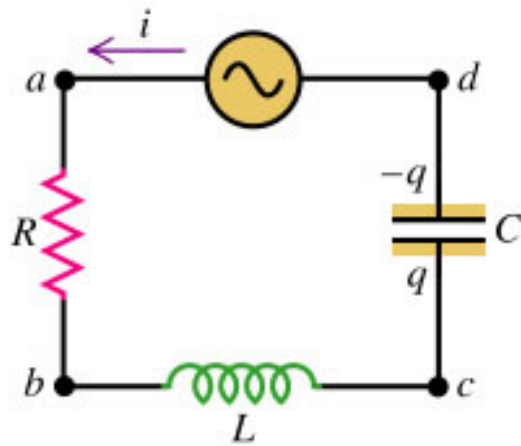

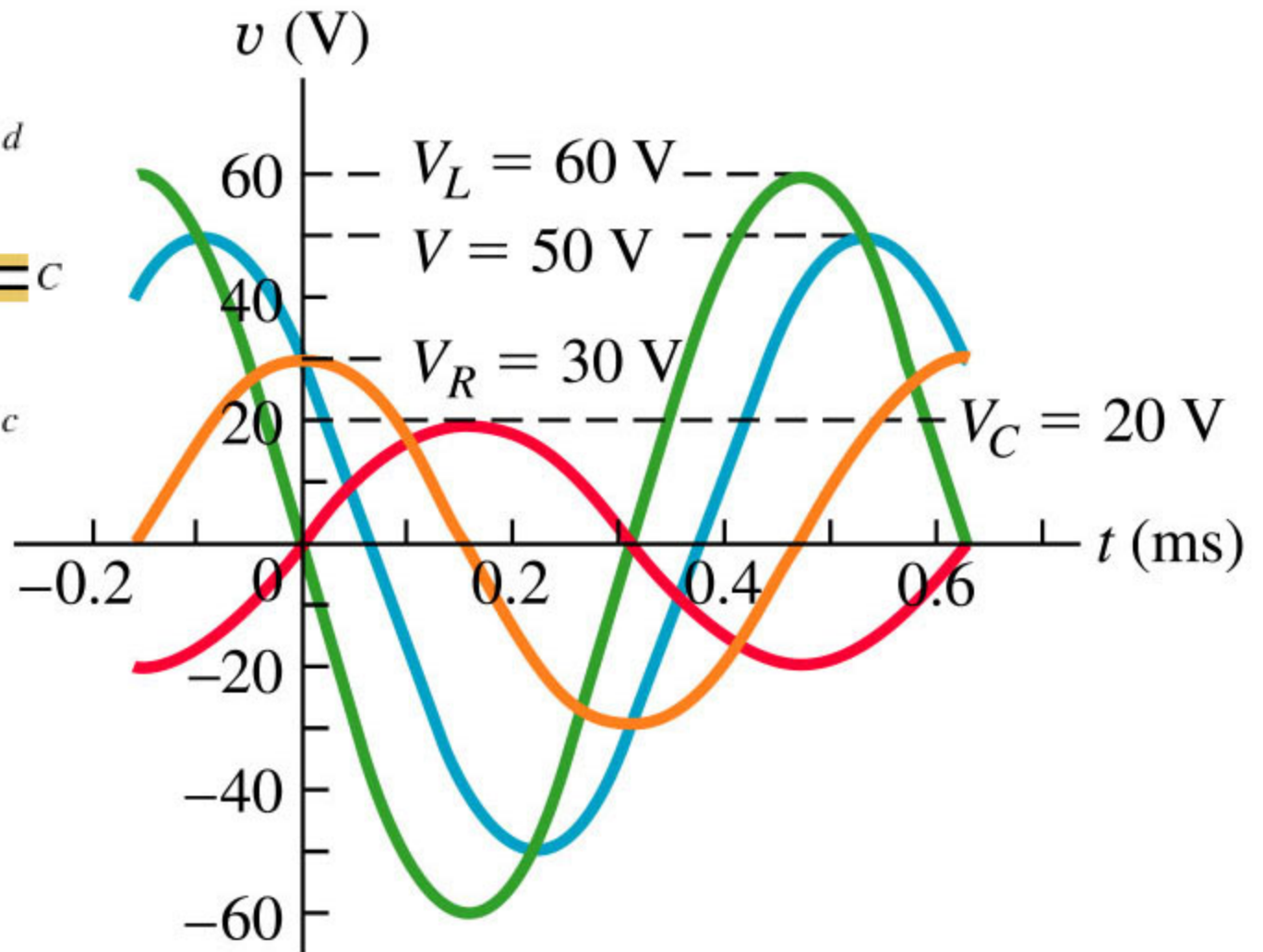$V=50\text{v}$
 $\omega=10000\text{rad/s}$
 $R=300\text{ohm}$
 $L=60\text{mH}$
 $C=0.5\mu\text{C}$



KEY: v — v_R — v_L — v_C —

LRC series circuit; Summary of instantaneous Current and voltages

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$i(t) = I \cos(\omega t)$$


$$v_R(t) = IR \cos(\omega t)$$

$$v_C(t) = IX_C \cos(\omega t - 90) = I \frac{1}{\omega C} \cos(\omega t - 90)$$

$$v_L(t) = IX_L \cos(\omega t + 90) = I\omega L \cos(\omega t + 90)$$

$$v_{ad}(t) = I \sqrt{(X_R)^2 + (X_L - X_C)^2} \cos(\omega t + \phi)$$
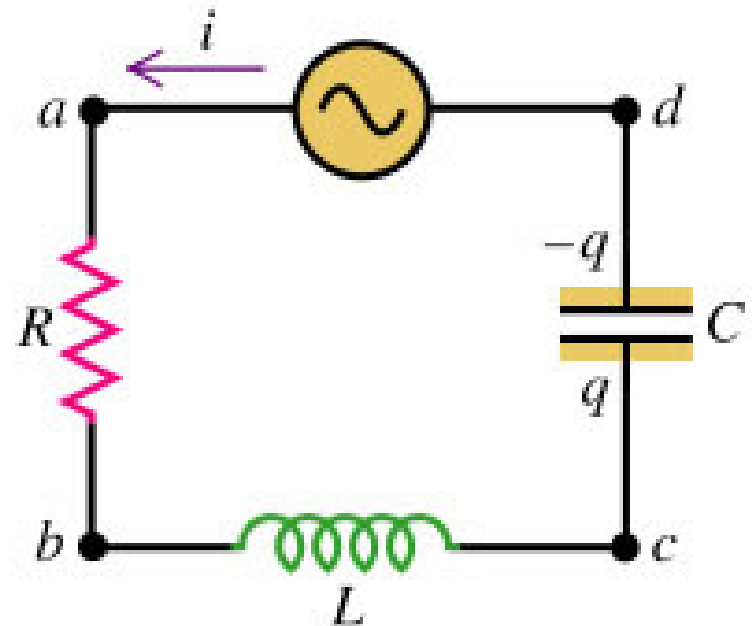
$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{\omega L - 1/\omega C}{R}$$



For next time

- Homework #10 [due now]
- Homework #11 posted this afternoon, due next Wed.
- Quiz on Friday: Faraday's Law, Inductance and Inductors, RLC circuits

