



Course Updates

<http://www.phys.hawaii.edu/~varner/PHYS272-Spr10/physics272.html>

Reminders:

- 1) Assignment #11 → posted, due next Wednesday
- 2) Quiz # 5 **today** (Chap 29, 30)
- 3) Complete AC Circuits

Last time: LRC Circuits with phasors...

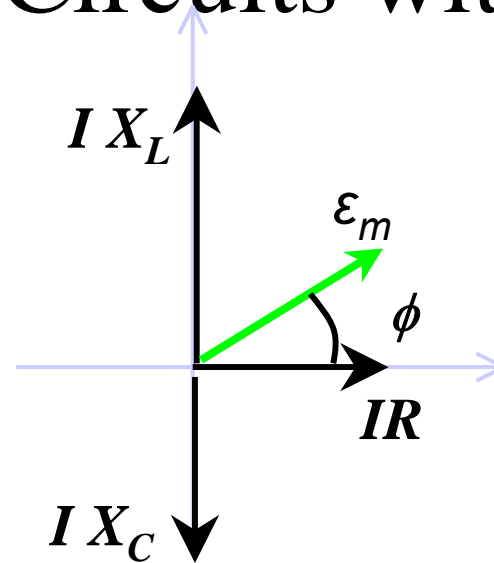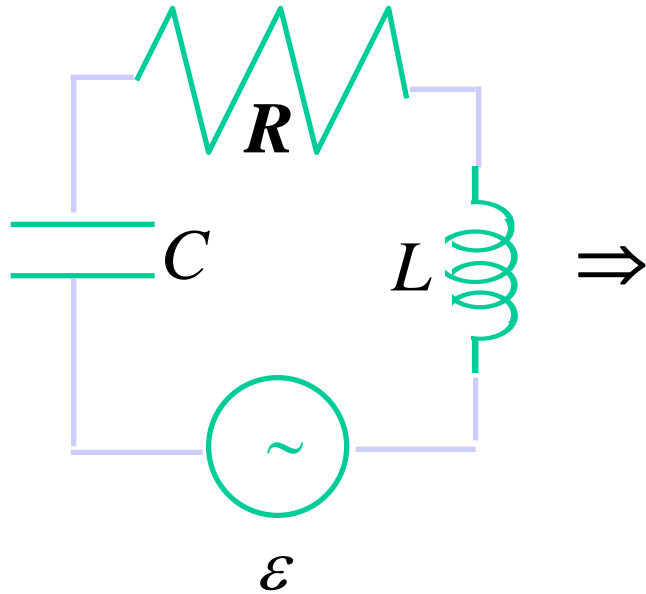


where ...

$$X_L \equiv \omega L$$

$$X_C \equiv \frac{1}{\omega C}$$

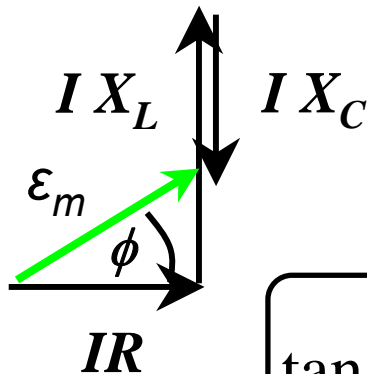The phasor diagram gives us graphical solutions for ϕ and I :



$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\varepsilon_m^2 = I^2 \left(R^2 + (X_L - X_C)^2 \right)$$

\Downarrow

$$\varepsilon_m = I \sqrt{R^2 + (X_L - X_C)^2} = IZ$$

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

LRC series circuit; Summary of instantaneous Current and voltages

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$i(t) = I \cos(\omega t)$$

$$v_R(t) = IR \cos(\omega t)$$


$$v_C(t) = IX_C \cos(\omega t - 90) = I \frac{1}{\omega C} \cos(\omega t - 90)$$

$$v_L(t) = IX_L \cos(\omega t + 90) = I\omega L \cos(\omega t + 90)$$

$$\varepsilon(t) = v_{ad}(t) = IZ \cos(\omega t + \phi) = \varepsilon_m \cos(\omega t + \phi)$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{\omega L - 1/\omega C}{R}$$

$$Z = \sqrt{(X_R)^2 + (X_L - X_C)^2}$$

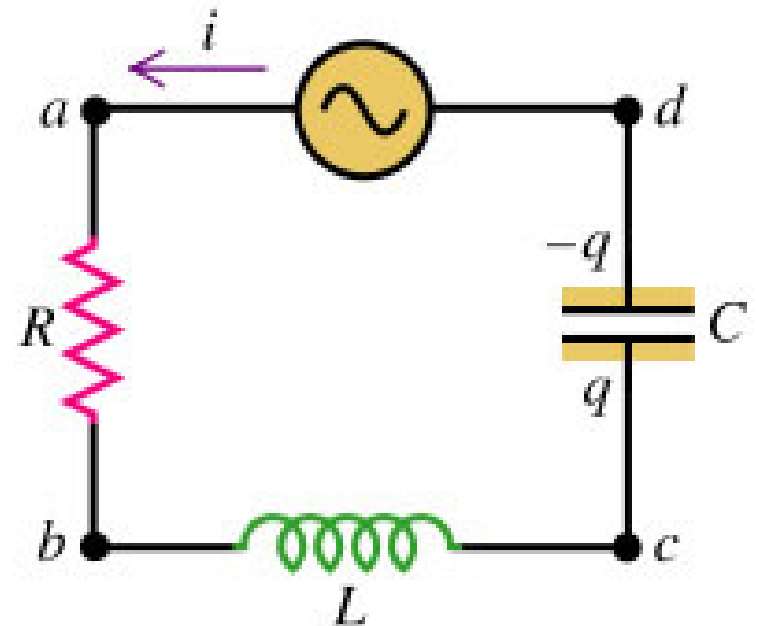


Lagging & Leading

The phase ϕ between the current and the driving emf depends on the relative magnitudes of the inductive and capacitive reactances.

$$I = \frac{\varepsilon_m}{Z}$$


$$\tan \phi = \frac{X_L - X_C}{R}$$
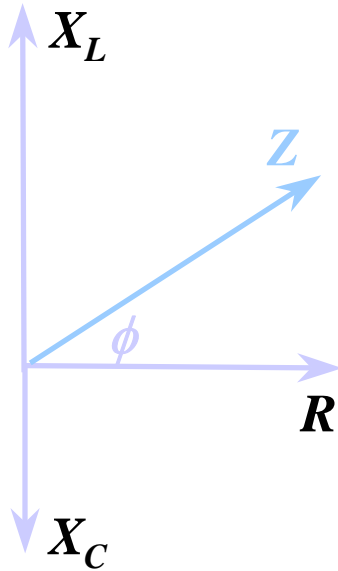
$$X_L \equiv \omega L$$
$$X_C \equiv \frac{1}{\omega C}$$




$$X_L > X_C$$
$$\phi > 0$$

**current
LAGS
applied voltage**

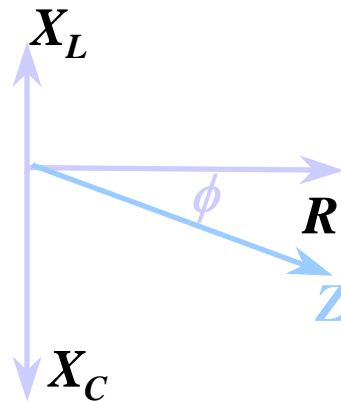

$$X_L < X_C$$
$$\phi < 0$$

**current
LEADS
applied voltage**

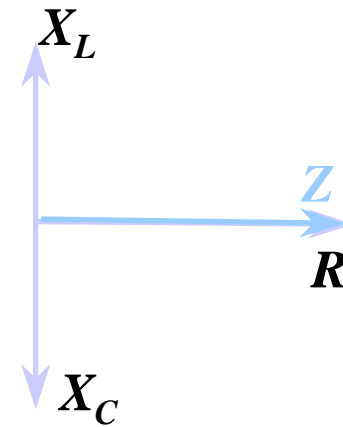

$$X_L = X_C$$
$$\phi = 0$$


**current
IN PHASE WITH
applied voltage**

Impedance, Z

- From the phasor diagram we found that the current amplitude I was related to the drive voltage amplitude ε_m by

$$\varepsilon_m = I Z$$

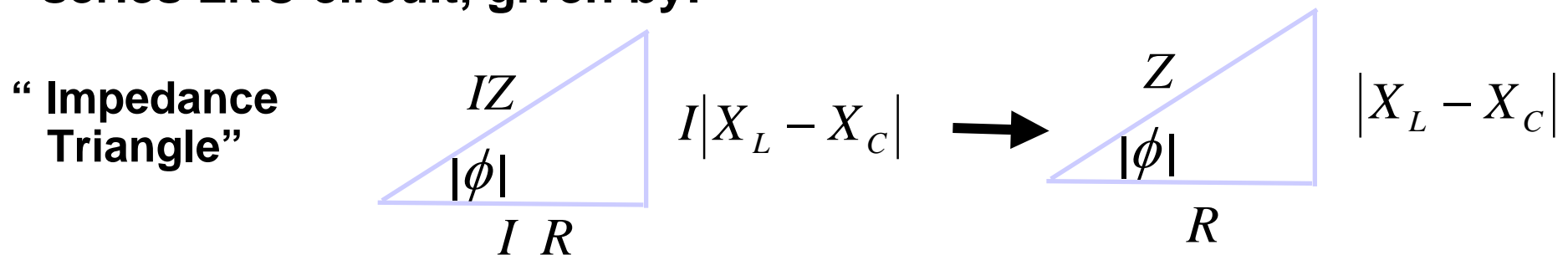- Z is known as the “impedance”, and is basically the frequency dependent equivalent resistance of the series LRC circuit, given by:



$$Z \equiv \frac{\varepsilon_m}{I} = \sqrt{R^2 + (X_L - X_C)^2}$$

or

$$Z = \frac{R}{\cos(\phi)}$$

- Note that Z achieves its minimum value (R) when $\phi = 0$. Under this condition the maximum current flows in the circuit.

Resonance

- For fixed R , C , L the current I will be a maximum at the resonant frequency ω which makes the impedance Z purely resistive ($Z = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$ i.e., $Z = R$)

reaches a maximum when:

$$X_L = X_C$$

This condition is obtained when:


$$\omega L = \frac{1}{\omega C} \quad \Rightarrow \quad \omega = \frac{1}{\sqrt{LC}}$$

- Note that this resonant frequency is identical to the natural frequency of the LC circuit by itself!
- At this frequency, the current and the driving voltage are in phase:

$$\tan \phi = \frac{X_L - X_C}{R} = 0$$

Resonance

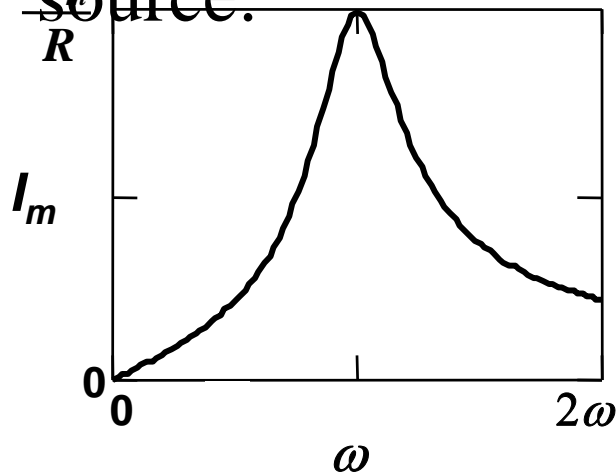Plot the current versus ω , the frequency of the voltage source:



- For ω very large, $X_L \gg X_C$, $\phi \rightarrow 90^\circ$, $I_m \rightarrow 0$
- For ω very small, $X_C \gg X_L$, $\phi \rightarrow -90^\circ$, $I_m \rightarrow 0$

Example: vary R


V=100 v

$\omega=1000$ rad/s

R=200, 500, 2000 ohm


L=2 H

C=0.5 μ C

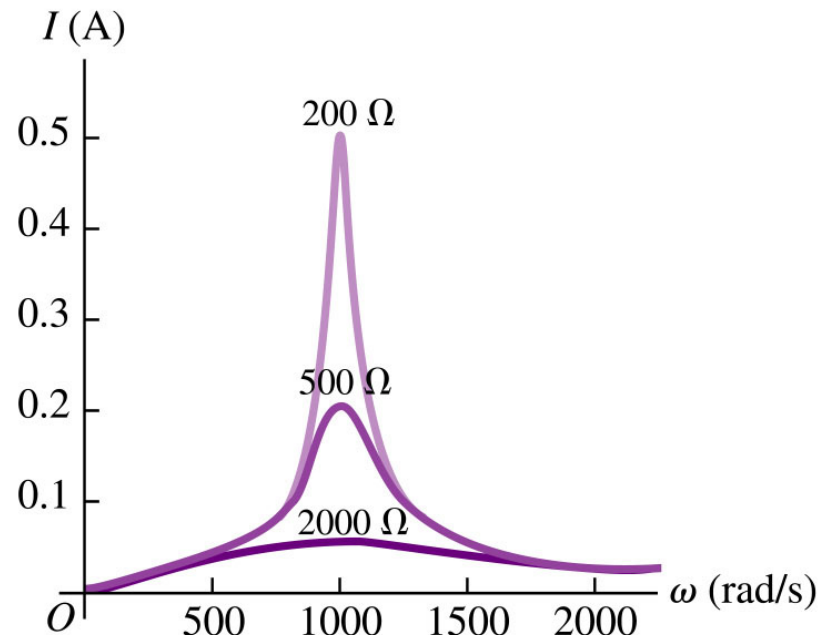

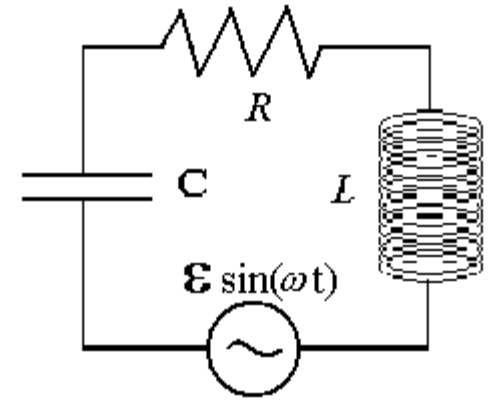
Question 1

Consider a general AC circuit containing a resistor, capacitor, and inductor, driven by an AC generator.




As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit _____.

- a) always increases
- b) only increases for lowering the frequency below resonance
- c) only increases for raising the frequency above resonance

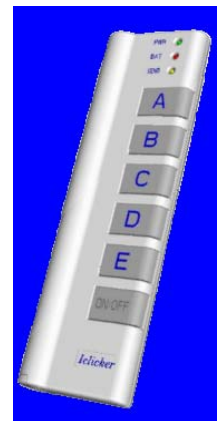

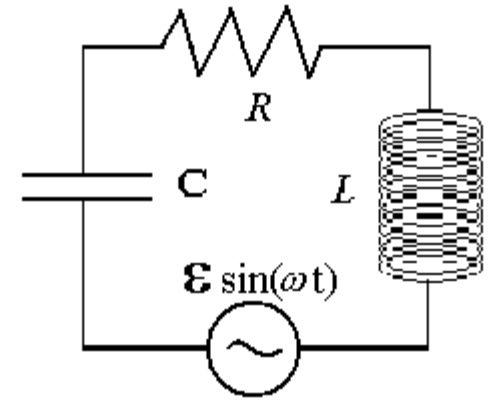Question 1

Consider a general AC circuit containing a resistor, capacitor, and inductor, driven by an AC generator.



As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit _____.


a) always increases

b) only increases for lowering the frequency below resonance

c) only increases for raising the frequency above resonance

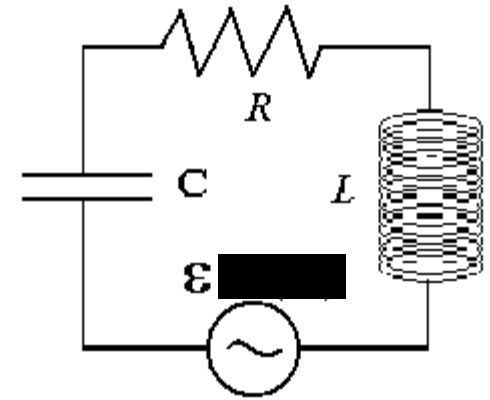
Question 2

Consider a general AC circuit containing a resistor, capacitor, and inductor, driven by an AC generator.




At the resonant frequency, which of the following is true?

- a) The current leads the voltage across the generator.
- b) The current lags the voltage across the generator.
- c) The current is in phase with the voltage across the generator.

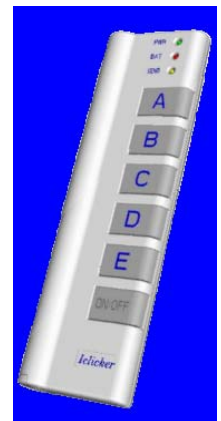

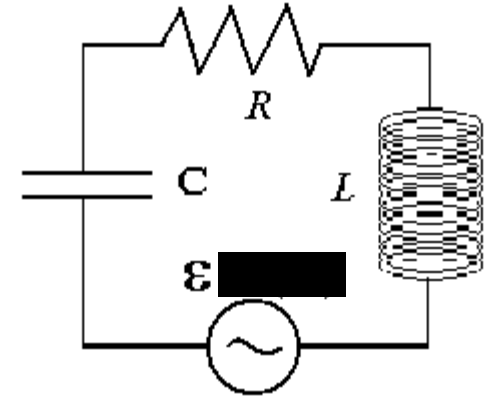
Question 2

Consider a general AC circuit containing a resistor, capacitor, and inductor, driven by an AC generator.



At the resonant frequency, which of the following is true?

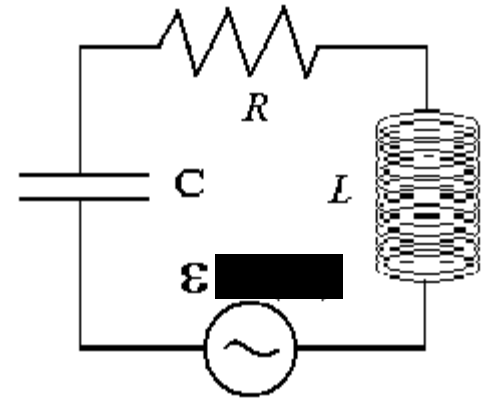- a) The current leads the voltage across the generator.
- b) The current lags the voltage across the generator.
- c) The current is in phase with the voltage across the generator.





- Impedance = $Z = \sqrt{R^2 + (X_L - X_C)^2}$
- At resonance, $(X_L - X_C) = 0$, and the impedance has its minimum value: $Z = R$
- As frequency is changed from resonance, either up or down, $(X_L - X_C)$ no longer is zero and Z must therefore increase.

Changing the frequency away from the resonant frequency will change both the inductive and capacitive reactance such that $X_L - X_C$ is no longer 0. This, when squared, gives a positive term to the impedance, increasing its value. By definition, at the resonance frequency, I_{\max} is at its greatest and the phase angle is 0, so the current is in phase with the voltage across the generator.


Question 3

Fill in the blank. This circuit is being driven _____ its resonance frequency.

- a) above
- b) below
- c) exactly at

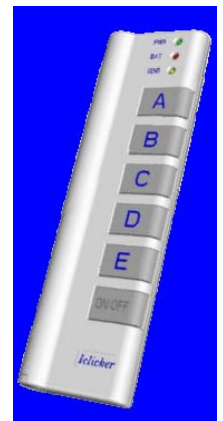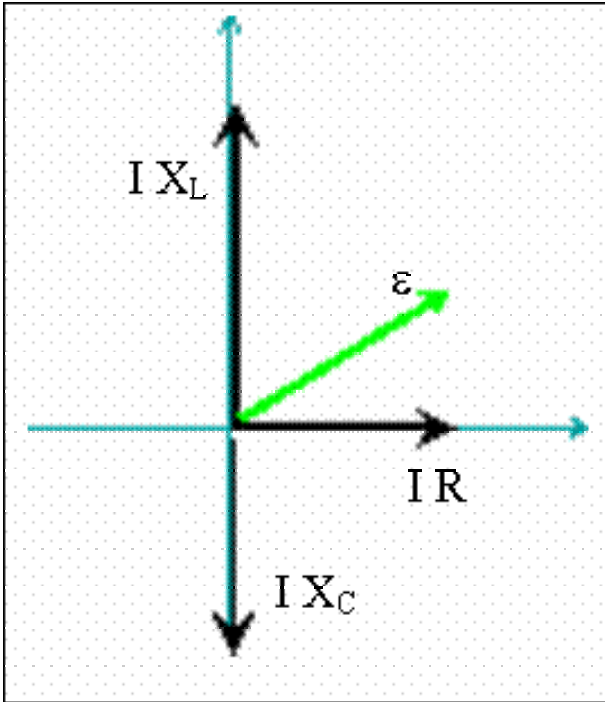

Question 3

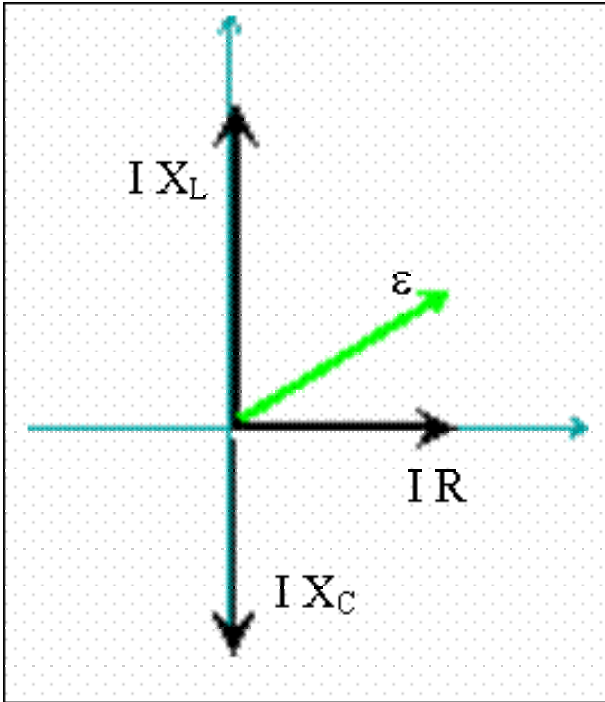


Fill in the blank. This circuit is being driven _____ its resonance frequency.

a) above

b) below


c) exactly at

Question 4

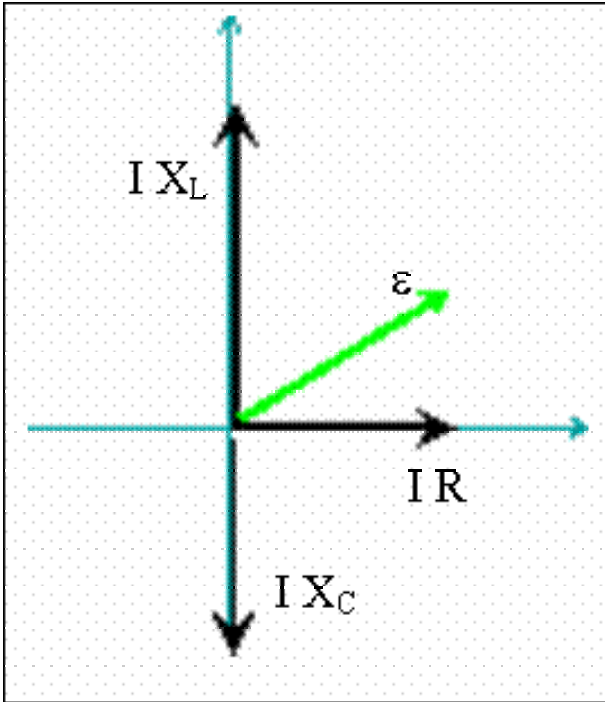


The generator voltage _____ the current.

- a) leads
- b) lags
- c) is in phase with

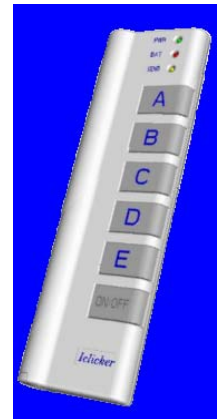

Question 4

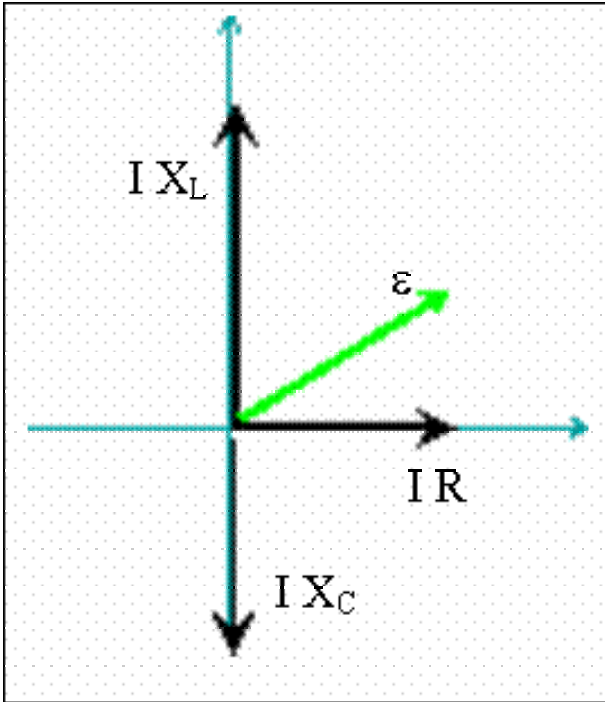


The generator voltage _____ the current.

a) leads

b) lags


c) is in phase with

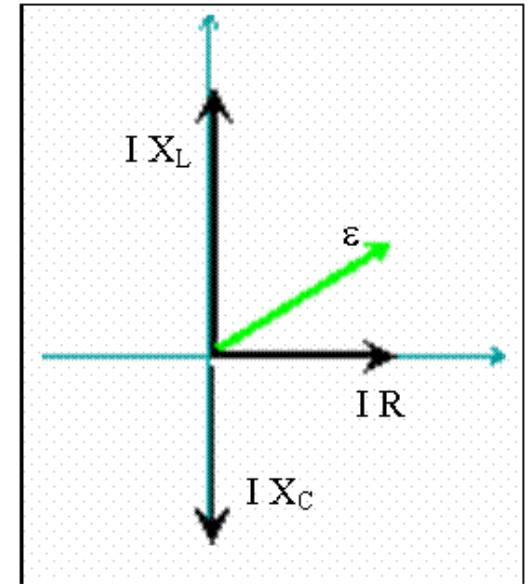

- At resonance, $X_L = X_C$.
- Here, $X_L > X_C$
- Therefore, need to reduce $X_L = \omega L$ and increase $X_C = 1/(\omega C)$
- Therefore, lower ω !!
- From diagram, ε leads IR (rotation = ccw)

Power in LRC circuit
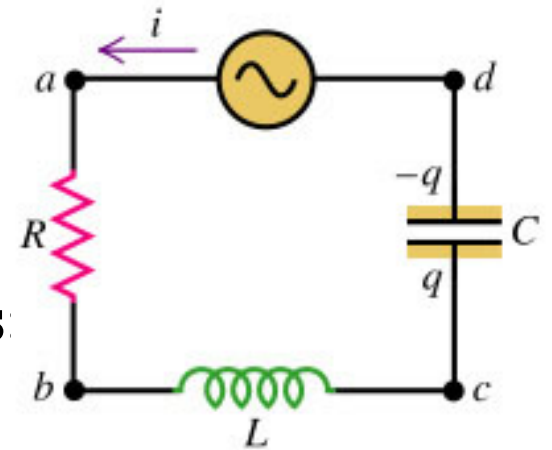
$$i(t) = I(t)\cos(\omega t); \quad v_{ad}(t) = V \cos(\omega t + \phi)$$



The instantaneous power delivered to L-R-C is

$$P(t) = i(t)v_{ad}(t) = V \cos(\omega t + \phi)I \cos(\omega t)$$

We can use trig identities to expand the above to,

$$P(t) = V[\cos(\omega t)\cos(\phi) - \sin(\omega t)\sin(\phi)]I \cos(\omega t)$$

$$= VI \cos^2(\omega t)\cos(\phi) - VI \sin(\omega t)\cos(\omega t)\sin(\phi)$$

$$P_{ave} = \langle P(t) \rangle = VI \langle \cos^2(\omega t) \rangle \cos(\phi) - VI \langle \sin(\omega t)\cos(\omega t) \rangle \sin(\phi)$$

$$= VI \langle \cos^2(\omega t) \rangle \cos(\phi) = VI \left(\frac{1}{2} \right) \cos(\phi)$$

$$P_{ave} = \langle P(t) \rangle = \frac{1}{2} VI \cos(\phi) = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos(\phi)$$

$$= V_{RMS} I_{RMS} \cos(\phi)$$

Power in LRC circuit, continued

$$P_{ave} = \langle P(t) \rangle = \frac{1}{2} VI \cos(\phi) = V_{RMS} I_{RMS} \cos(\phi)$$

General result. V_{RMS} is voltage across element, I_{RMS} is current through element, and ϕ is phase angle between them.

Example; 100Watt light bulb plugged into 120V house outlet, Pure resistive load (no L and no C), $\phi = 0$.

$$P = I_{rms} V_{rms} = \frac{V_{rms}^2}{R}$$


$$R = \frac{V_{rms}^2}{P_{ave}} = \frac{120^2}{100} = 144\Omega$$

$$I_{rms} = \frac{P_{ave}}{V_{rms}} = \frac{100}{120} = 0.83A$$

Note; 120V house voltage is rms and has peak voltage of $120\sqrt{2} = 170V$


Question: What is P_{AVE} for an inductor or capacitor?

Question 5

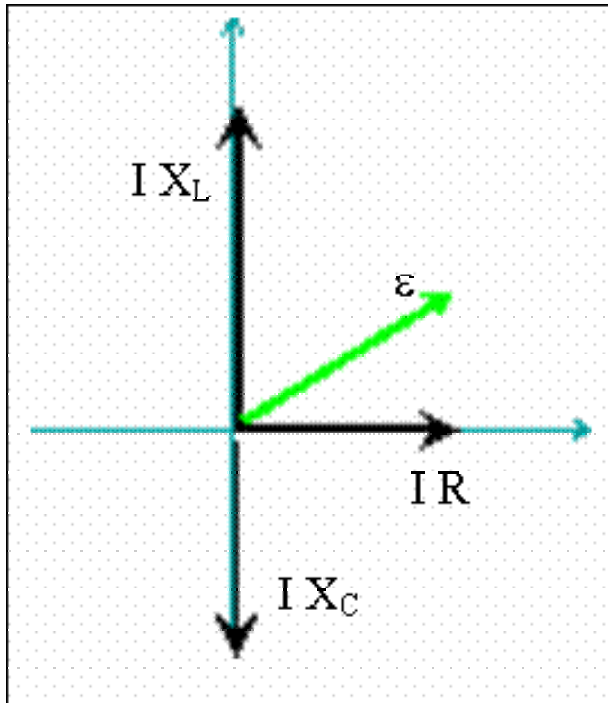


If you wanted to increase the power delivered to this *RLC* circuit, which modification(s) would work?

- a) increase R
- b) increase C
- c) increase C, L
- d) decrease R
- e) decrease C, L

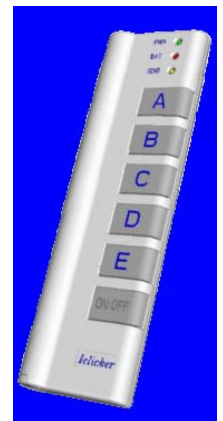

Question 5

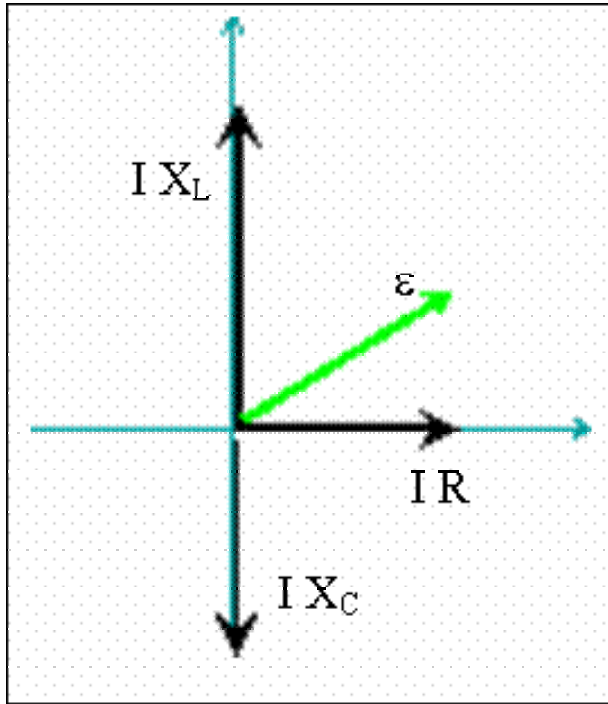

If you wanted to increase the power delivered to this *RLC* circuit, which modification(s) would work?

a) increase R


d) decrease R

b) increase C or L

e) decrease C, L

c) increase C, L


Question 6

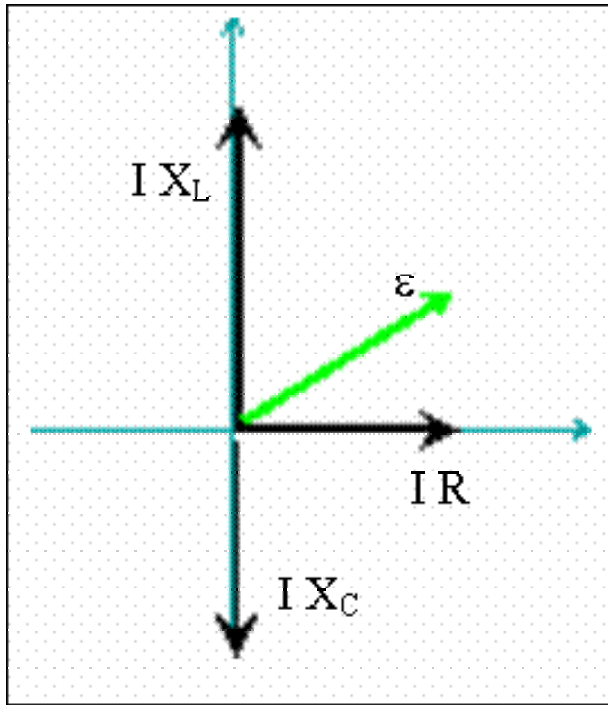


Would using a larger resistor increase the current?

a) yes

b) no

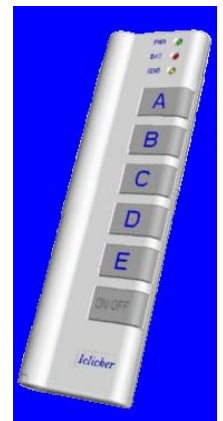

Question 6

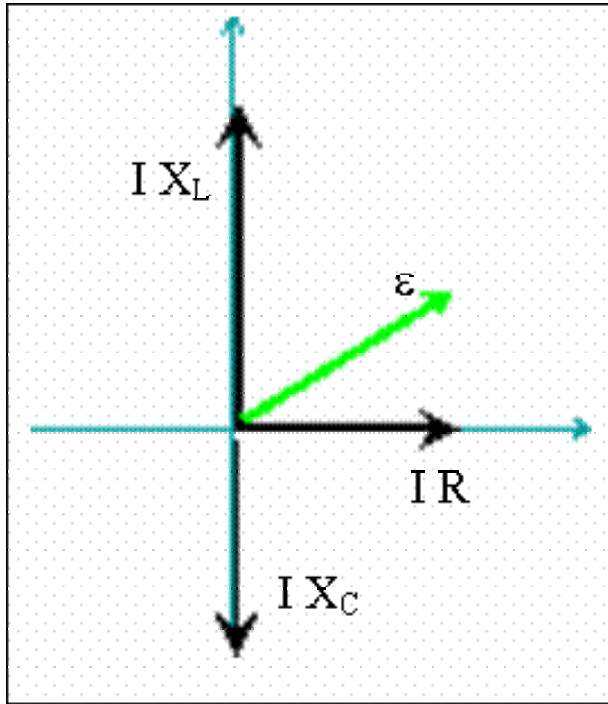


Would using a larger resistor increase the current?

a) yes

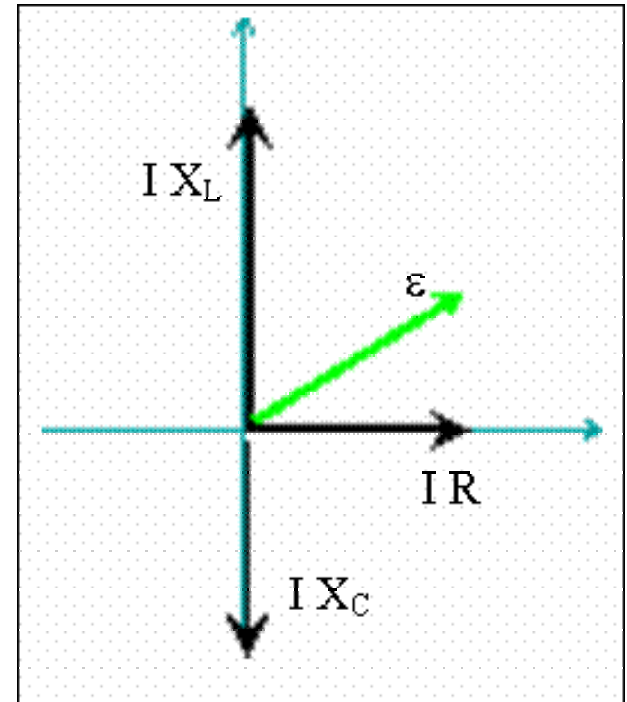b) no

- Power $\sim I \cos \phi \sim (1/Z)(R/Z) = (R/Z^2)$
- To increase power, want Z to decrease:
 - L : decrease $X_L \Rightarrow$ decrease L
 - C : increase $X_C \Rightarrow$ decrease C
 - R : decrease $Z \Rightarrow$ decrease R



Since power peaks at the resonant frequency, try to get X_L and X_C to be equal. Power also depends inversely on R , so decrease R to increase Power.

Summary

- Power

“power factor”

$$\begin{aligned}\langle P(t) \rangle &= \varepsilon_{rms} I_{rms} \cos \phi \\ &= (I_{rms})^2 R\end{aligned}$$

$$\varepsilon_{rms} \equiv \frac{1}{\sqrt{2}} \varepsilon_m$$

$$I_{rms} \equiv \frac{1}{\sqrt{2}} I_m$$

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

- Driven Series LRC Circuit:

$$\omega = \frac{1}{\sqrt{LC}}$$

- Resonance condition

- Resonant frequency

For next time

- Homework #11 posted, due next Wed.
- Quiz now: Faraday's Law, Inductance and Inductors, RLC circuits

