
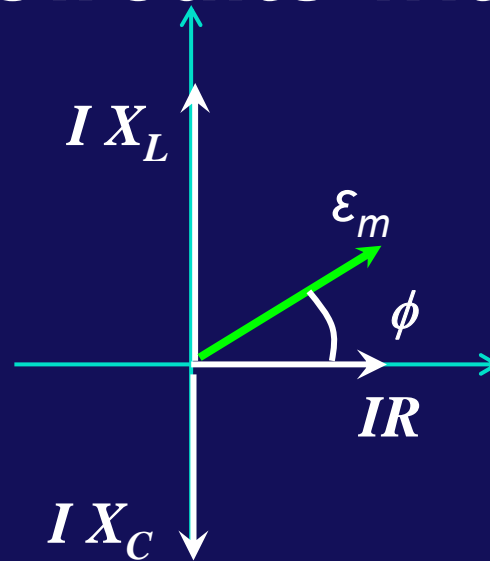

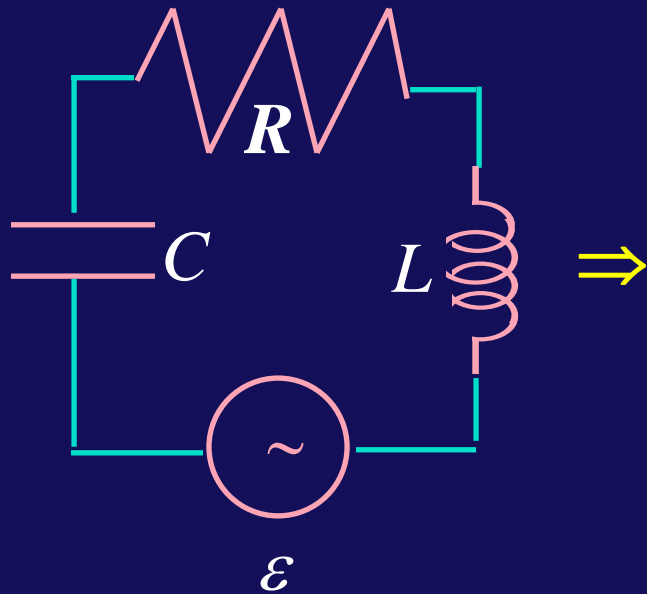
# Last time: LRC Circuits with phasors...




where ...

$$X_L \equiv \omega L$$

$$X_C \equiv \frac{1}{\omega C}$$

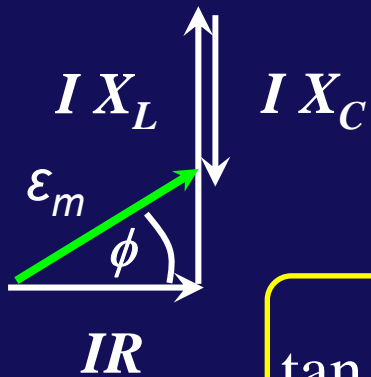The phasor diagram gives us graphical solutions for  $\phi$  and  $I$ :



$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\epsilon_m^2 = I^2 \left( R^2 + (X_L - X_C)^2 \right)$$



$$\epsilon_m = I \sqrt{R^2 + (X_L - X_C)^2} = IZ$$

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

# LRC series circuit; Summary of instantaneous Current and voltages

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$i(t) = I \cos(\omega t)$$

$$v_R(t) = IR \cos(\omega t)$$


$$v_C(t) = IX_C \cos(\omega t - 90) = I \frac{1}{\omega C} \cos(\omega t - 90)$$

$$v_L(t) = IX_L \cos(\omega t + 90) = I\omega L \cos(\omega t + 90)$$

$$\varepsilon(t) = v_{ad}(t) = IZ \cos(\omega t + \phi) = \varepsilon_m \cos(\omega t + \phi)$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{\omega L - 1/\omega C}{R}$$

$$Z = \sqrt{(X_R)^2 + (X_L - X_C)^2}$$

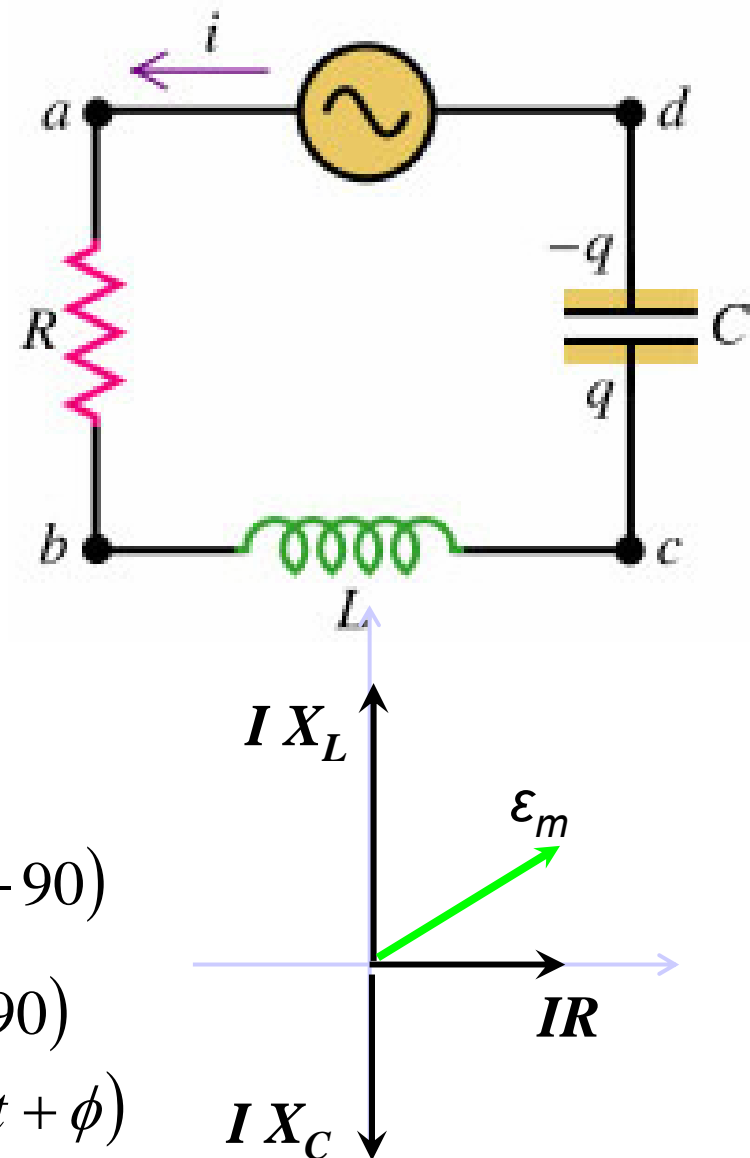


# Lagging & Leading

The phase  $\phi$  between the current and the driving emf depends on the relative magnitudes of the inductive and capacitive reactances.

$$I = \frac{\varepsilon_m}{Z}$$


$$\tan \phi = \frac{X_L - X_C}{R}$$
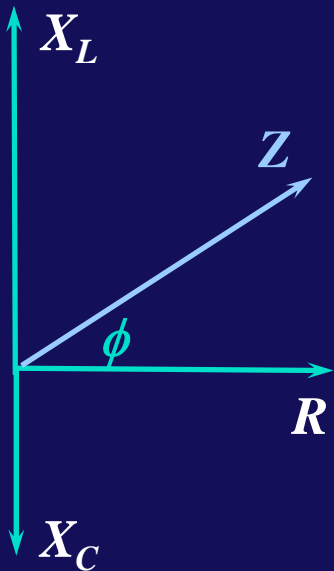
$$X_L \equiv \omega L$$
$$X_C \equiv \frac{1}{\omega C}$$




$$X_L > X_C$$
$$\phi > 0$$

**current  
LAGS  
applied voltage**

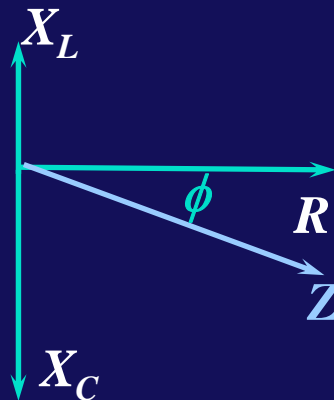

$$X_L < X_C$$
$$\phi < 0$$

**current  
LEADS  
applied voltage**

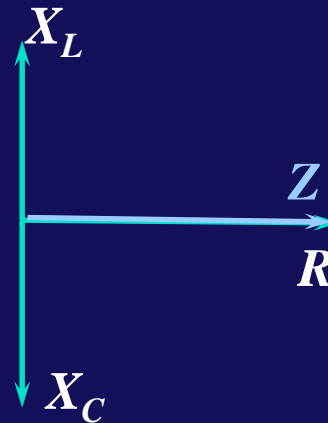



$$X_L = X_C$$
$$\phi = 0$$

**current  
IN PHASE WITH  
applied voltage**

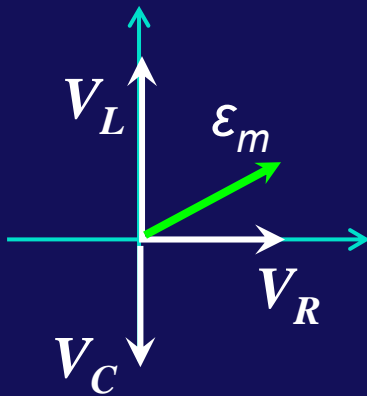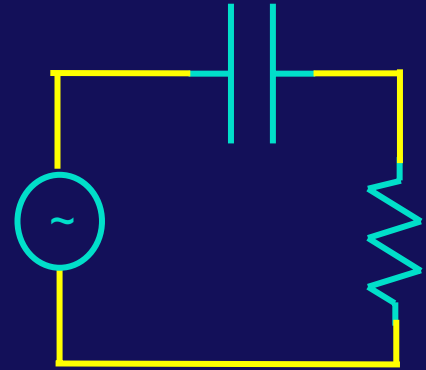
# Lecture 19, Act 2

2A


A series RC circuit is driven by emf  $\mathcal{E}$ . Which of the following could be an appropriate phasor diagram?



(a)

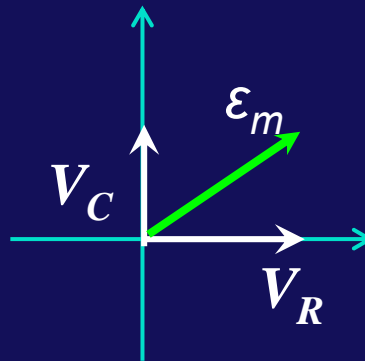

(b)

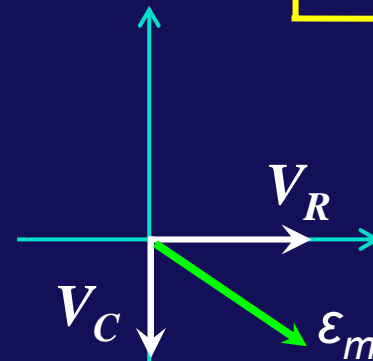

(c)

2B





For this circuit which of the following is true?

- (a) The drive voltage is in phase with the current.
- (b) The drive voltage lags the current.
- (c) The drive voltage leads the current.
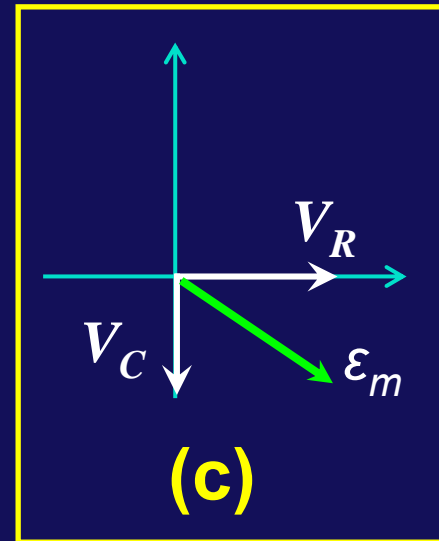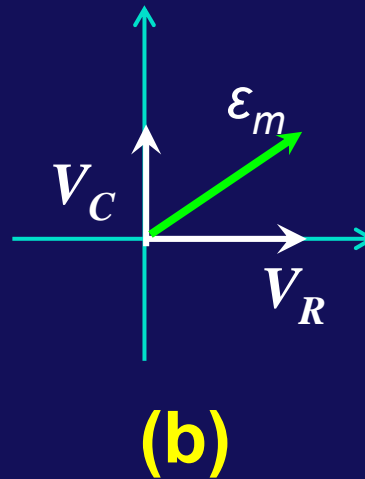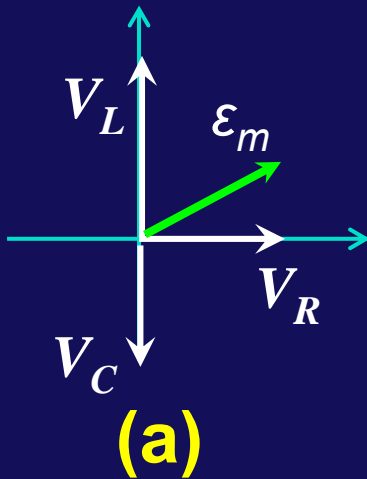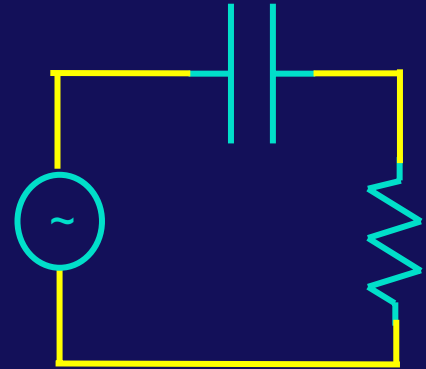
# Lecture 19, Act 2

2A

A series RC circuit is driven by emf  $\epsilon$ . Which of the following could be an appropriate phasor diagram?




- The phasor diagram for the driven series RLC circuit always has the voltage across the capacitor lagging the current by  $90^\circ$ . The vector sum of the  $V_C$  and  $V_R$  phasors must equal the generator emf phasor  $\epsilon_m$ .

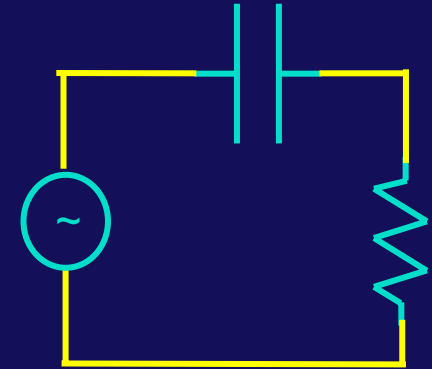
# Lecture 19, Act 2

2B

For this circuit which of the following is true?



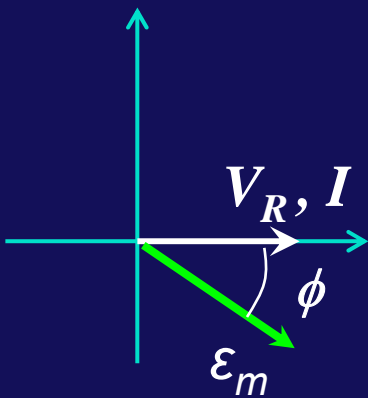- (a) The drive voltage is in phase with the current.
- (b) The drive voltage lags the current.
- (c) The drive voltage leads the current.



First, remember that the current phasor  $I$  is *always* in the same orientation as the resistor voltage phasor  $V_R$  (since the current and voltage are always in phase). From the diagram, we see that the drive phasor  $\varepsilon_m$  is *lagging* (clockwise)  $I$ . Just as  $V_C$  lags  $I$  by  $90^\circ$ , in an AC driven RC circuit, the drive voltage will also lag  $I$  by some angle less than  $90^\circ$ . The precise phase lag  $\phi$  depends on the values of  $R$ ,  $C$  and  $\omega$ .


# Impedance, $Z$

- From the phasor diagram we found that the current amplitude  $I$  was related to the drive voltage amplitude  $\varepsilon_m$  by

$$\varepsilon_m = I Z$$

- $Z$  is known as the “impedance”, and is basically the frequency dependent equivalent resistance of the series LRC circuit, given by:

“Impedance Triangle”

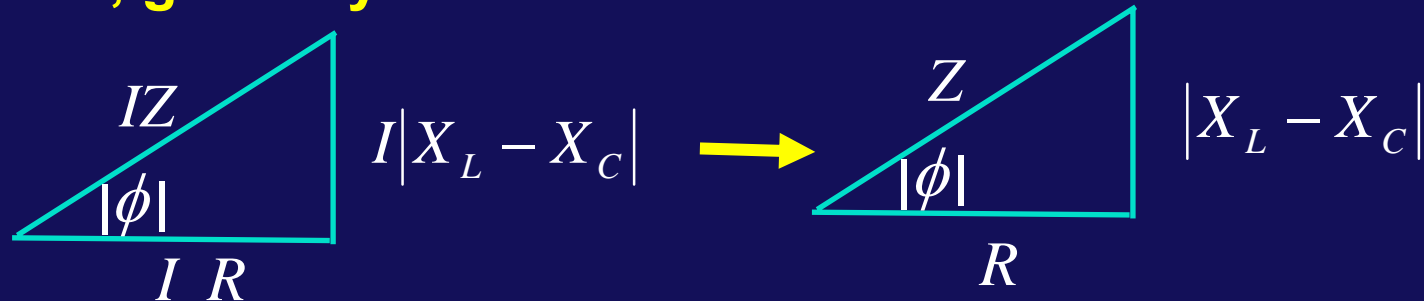

$$Z \equiv \frac{\varepsilon_m}{I} = \sqrt{R^2 + (X_L - X_C)^2}$$

or

$$Z = \frac{R}{\cos(\phi)}$$

- Note that  $Z$  achieves its minimum value ( $R$ ) when  $\phi = 0$ . Under this condition the maximum current flows in the circuit.

# Resonance

- For fixed  $R$ ,  $C$ ,  $L$  the current  $I$  will be a maximum at the resonant frequency  $\omega$  which makes the impedance  $Z$  purely resistive ( $Z = R$ ). i.e.,

$$I = \frac{\mathcal{E}_m}{Z} = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

reaches a maximum when:

$$X_L = X_C$$

This condition is obtained when:

$$\omega L = \frac{1}{\omega C} \quad \Rightarrow \quad \omega = \frac{1}{\sqrt{LC}}$$


- Note that this resonant frequency is identical to the natural frequency of the LC circuit by itself!
- At this frequency, the current and the driving voltage are in phase:

$$\tan \phi = \frac{X_L - X_C}{R} = 0$$


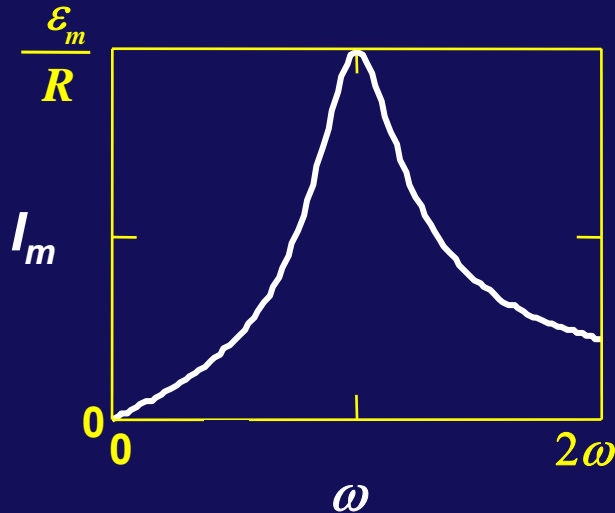
# Resonance

Plot the current versus  $\omega$ , the frequency of the voltage source:



- For  $\omega$  very large,  $X_L \gg X_C$ ,  $\phi \rightarrow 90^\circ$ ,  $I_m \rightarrow 0$
- For  $\omega$  very small,  $X_C \gg X_L$ ,  $\phi \rightarrow -90^\circ$ ,  $I_m \rightarrow 0$

**Example: vary R**


**V=100 v**

**$\omega=1000$  rad/s**


**R=200, 500, 2000 ohm**

**L=2 H**

**C=0.5  $\mu$ C**

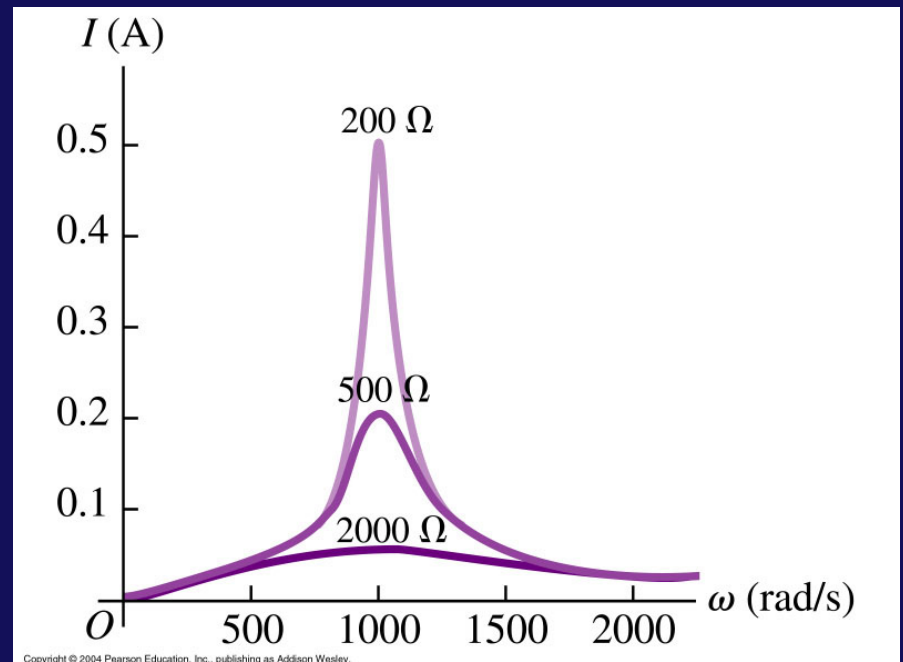

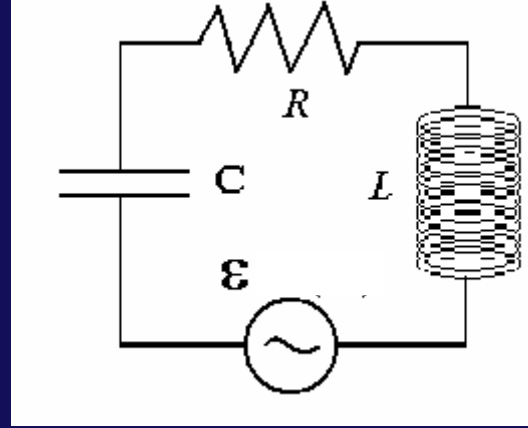Consider a general AC circuit containing a resistor, capacitor, and inductor, driven by an AC generator.



1) As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit \_\_\_\_\_.

- a) always increases
- b) only increases for lowering the frequency below resonance
- c) only increases for raising the frequency above resonance


2) At the resonant frequency, which of the following is true?

- a) The current leads the voltage across the generator.
- b) The current lags the voltage across the generator.
- c) The current is in phase with the voltage across the generator.

- Impedance  $= Z = \sqrt{R^2 + (X_L - X_C)^2}$
- At resonance,  $(X_L - X_C) = 0$ , and the impedance has its minimum value:  $Z = R$

- As frequency is changed from resonance, either up or down,  $(X_L - X_C)$  no longer is zero and  $Z$  must therefore increase.

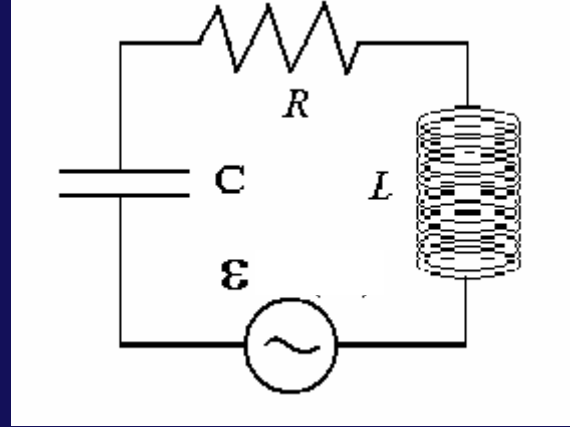Changing the frequency away from the resonant frequency will change both the inductive and capacitive reactance such that  $X_L - X_C$  is no longer 0. This, when squared, gives a positive term to the impedance, increasing its value. By definition, at the resonance frequency,  $I_{\max}$  is at its greatest and the phase angle is 0, so the current is in phase with the voltage across the generator.




4) Fill in the blank. This circuit is being driven \_\_\_\_\_ its resonance frequency.

a) above

b) below

c) exactly at

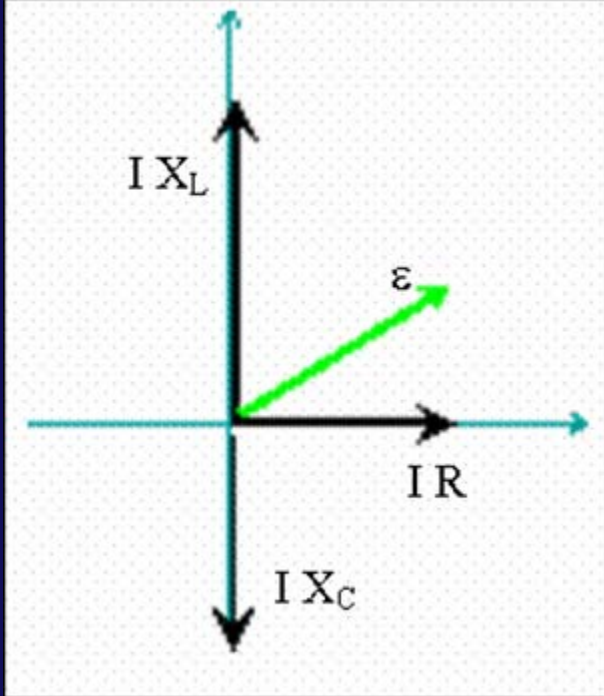

5) The generator voltage \_\_\_\_\_ the current.

a) leads

b) lags


c) is in phase with

# Power in LRC circuit

$$i(t) = I(t) \cos(\omega t); \quad v_{ad}(t) = V \cos(\omega t + \phi)$$

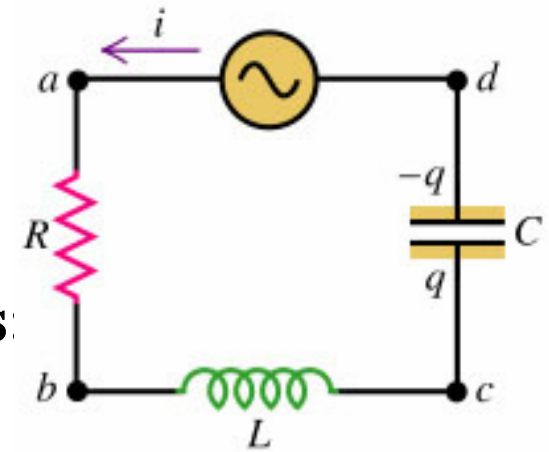**The instantaneous power delivered to L-R-C is:**

$$P(t) = i(t)v_{ad}(t) = V \cos(\omega t + \phi) I \cos(\omega t)$$



**We can use trig identities to expand the above to,**

$$P(t) = V[\cos(\omega t)\cos(\phi) - \sin(\omega t)\sin(\phi)]I \cos(\omega t)$$

$$= VI \cos^2(\omega t)\cos(\phi) - VI \sin(\omega t)\cos(\omega t)\sin(\phi)$$

$$P_{ave} = \langle P(t) \rangle = VI \left\langle \frac{1}{2}(\cos(2\omega t) + 1) \right\rangle \cos(\phi) - VI \left\langle \frac{1}{2}\sin(2\omega t) \right\rangle \sin(\phi)$$

$$= VI \left( \frac{1}{2} \right) \cos(\phi)$$

$$P_{ave} = \langle P(t) \rangle = \frac{1}{2} VI \cos(\phi) = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} \cos(\phi)$$

$$= V_{RMS} I_{RMS} \cos(\phi)$$

# Power in LRC circuit, continued

$$P_{ave} = \langle P(t) \rangle = \frac{1}{2} VI \cos(\phi) = V_{RMS} I_{RMS} \cos(\phi)$$

General result.  $V_{RMS}$  is voltage across element,  $I_{RMS}$  is current through element, and  $\phi$  is phase angle between them.

Example; 100Watt light bulb plugged into 120V house outlet, Pure resistive load (no L and no C),  $\phi = 0$ .

$$P = I_{rms} V_{rms} = \frac{V_{rms}^2}{R}$$

$$R = \frac{V_{rms}^2}{P_{ave}} = \frac{120^2}{100} = 144\Omega$$

$$I_{rms} = \frac{P_{ave}}{V_{rms}} = \frac{100}{120} = 0.83A$$

Note; 120V house voltage is rms and has peak voltage of  $120\sqrt{2} = 170V$

Question: What is  $P_{AVE}$  for an inductor or capacitor?

# Summary

- **Power**

“power factor”

$$\langle P(t) \rangle = \varepsilon_{rms} I_{rms} \cos \phi$$
$$= (I_{rms})^2 R$$

$$\varepsilon_{rms} \equiv \frac{1}{\sqrt{2}} \varepsilon_m$$

$$I_{rms} \equiv \frac{1}{\sqrt{2}} I_m$$

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

- **Driven Series LRC Circuit:**

- **Resonance condition**
  - » **Resonant frequency**

$$\omega = \frac{1}{\sqrt{LC}}$$