
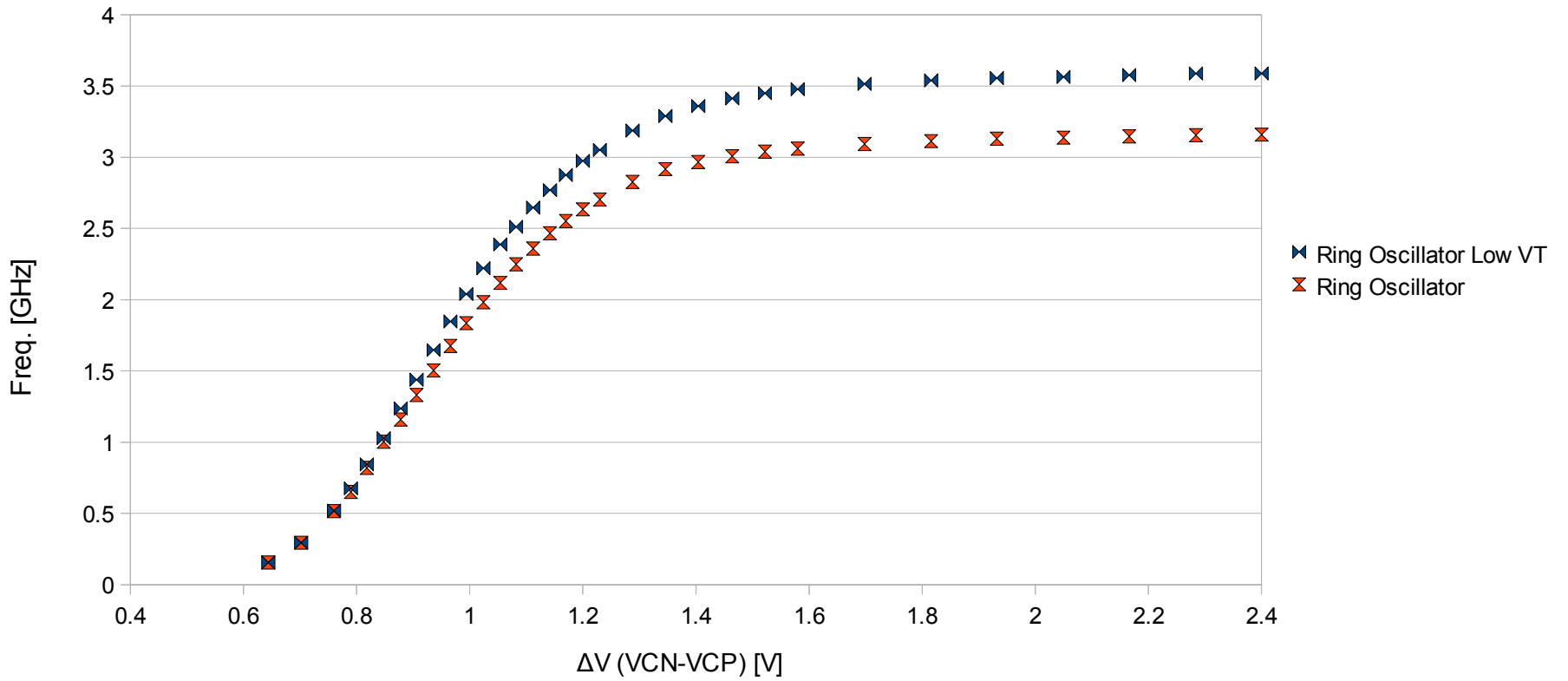


Ring Oscillators Freq vs. delta V (VCN-VCP)

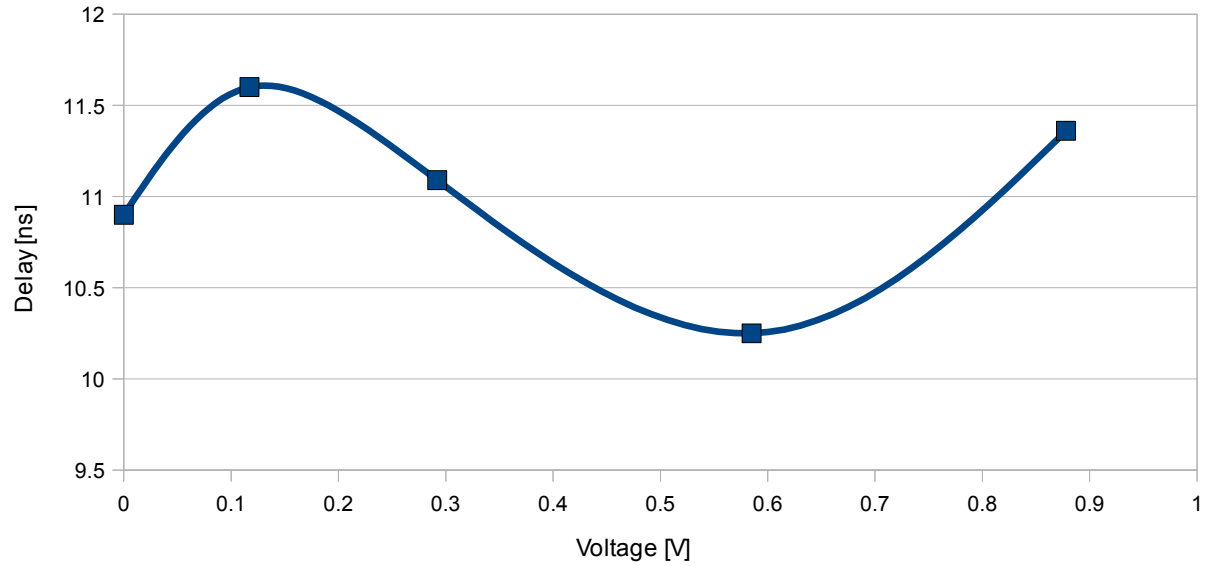
Below voltage differences of 640mV the output does not behave reliably



VCDLOUT1 vs Delay



VCDLOUT2 vs Delay

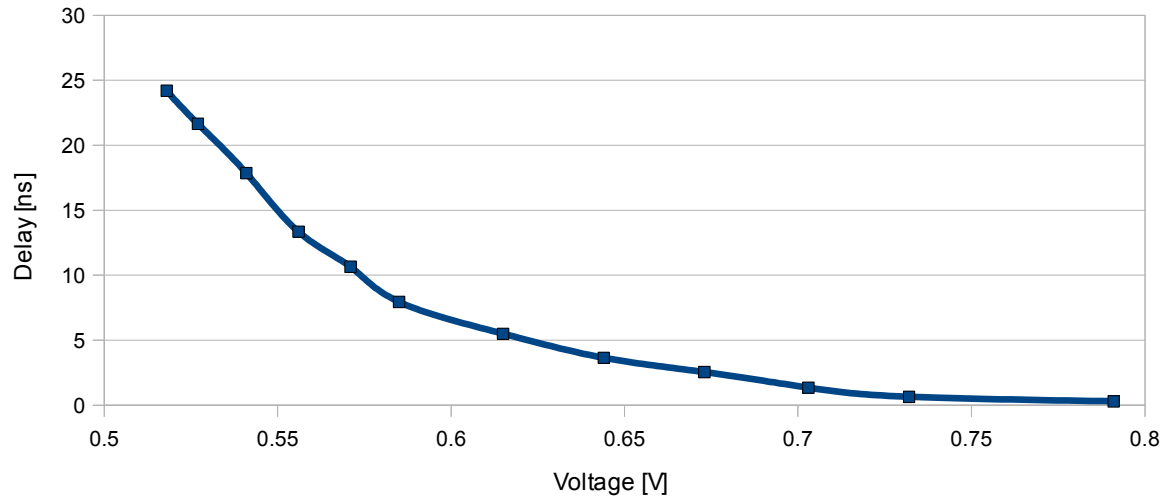

For voltages below .515 V there was no measurable output.
For voltages above .8 V the scope included an extra clock cycle in the delay