



UNIVERSITY
of HAWAI'I®
MĀNOA

Instrumentation Development Laboratory

XRM – Detector Electronics tests, Pulse response investigation


Peter Orel, Gary S. Varner, Matt Andrew

Pre-Amp Pulse response

Test setup



Equipment:

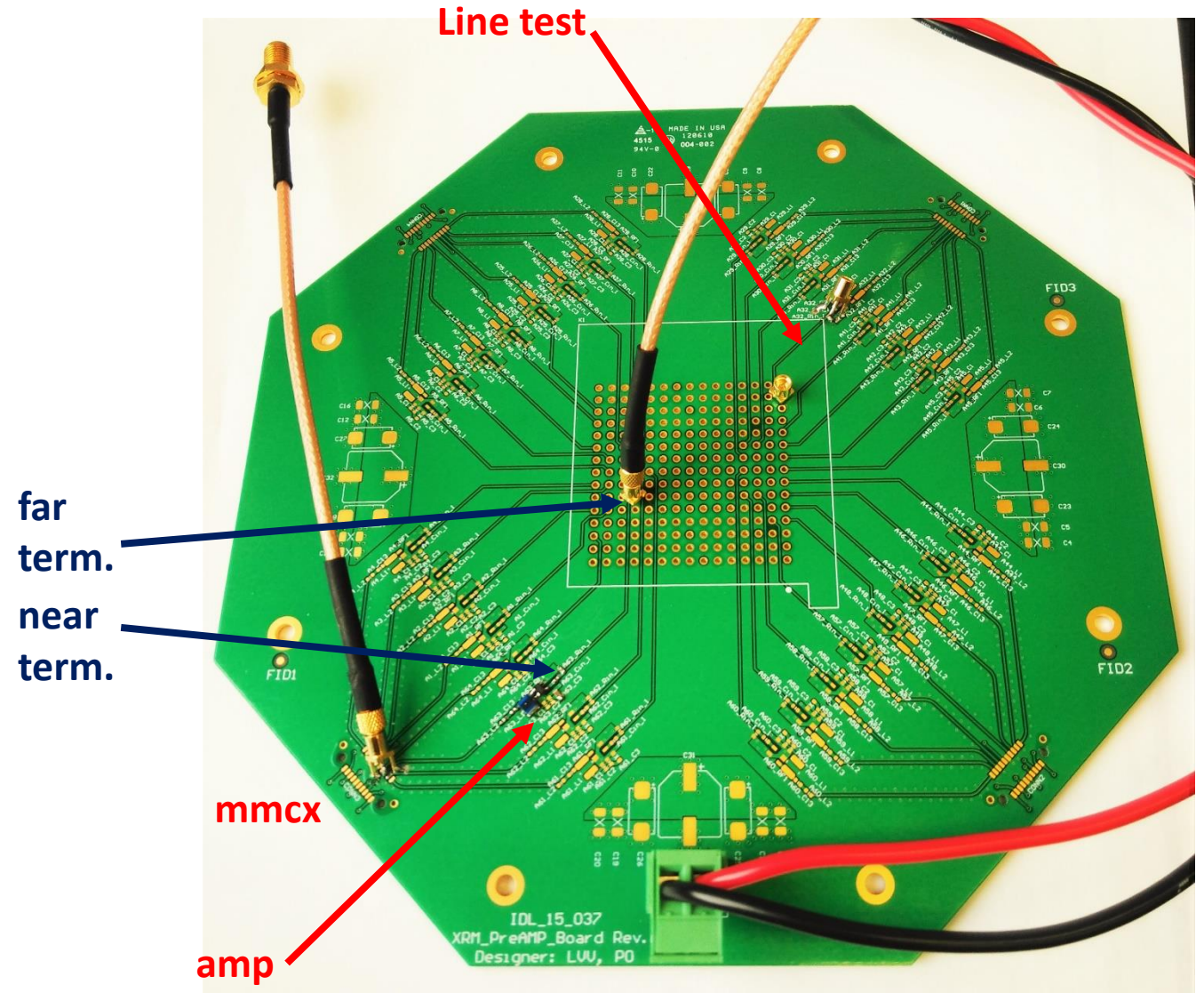- Voltage probe: Fluke 179
- Pulse generators:
 - Avtech AVP-25-C-P-CM1-OS (4944)
 - Picosecond Pulse Labs m.3500c
 - Agilent 33250A
- Power supply: Quakko HY3005DP-3
- VNA: Agilent PNA-L N5230C
- Scope: Agilent MSO8104A




Pre-Amp Pulse response

Input pulse(s)

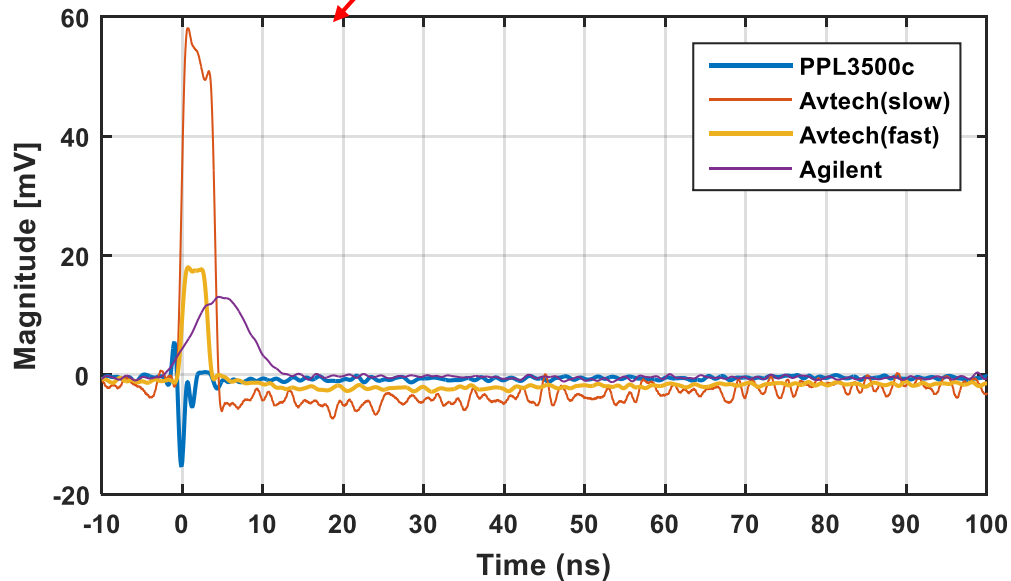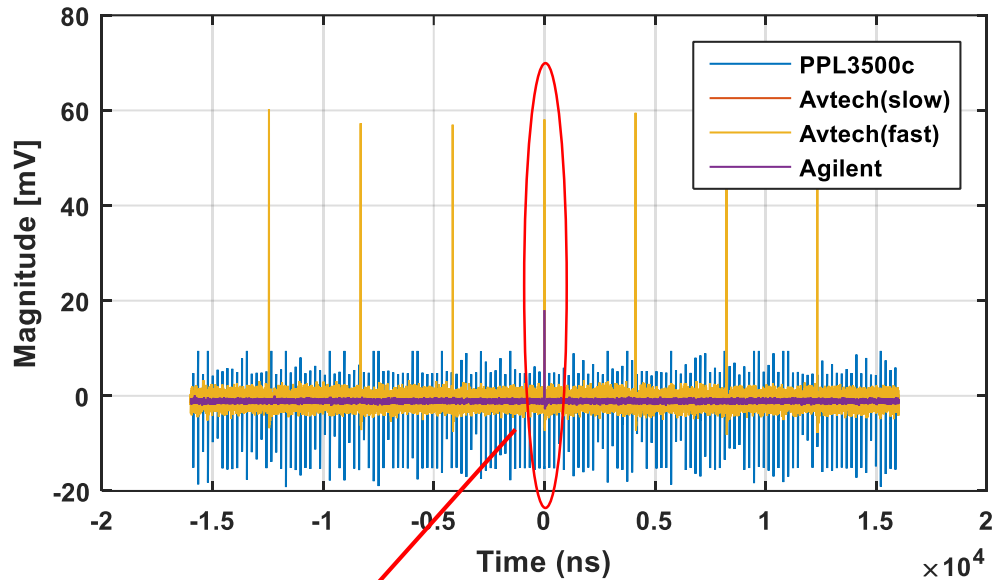



Input pulse comparison

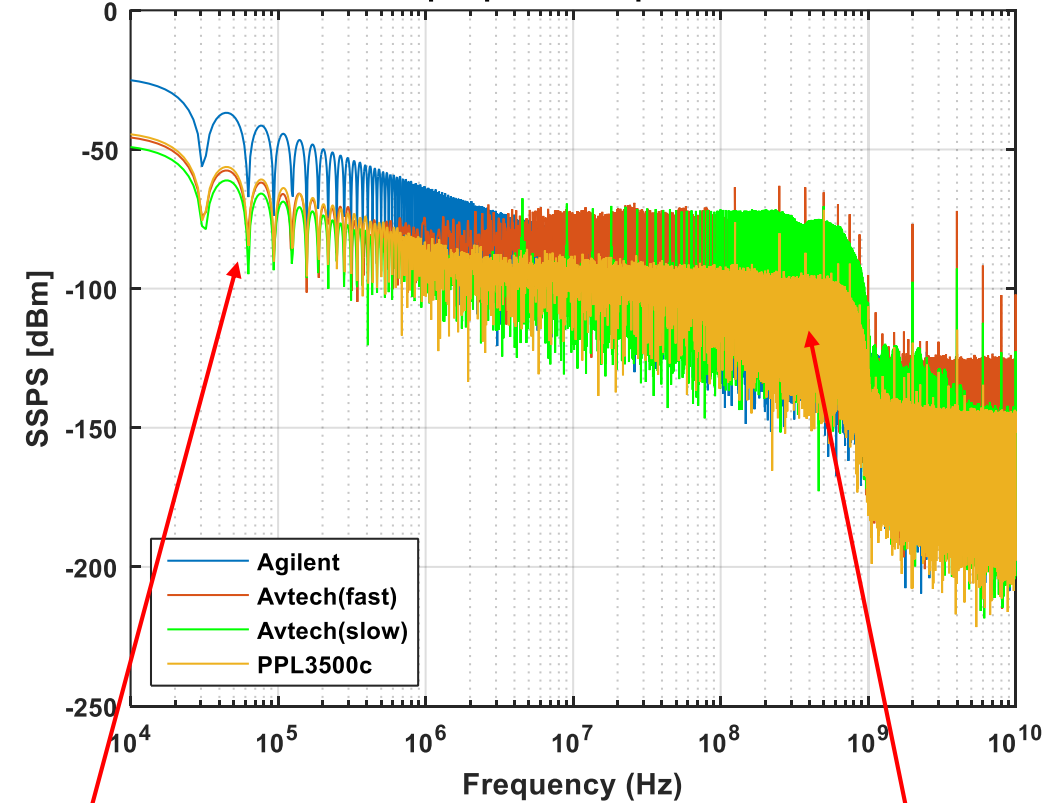

- Slow rate and slow pulse(Agilent) → some energy other than noise present at low-frequency
- Fast rate and fast pulse (PPL3500c) → most energy at high frequency

Pre-Amp Pulse response

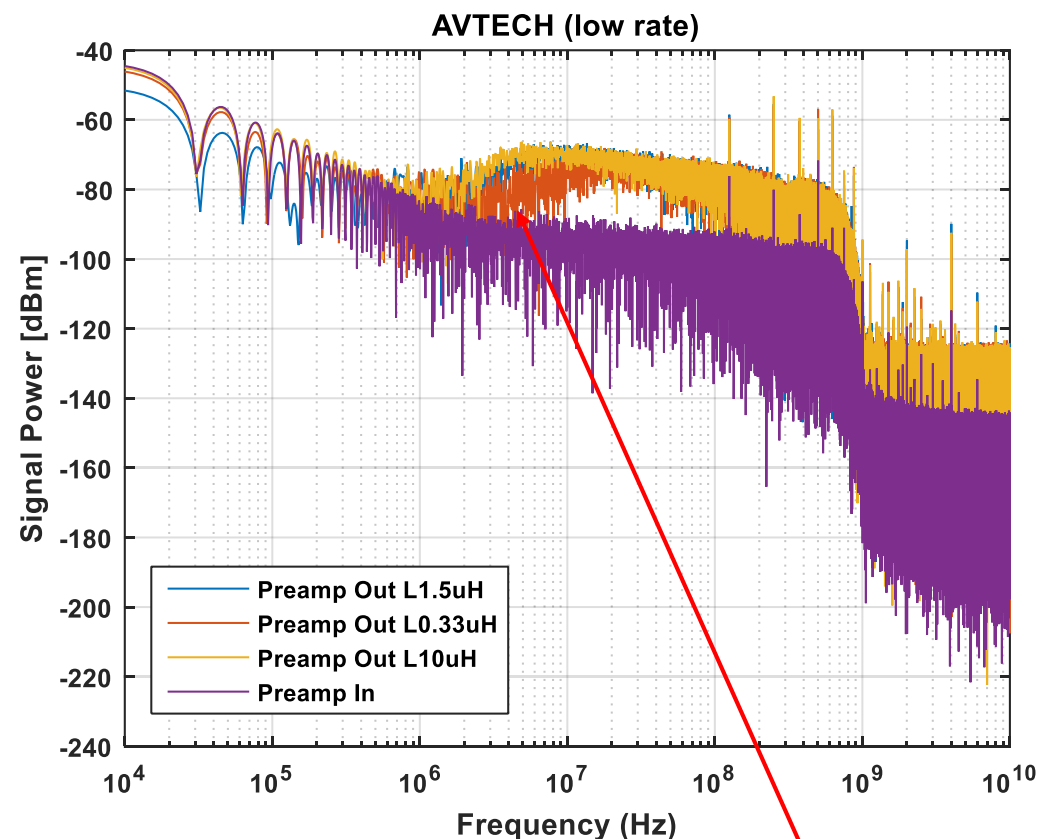
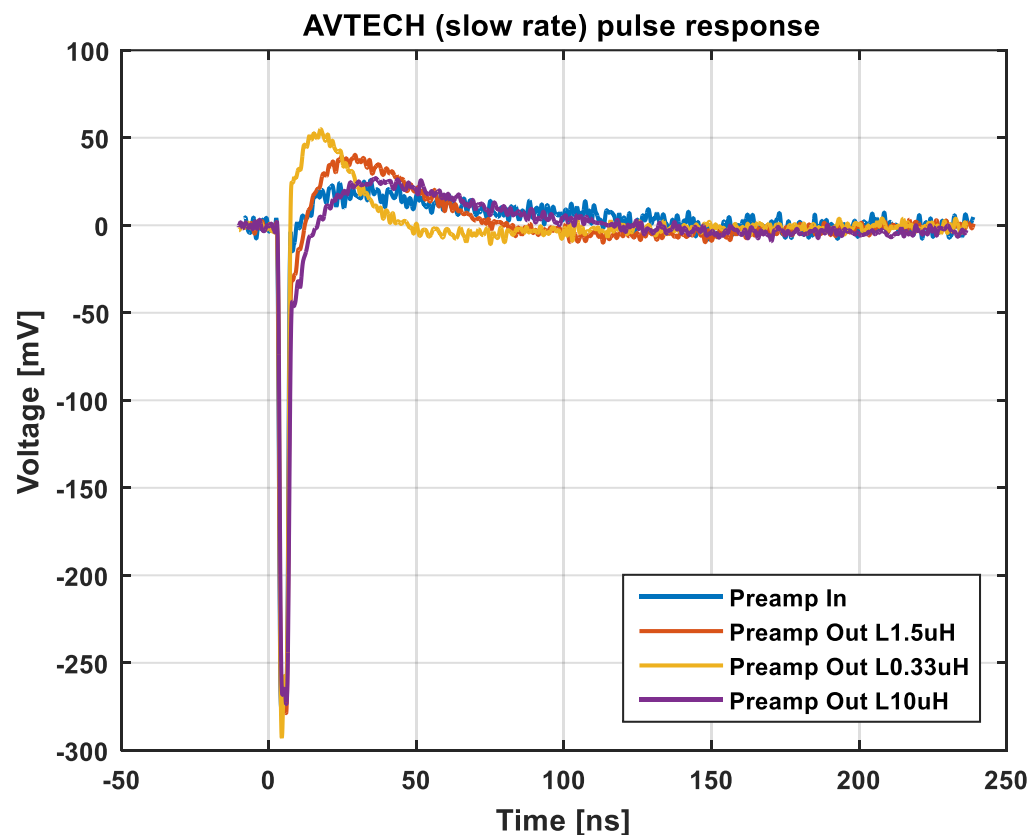
AVTECH pulse with different bias inductors



- Different inductor changes mid-frequency response
- A pronounced tail (L1.5) creates some mid-freq. components while a faster tail doesn't (L0.33).
- All measurements from now on are with 10uH inductor

Pre-Amp Pulse response



Agilent Pulse Generator (slow pulse)

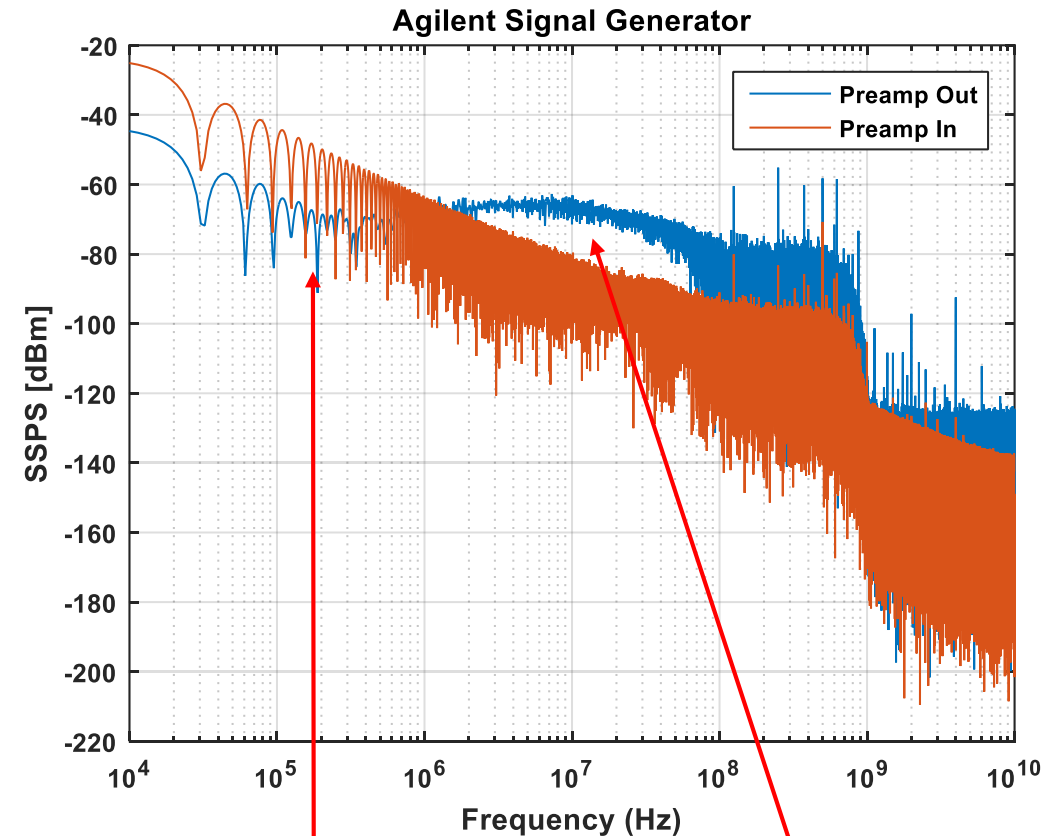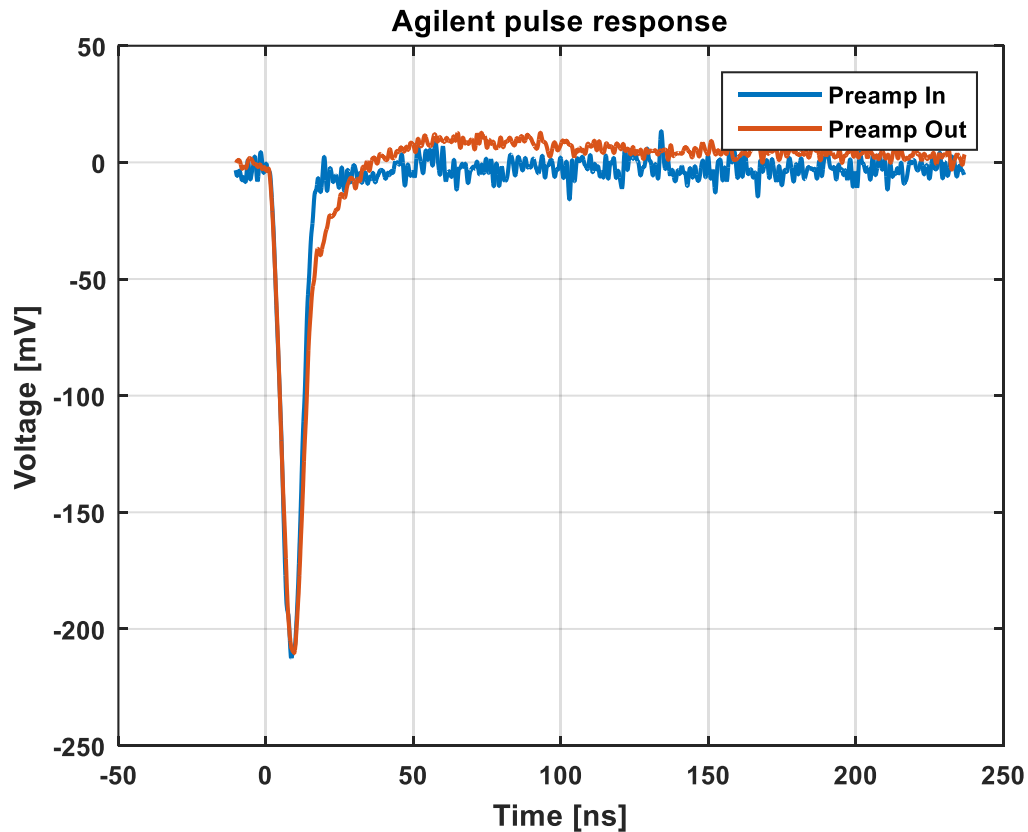

- A lot of DC energy cut off
- Pulse altered...tail produces low-mid frequency components (even more pronounced than before)

Pre-Amp Pulse response


PPL3500c (fast pulses)

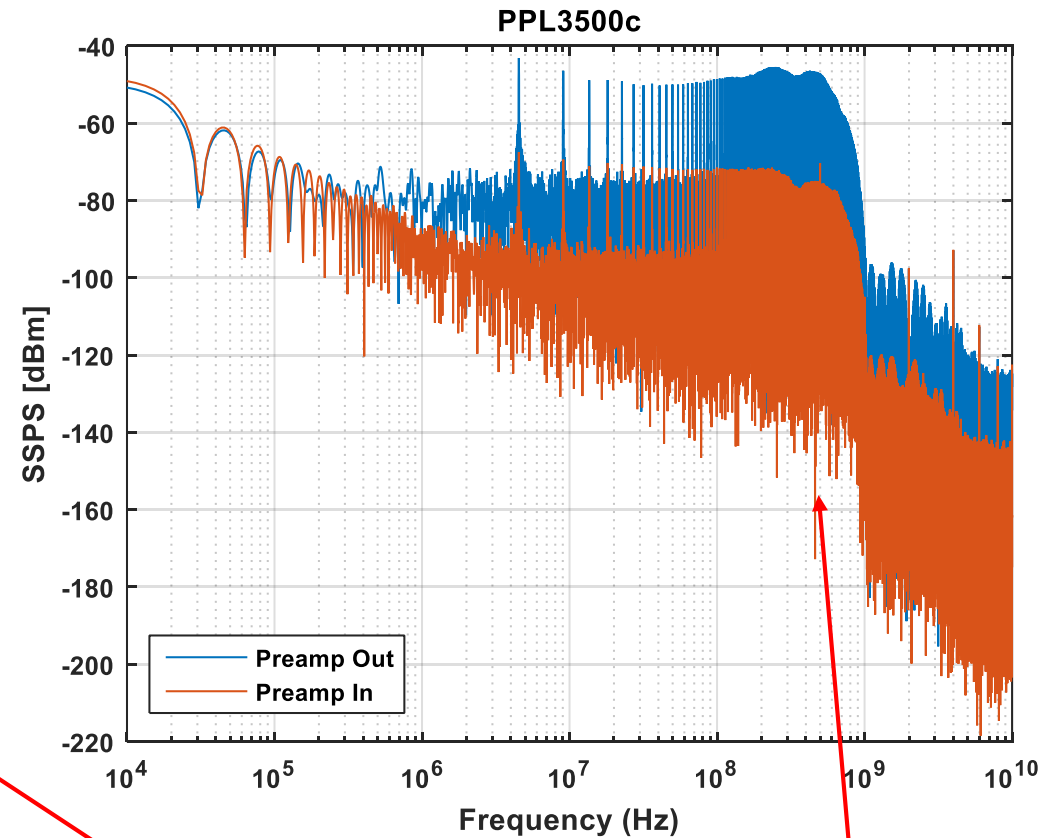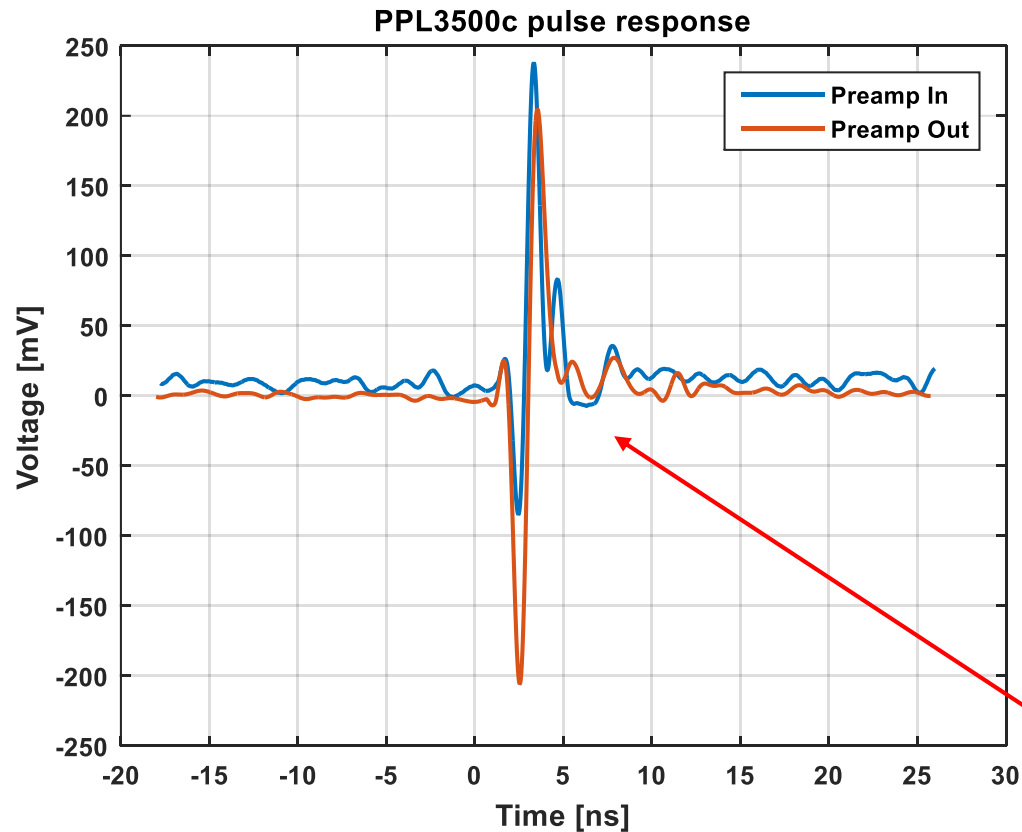

- Pulse is not significantly altered (most of the energy is at high frequency)

Amp Pulse response

Test setup






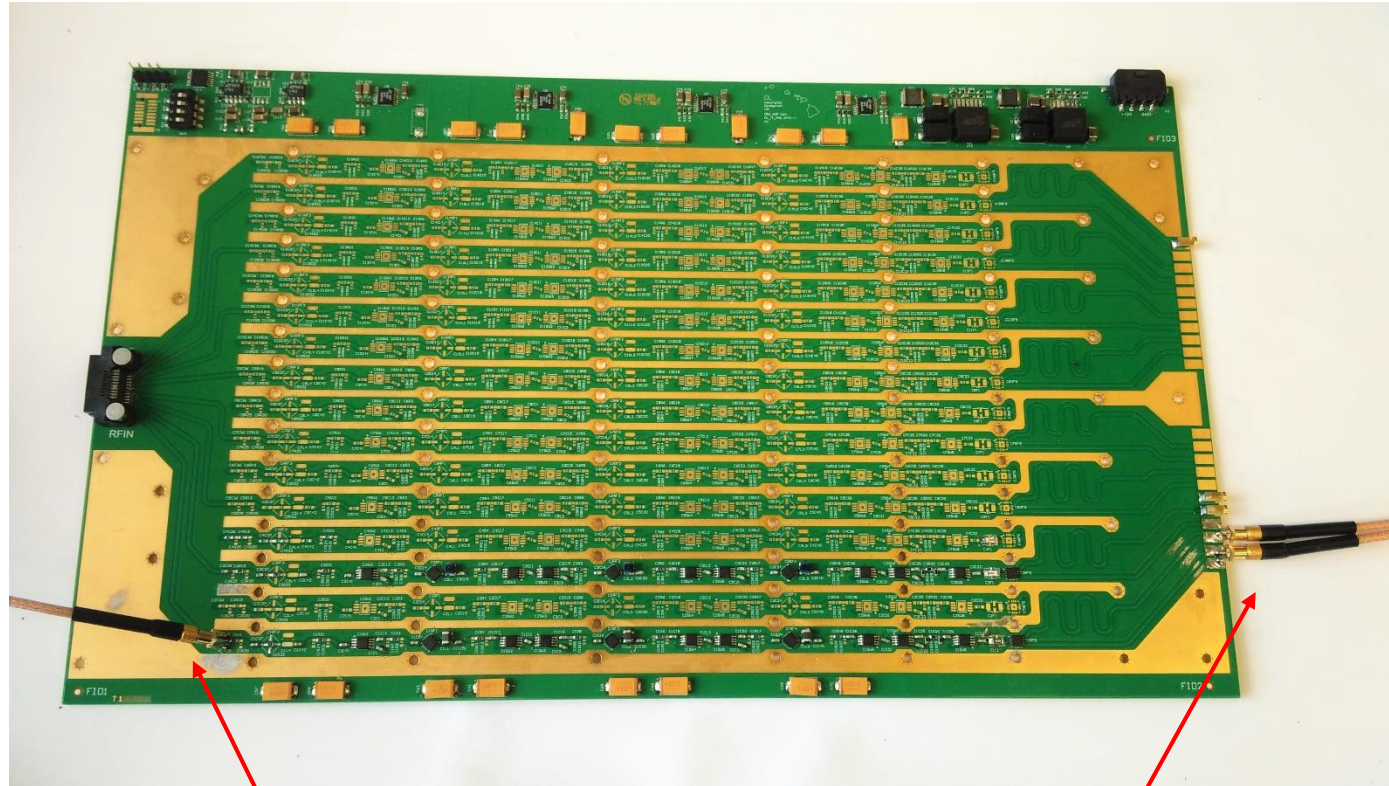


- MMCX on input and output
- All AC coupling capacitors were changed to 100nF and the bias inductors to 10uH

- Similar story as with the Pre-Amp but better at low frequency

Amp Pulse response


Pulse response

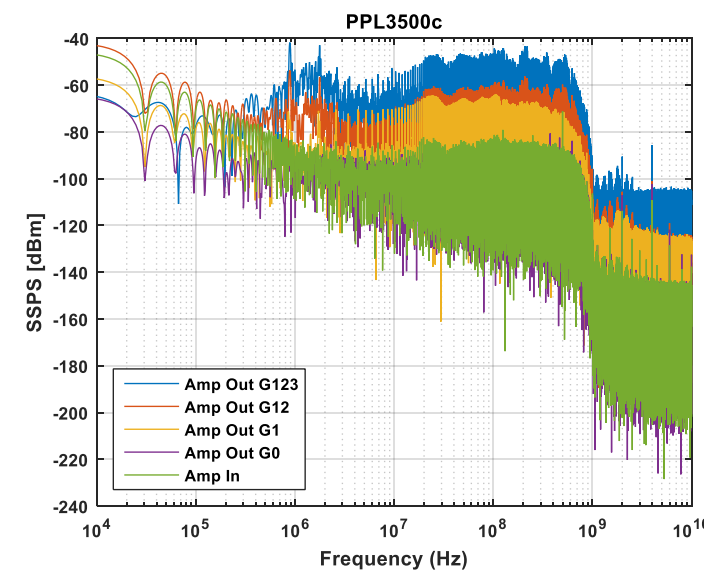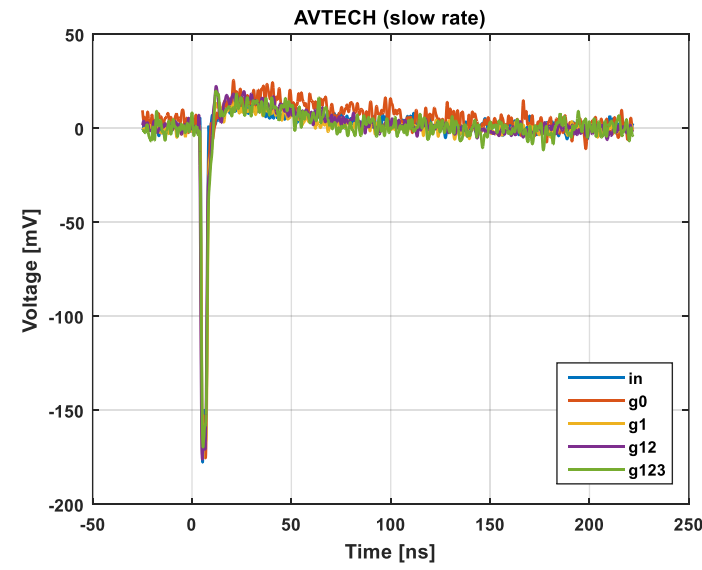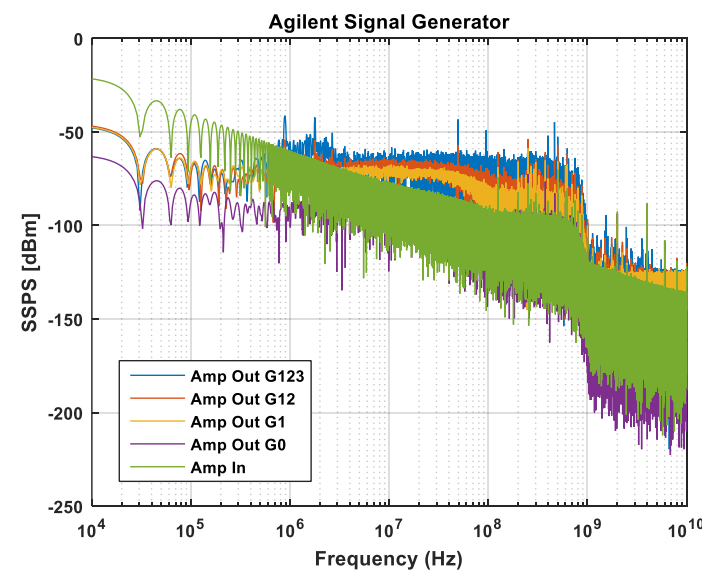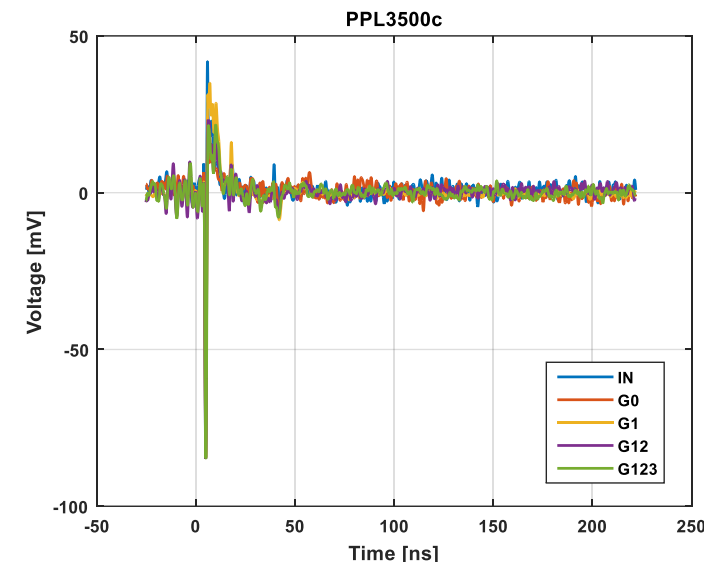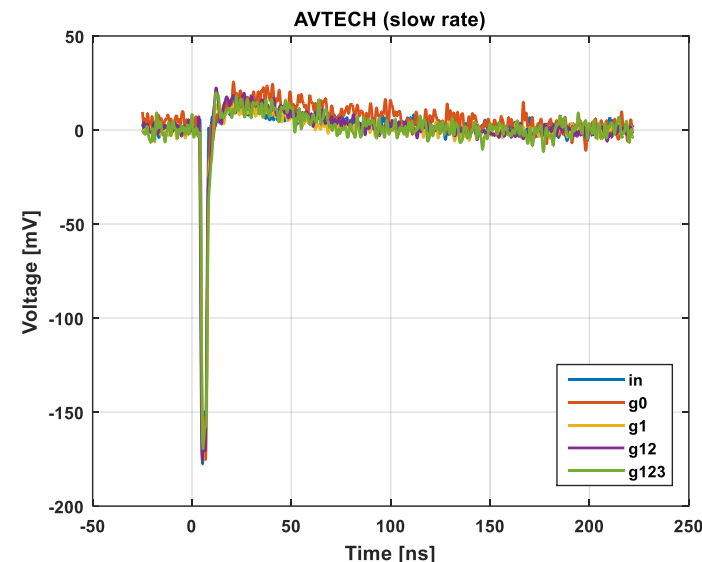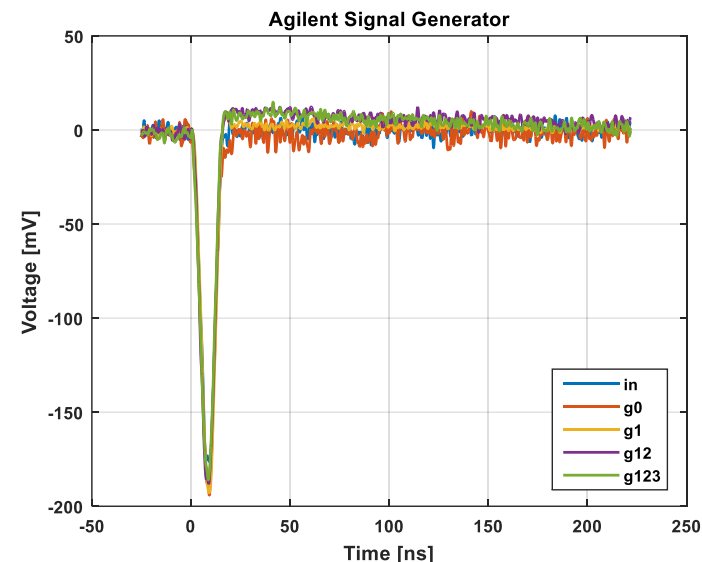


Pre-Amp & Amp Pulse response

Summary

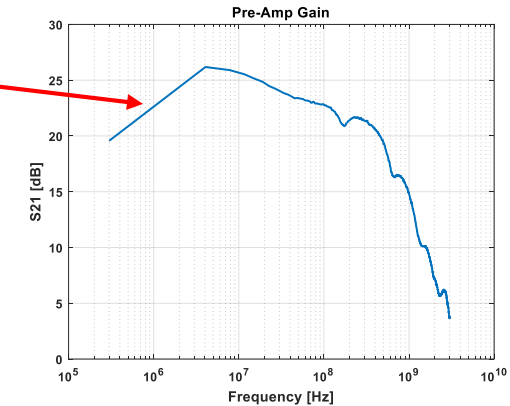- System not optimized for amplifying low frequency content
 - Slower pulses make for worse response
 - Tails seem to give rise to mid-frequency components
- System seem to respond reasonably well to faster pulses
 - Do to 1GHz bandwidth limitation of the Scope the real pulse might be a bit different -> need faster scope
- All of the tried pulses do not reach the “expected” target waveform



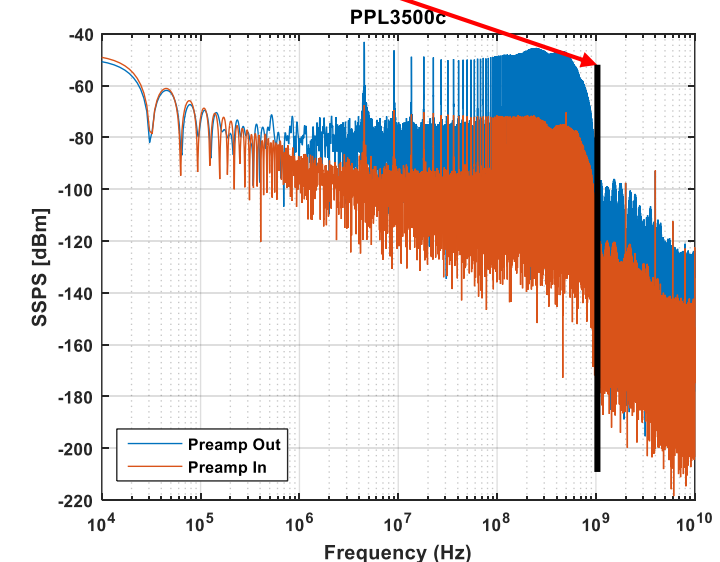
- Next priority should be to get some “expected” waveform data and optimize the electronics for it




Pre-Amp & Amp Frequency response

Summary


Pre-Amp & Amp Gain

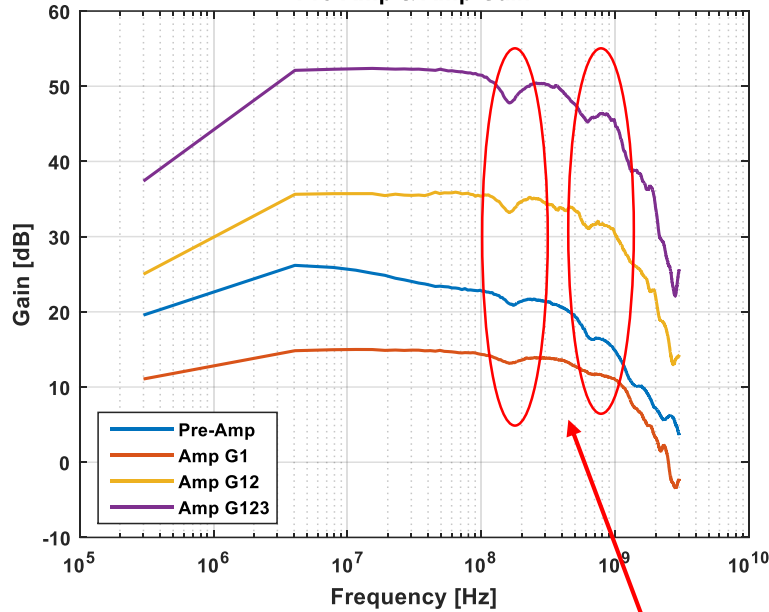

Pre-Amp & Amp Compression curve

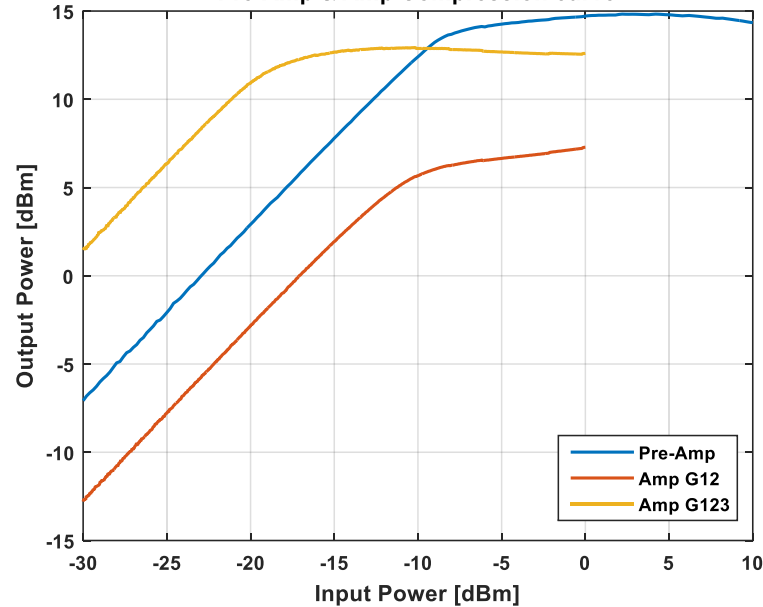

Pre-Amp & Amp Group Delay

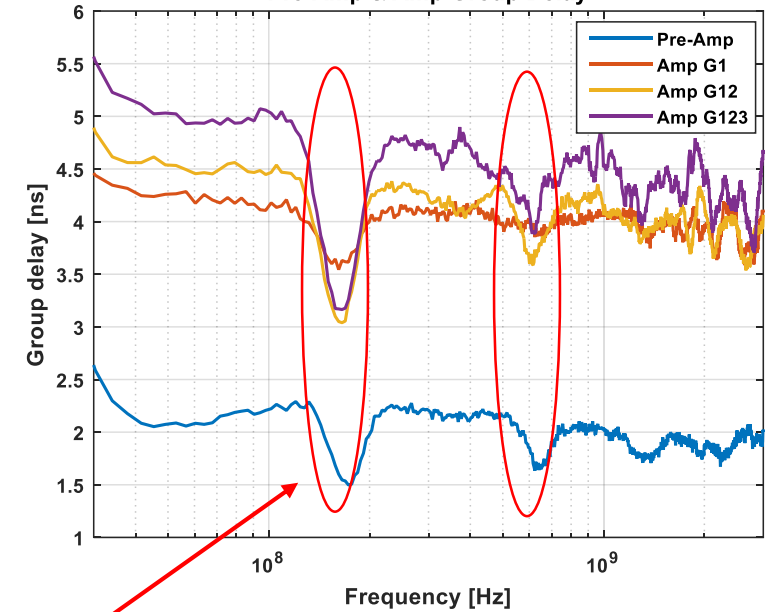

- Amp board has flatter gain response

- Compression is consistent with datasheet

- Group delay reasonably flat
 - Pre-amp: 2ns
 - Amp cumulative: 5ns

- Artifact of VNA (cold startup)

Potential issue for narrow pulse?