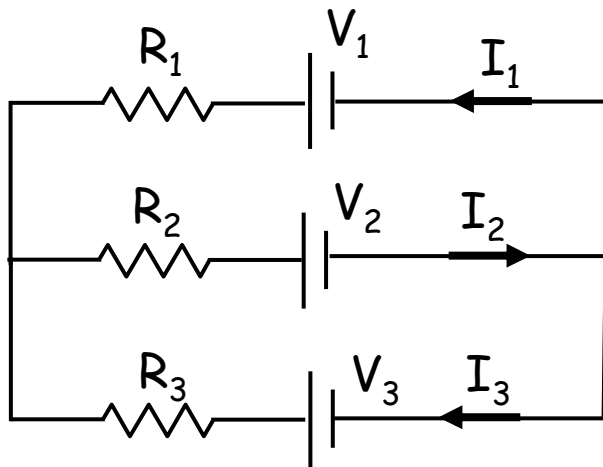


Lecture 11

Kirchoff Circuit Rules

RC- Circuits

Review



In this circuit, assume V_i and R_i are known.

What is I_2 ??

We need 3 equations:
which 3 should we use?

A) Any 3 will do

B) 1, 2, and 4

C) 2, 3, and 4

• We have the following 4 equations:

1. $I_2 = I_1 + I_3$

2. $-V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$

3. $-V_3 + I_3 R_3 + I_2 R_2 + V_2 = 0$

4. $-V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$



• Why??

- We need 3 INDEPENDENT equations
- We must choose Equation 1 and any two of the remaining (2, 3, and 4)
- Equations 2, 3, and 4 are NOT INDEPENDENT
 - Eqn 2 + Eqn 3 = - Eqn 4

$$\begin{array}{l} \text{EQ2} + \text{EQ3} \\ -V_1 + I_1 R_1 + I_2 R_2 + V_2 = 0 \end{array}$$



Calculation

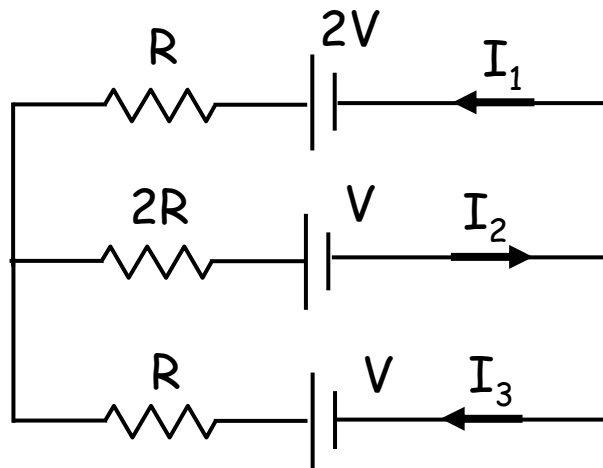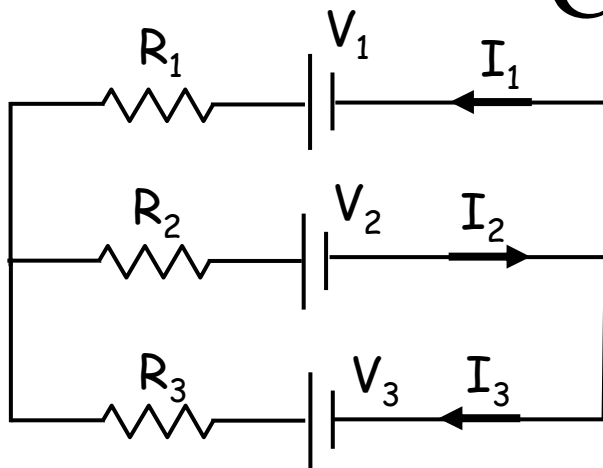

In this circuit, assume V_i and R_i are known.

What is I_2 ??

- We have 3 equations and 3 unknowns.

$$I_2 = I_1 + I_3$$

$$V_1 + I_1 R_1 - I_3 R_3 + V_3 = 0$$

$$V_2 - I_2 R_2 - I_1 R_1 + V_1 = 0$$

- The solution will get very messy in general.

• Instead do a simpler problem:


- assume $V_2 = V_3 = V$; $V_1 = 2V$; $R_1 = R_3 = R$ with $R_2 = 2R$



Calculation: Simplify

In this circuit, assume V and R are known.

What is I_2 ??

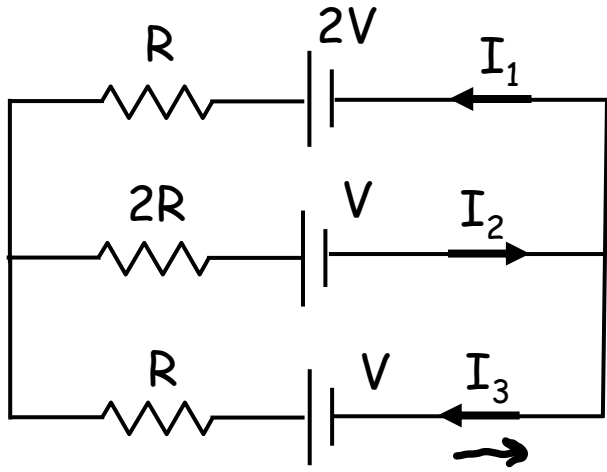

- We have 3 equations and 3 unknowns.

$$I_2 = I_1 + I_3$$

$$-2V + I_1R - I_3R + V = 0$$

(outside)

$$-V - I_2(2R) - I_1R + 2V = 0$$

(top)

- With this simplification, you can verify:

$$I_2 = (1/5) V/R$$

$$I_1 = (3/5) V/R$$

$$I_3 = (-2/5) V/R$$

$$\frac{1}{5} = \frac{3}{5} + (-\frac{2}{5}) = \frac{1}{5}$$



$$V - V + I_3 R + 2I_2 R = 0 \quad I_3 R + 2I_2 R = 0 \rightarrow I_2 = -\frac{1}{2}I_3$$

$$-2V + I_1 R - I_3 R + V = 0 \rightarrow I_1 R - I_3 R = V \rightarrow I_1 - I_3 = \frac{V}{R}$$

$$I_3 + I_1 - I_2 = 0$$

$$\rightarrow I_3 + \frac{V}{R} + I_3 + \frac{1}{2}I_3 = 0$$

$$I_3 \left(1 + 1 + \frac{1}{2}\right) = -\frac{V}{R} \Rightarrow \frac{5}{2}I_3 = -\frac{V}{R}$$


$$I_3 = -\frac{2}{5} \frac{V}{R}$$

$$\rightarrow I_2 = \frac{1}{5} \frac{V}{R}$$


$$\rightarrow I_1 = I_2 - I_3 = \frac{1}{5} \frac{V}{R} + \frac{2}{5} \frac{V}{R} = \underline{\underline{\frac{3}{5} \frac{V}{R}}}$$

For reference only

Follow-Up Clicker

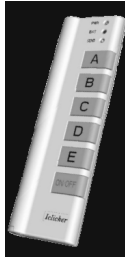

BB

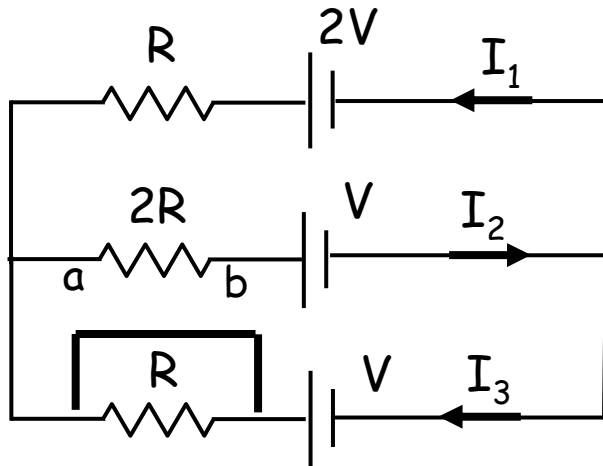

- We know:

$$I_2 = (1/5) V/R$$

$$I_1 = (3/5) V/R$$

$$I_3 = (-2/5) V/R$$

- Suppose we short R_3 :
(across R_2) ?

(A) V_{ab} remains the same


(B) V_{ab} changes sign

(C) V_{ab} increases

(D) V_{ab} goes to zero

What happens to V_{ab} (voltage

Why?
Redraw:

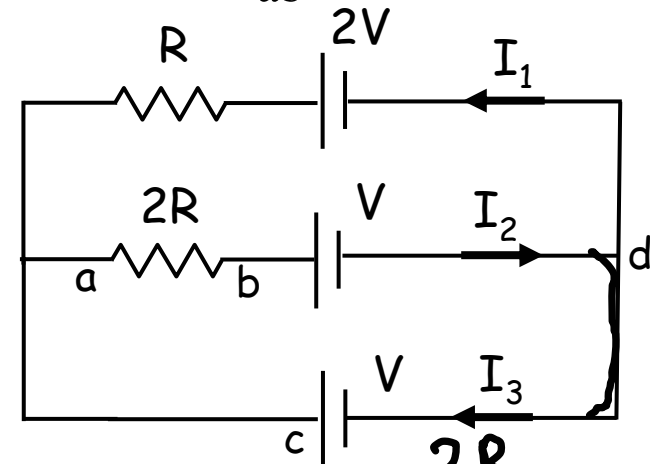


$$V_{cd} = +V$$



$$V_{bd} = +V$$

$$V_{ad} = V_{cd} = +V$$



$$V_{ab} = V_{ad} - V_{bd} = V - V = 0$$

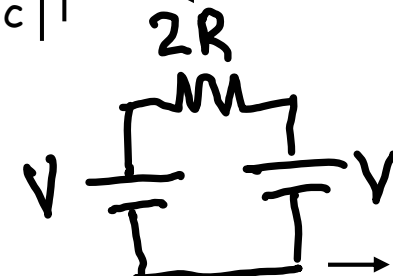

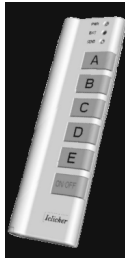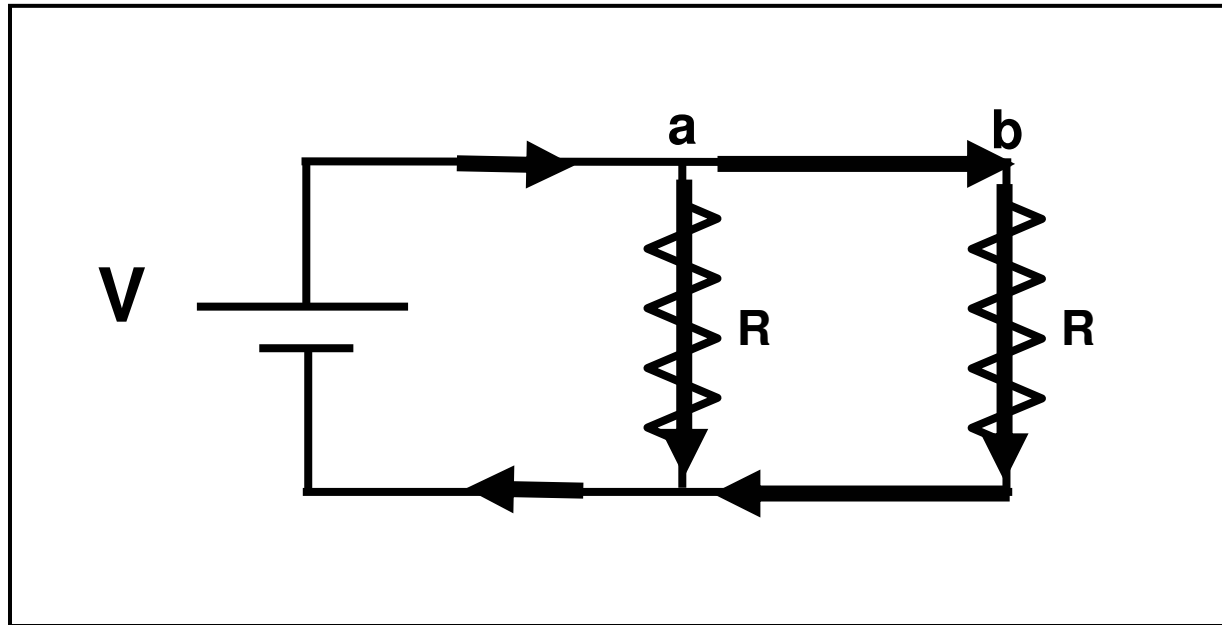


BB

Is there a current flowing between a and b ?

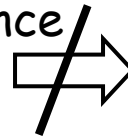
- A) Yes
- B) No

At first guess it might appear that since A & B have the same potential



No current flows between A & B

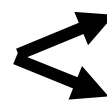Current flows from battery and splits at A





Some current flows down

Some current flows right

Consider the circuit shown below.

Clicker

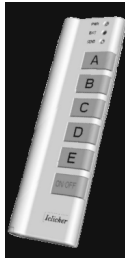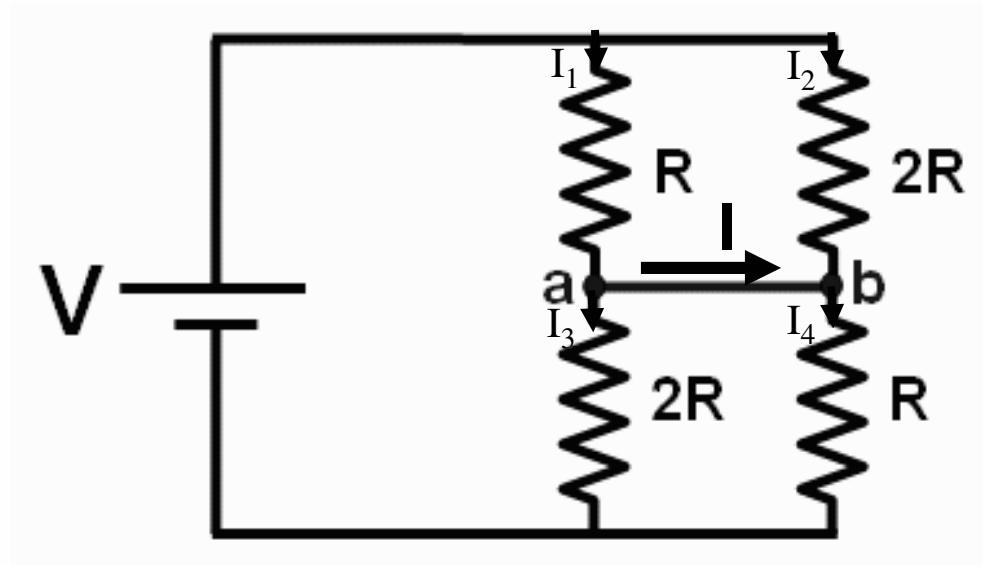

BB

Which of the following statements best describes the current flowing in the blue wire connecting points a and b



- Positive current flows from a to b Positive current flows from b to a No current flows between a and b

$$I_1 R - I_2 (2R) = 0 \Rightarrow I_1 = 2 I_2$$

$$I_4 R - I_3 (2R) = 0 \Rightarrow I_4 = 2 I_3$$


$$I_2 = I_3 \Rightarrow I_1 = 2 I_3$$

$$I = I_1 - I_3 = 2I_3 - I_3 = +I_3$$

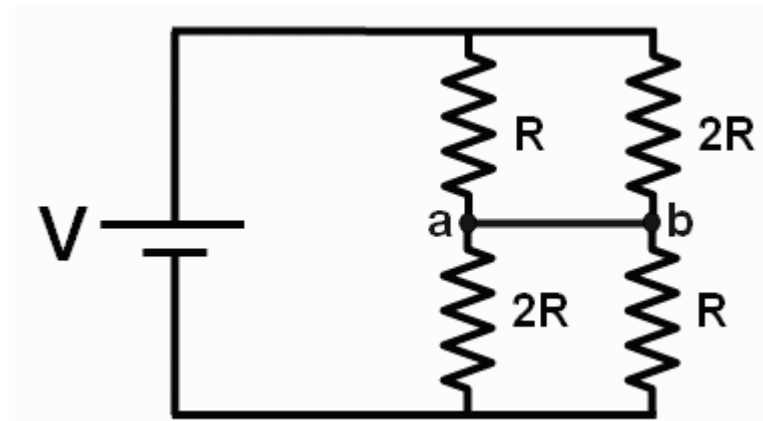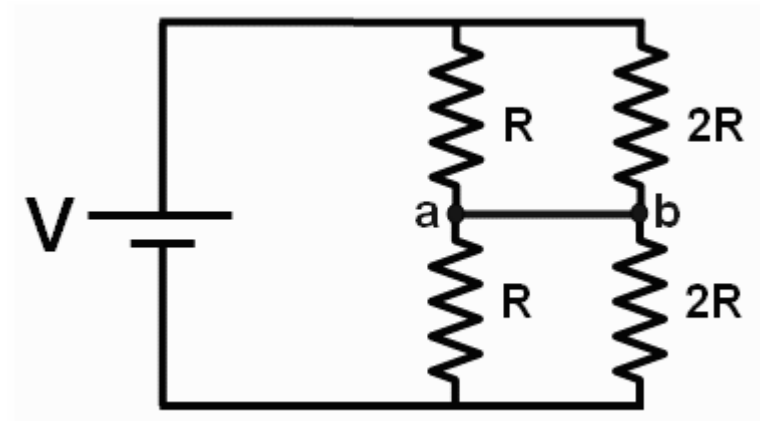



What is the same?

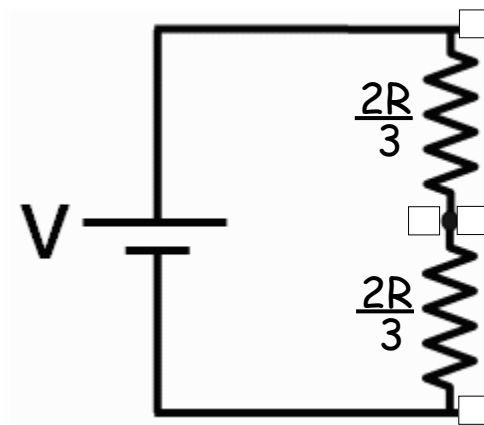Current flowing in and out of the battery




What is different?

Current flowing from a to b

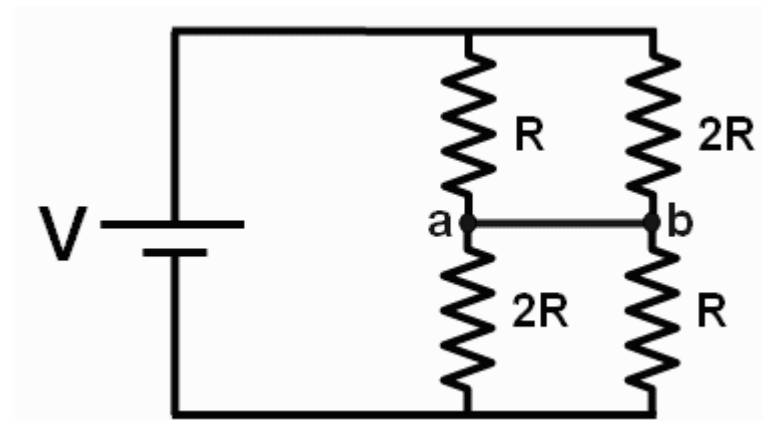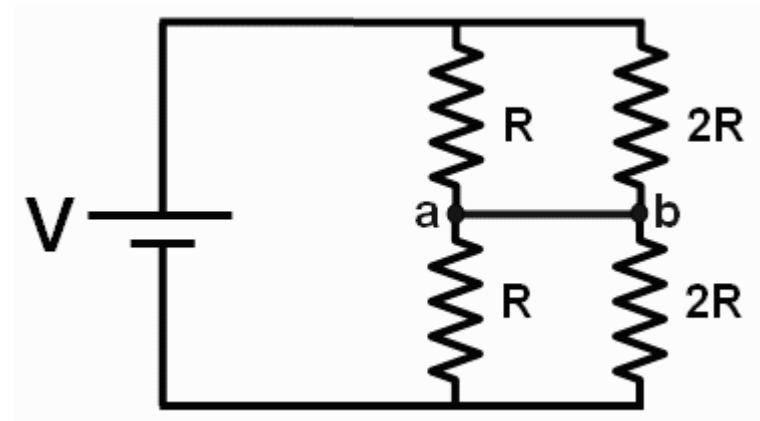




What is the same?

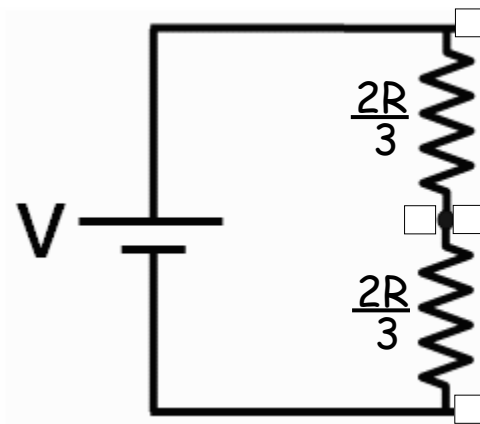Current flowing in and out of the battery



What is different?

Current flowing from a to b

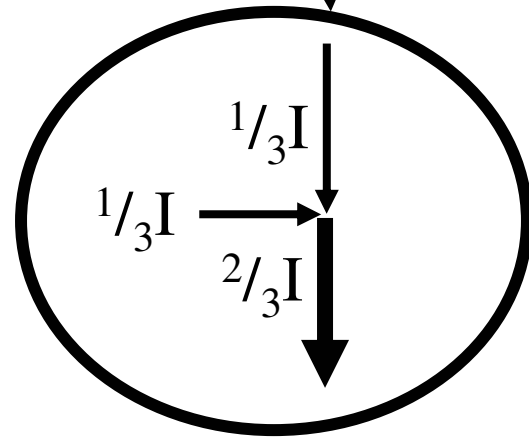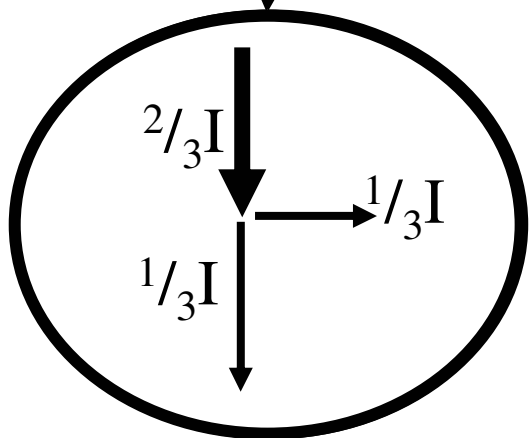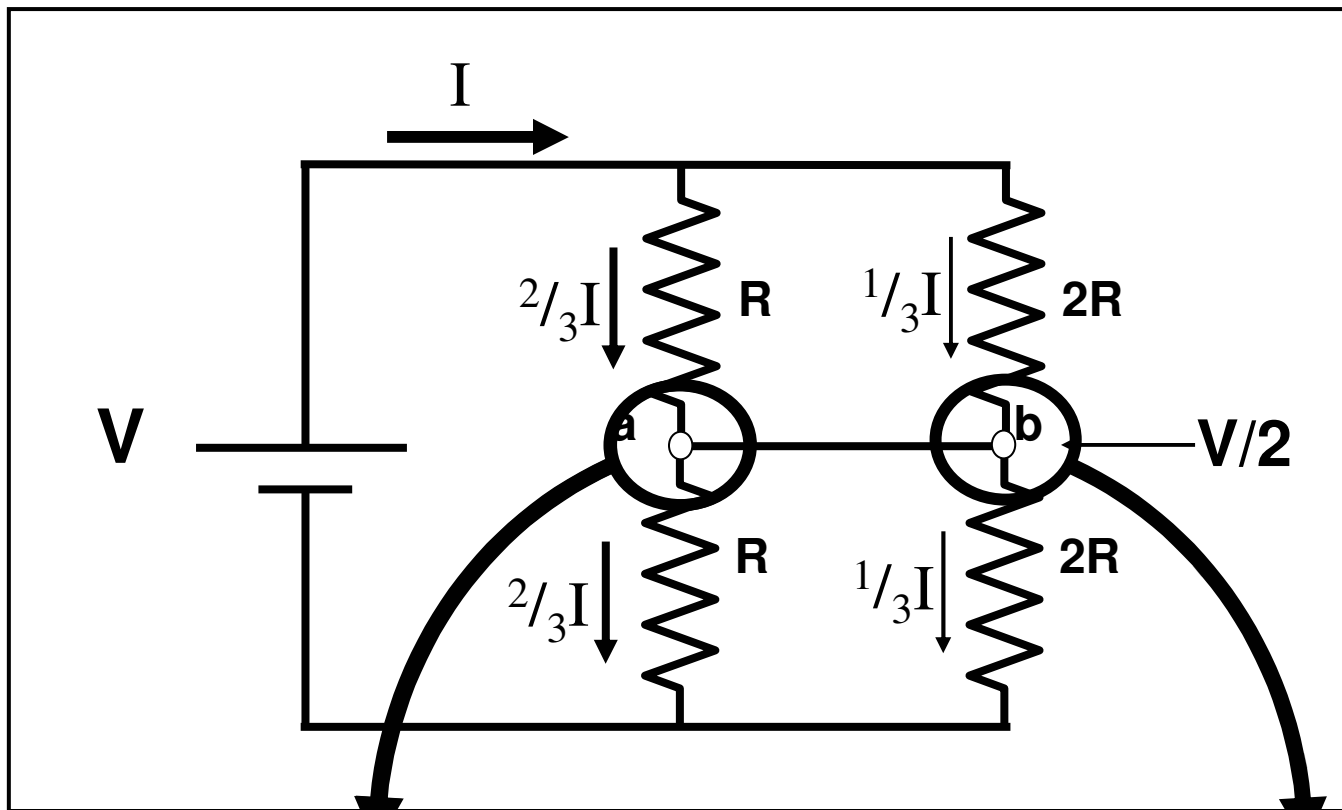


7) Consider the circuit shown below.


Clicker Problem



BB

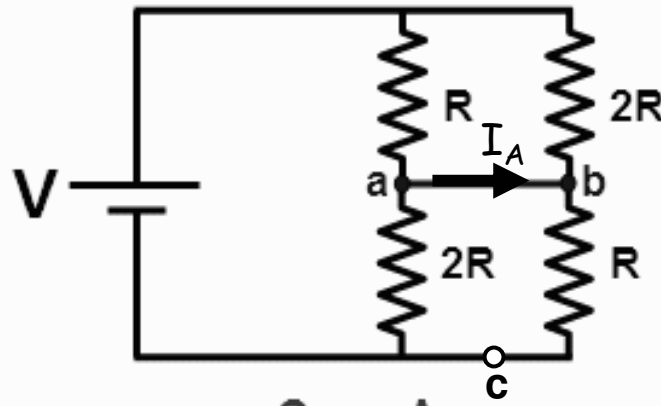

Case A

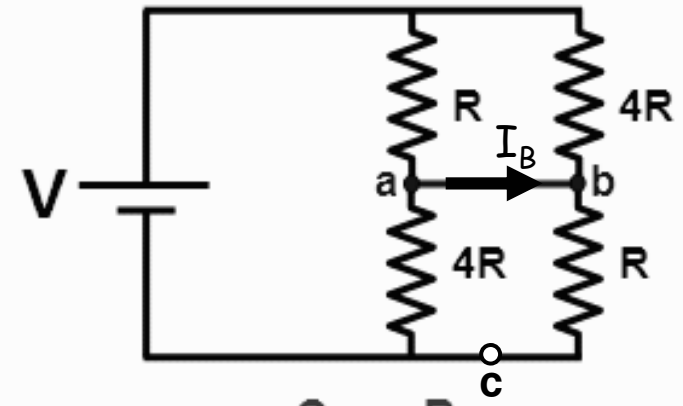

Case B

In which case is the current flowing in the blue wire connecting points a and b biggest

- Case A Case B They are the same

Current will flow from left to right in both cases

In both cases, $V_{ac} = V/2$







$$I(2R) = 2I(4R)$$

$$\begin{aligned} I_A &= I(R) - I(2R) \\ &= I(R) - 2I(4R) \end{aligned}$$

$$I_B = I(R) - I(4R)$$

RC Circuits

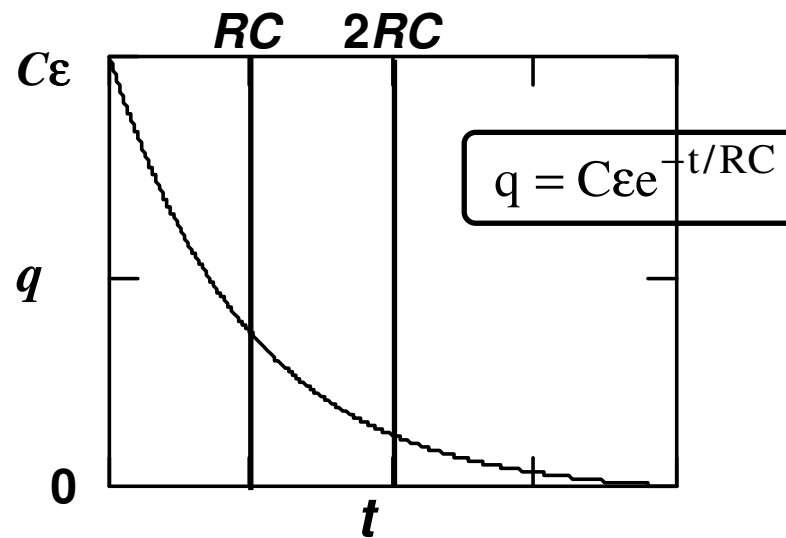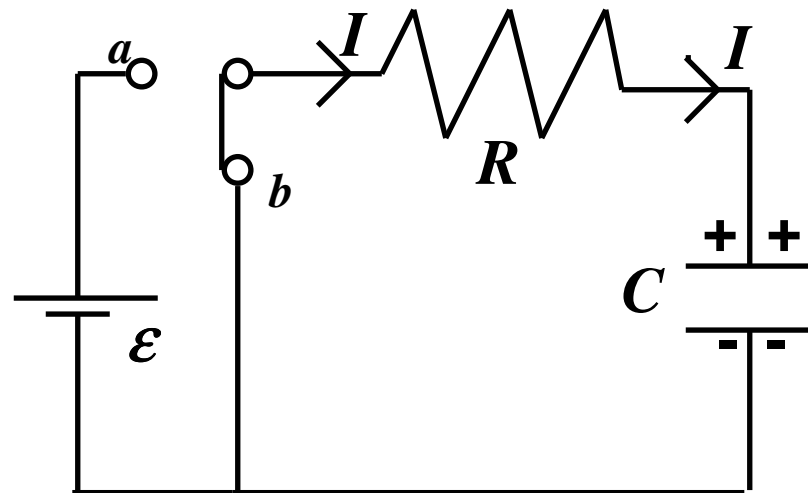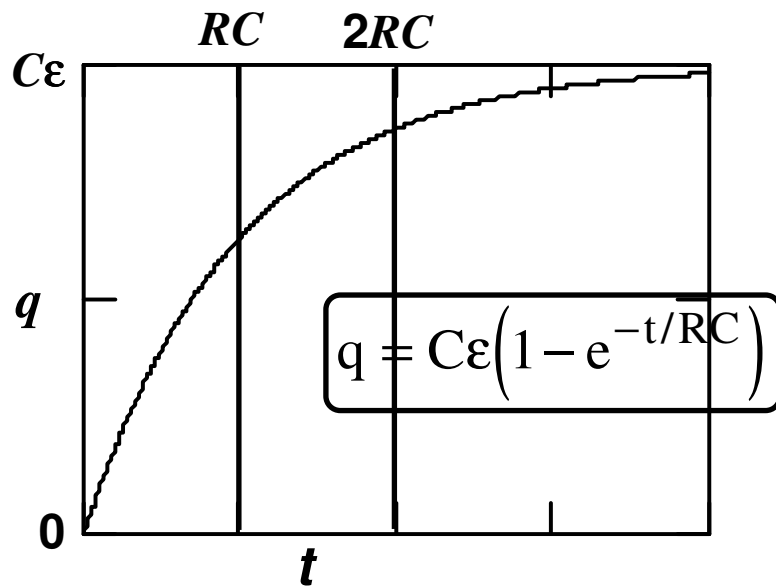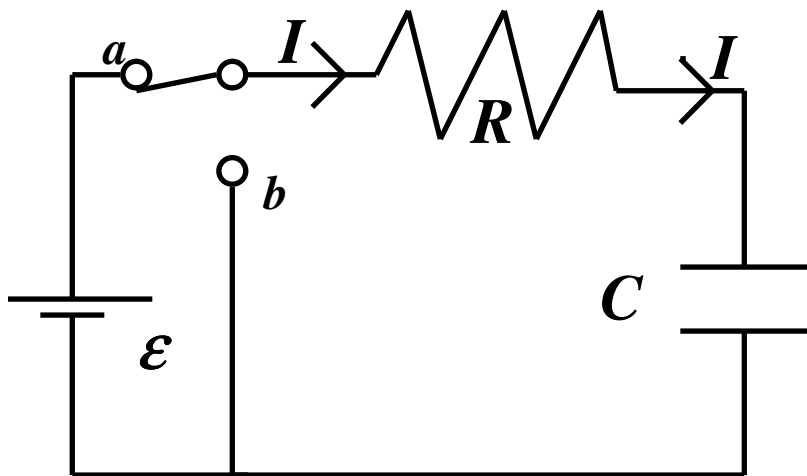


Resistor-capacitor circuits

Let's add a Capacitor to our simple circuit

Recall voltage "drop" on C ?

$$V = \frac{Q}{C}$$

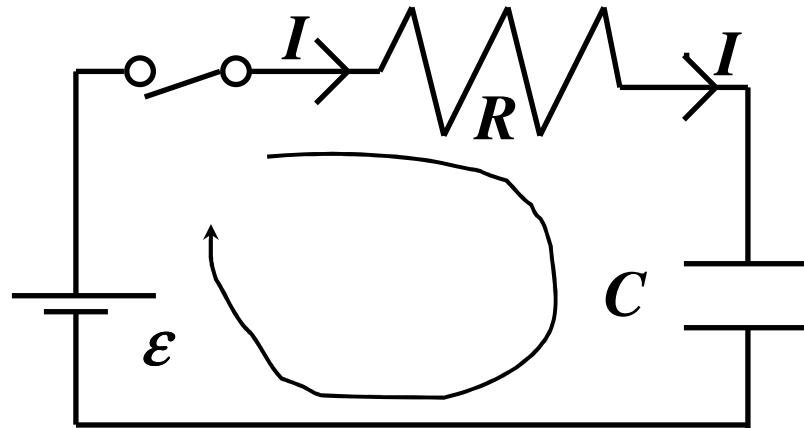

Write KVL: $\varepsilon - IR - \frac{Q}{C} = 0$

Use $I = \frac{dQ}{dt}$ Now eqn. has only "Q":

KVL gives Differential Equation ! $\varepsilon - R \frac{dQ}{dt} - \frac{Q}{C} = 0$

We will solve this later. For now, look at qualitative behavior...

Capacitors Circuits, Qualitative


Basic principle: Capacitor resists change in $Q \rightarrow$
resists changes in V

- **Charging (it takes time to put the final charge on)**
 - Initially, the capacitor behaves like a wire ($\Delta V = 0$, since $Q = 0$).
 - As current continues to flow, charge builds up on the capacitor
 - \rightarrow it then becomes more difficult to add more charge
 - \rightarrow the current slows down
 - After a long time, the capacitor behaves like an open switch.
- **Discharging**
 - Initially, the capacitor behaves like a battery.
 - After a long time, the capacitor behaves like a wire.

Clicker Problem (two parts)

2A

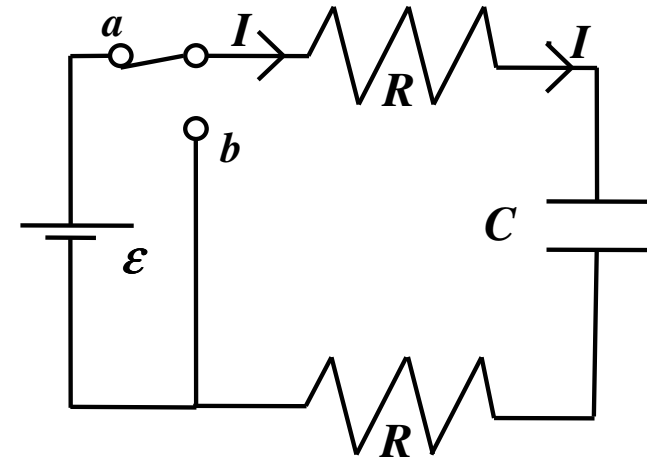- At $t=0$ the switch is thrown from position b to position a in the circuit shown: The capacitor is initially uncharged.
 - What is the value of the current I_{0+} just after the switch is thrown?



- (a) $I_{0+} = 0$ (b) $I_{0+} = \varepsilon/2R$ (c) $I_{0+} = 2\varepsilon/R$

2B

- What is the value of the current I_{∞} after a very long time?


- (a) $I_{\infty} = 0$ (b) $I_{\infty} = \varepsilon/2R$ (c) $I_{\infty} > 2\varepsilon/R$

Clicker problem (2 parts)

2A

- At $t=0$ the switch is thrown from position b to position a in the circuit shown: The capacitor is initially uncharged.

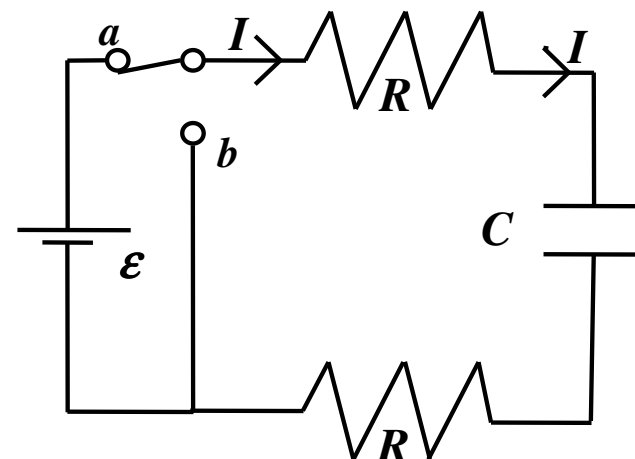– What is the value of the current I_{0+} just after the switch is thrown?



(a) $I_{0+} = 0$

(b) $I_{0+} = \varepsilon/2R$


(c) $I_{0+} = 2\varepsilon/R$

- Just after the switch is thrown, the capacitor still has no charge, therefore the voltage drop across the capacitor = 0!
- Applying KVL to the loop at $t=0+$, $\varepsilon - IR - 0 - IR = 0 \Rightarrow I = \varepsilon/2R$

Clicker problem (2 parts)

2A

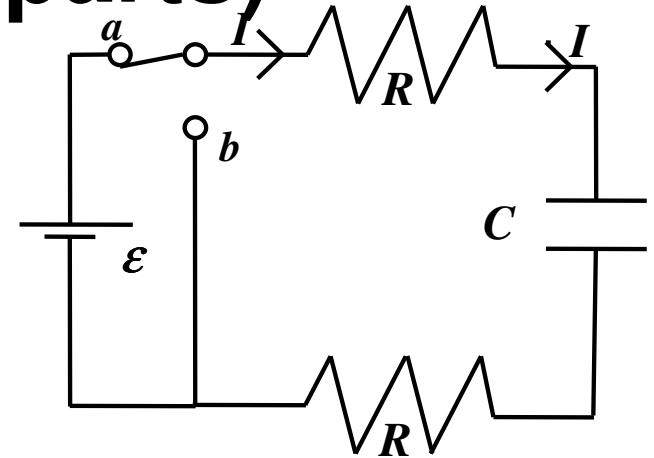- At $t=0$ the switch is thrown from position b to position a in the circuit shown: The capacitor is initially uncharged.
 - What is the value of the current I_{0+} just after the switch is thrown?



(a) $I_{0+} = 0$

(b) $I_{0+} = \varepsilon/2R$

(c) $I_{0+} = 2\varepsilon/R$

2B

- What is the value of the current I_{∞} after a very long time?

(a) $I_{\infty} = 0$


(b) $I_{\infty} = \varepsilon/2R$

(c) $I_{\infty} > 2\varepsilon/R$

- The key here is to realize that as the current continues to flow, the charge on the capacitor continues to grow.
- As the charge on the capacitor continues to grow, the voltage across the capacitor will increase.
- The voltage across the capacitor is limited to ε ; the current goes to 0.

Clicker problem

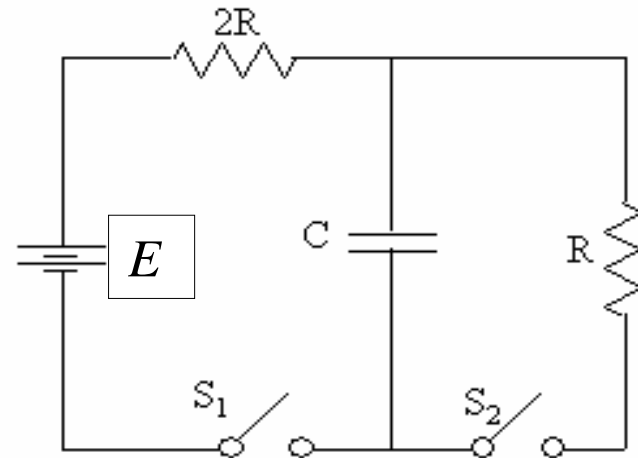The capacitor is initially uncharged, and the two switches are open.



3) What is the voltage across the capacitor immediately after switch S_1 is closed?

a) $V_c = 0$

b) $V_c = E$

Initially: $Q = 0$

$V_c = 0$ $I = E/(2R)$

c) $V_c = 1/2 E$

4) Find the voltage across the capacitor after the switch has been closed for a very long time.

a) $V_c = 0$


b) $V_c = E$

$Q = E C$

$I = 0$

c) $V_c = 1/2 E$

Clicker problem:

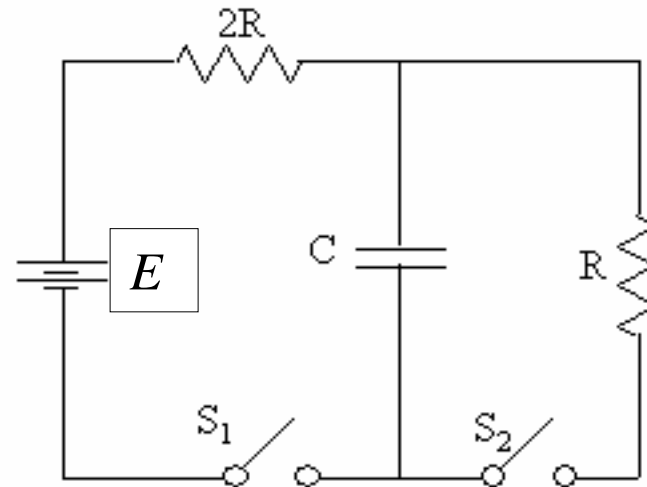

6) After being closed a long time, switch 1 is opened and switch 2 is closed. What is the current through the right resistor immediately after the switch 2 is closed?

a) $I_R = 0$

b) $I_R = E/(3R)$

c) $I_R = E/(2R)$

d) $I_R = E/R$

Now, the battery and the resistor $2R$ are disconnected from the circuit, so we have a different circuit.

Since C is fully charged, $V_C = E$. Initially, C acts like a battery, and $I = V_C/R$.


RC Circuits

(Time-varying currents, charging)

- Charge capacitor:

C initially uncharged;
connect switch to a at $t=0$

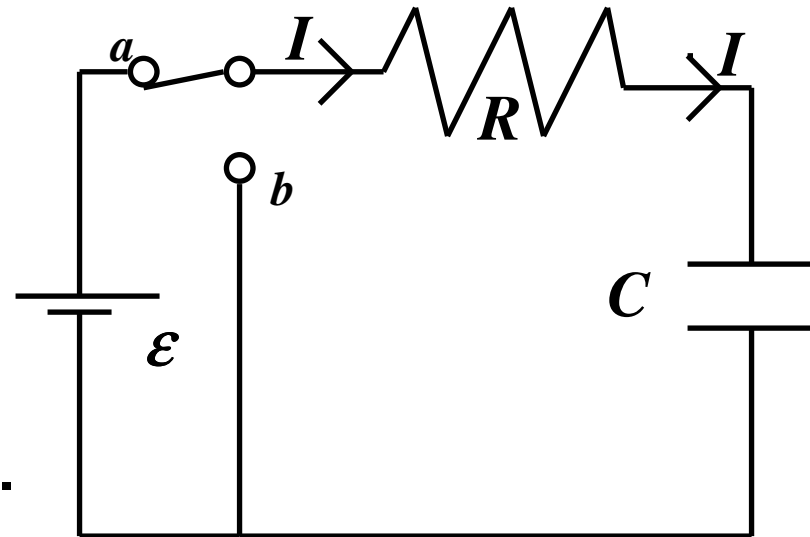Calculate current and
charge as function of time.



- Loop theorem $\Rightarrow \quad \varepsilon - IR - \frac{Q}{C} = 0$

Would it matter where R
is placed in the loop??

- Convert to differential equation for Q :


$$I = \frac{dQ}{dt} \Rightarrow \boxed{\varepsilon = R \frac{dQ}{dt} + \frac{Q}{C}}$$

NO!

Charging Capacitor

- Charge capacitor:
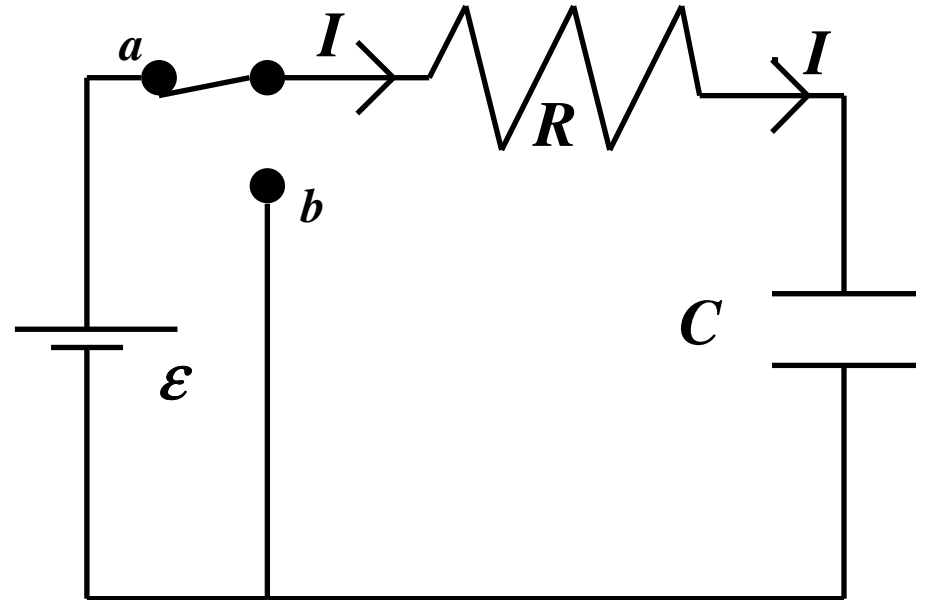
$$\varepsilon = R \frac{dQ}{dt} + \frac{Q}{C}$$



- Guess solution:

$$Q = C\varepsilon(1 - e^{-t/RC})$$

- Check that it is a solution:

$$\frac{dQ}{dt} = C\varepsilon e^{-t/RC} \left(\boxed{+} \frac{1}{RC} \right)$$

$$\Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = \boxed{+} \varepsilon e^{-t/RC} + \varepsilon(1 - e^{-t/RC}) = \varepsilon \quad !$$

Note that this “guess” fits the boundary conditions:

$$t = 0 \Rightarrow Q = 0$$

$$t = \infty \Rightarrow Q = C\varepsilon$$

Charging Capacitor in a RC circuit

- Charge capacitor:

$$Q = C\varepsilon(1 - e^{-t/RC})$$


- Current is found from differentiation:


$$I = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$



Conclusion:

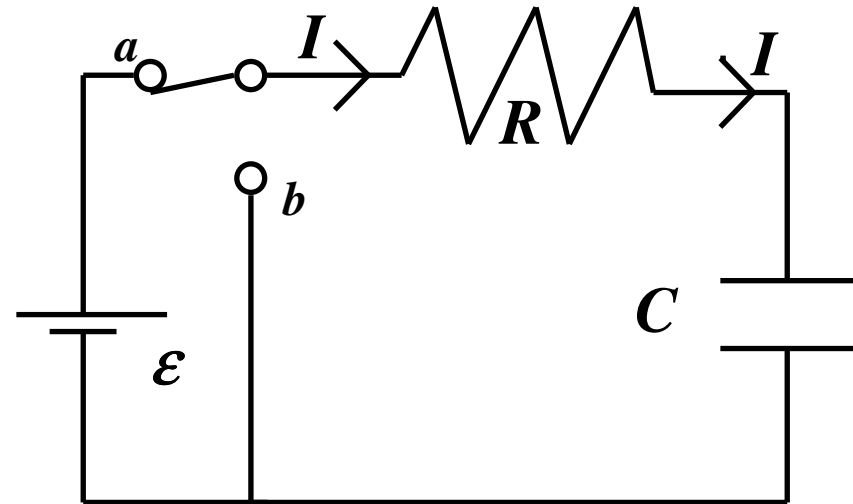- Capacitor reaches its final charge ($Q = C\varepsilon$) exponentially with time constant $\tau = RC$.
- Current decays from max ($= \varepsilon/R$) with same time constant.



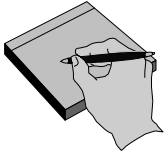

Charging Capacitor

Charge on C

$$Q = C\varepsilon(1 - e^{-t/RC})$$

$$\text{Max} = C\varepsilon$$


$$\text{63\% Max at } t = RC$$

Current

$$I = \frac{dQ}{dt} = \frac{\varepsilon}{R} e^{-t/RC}$$

$$\text{Max} = \varepsilon/R$$

$$\text{37\% Max at } t = RC$$

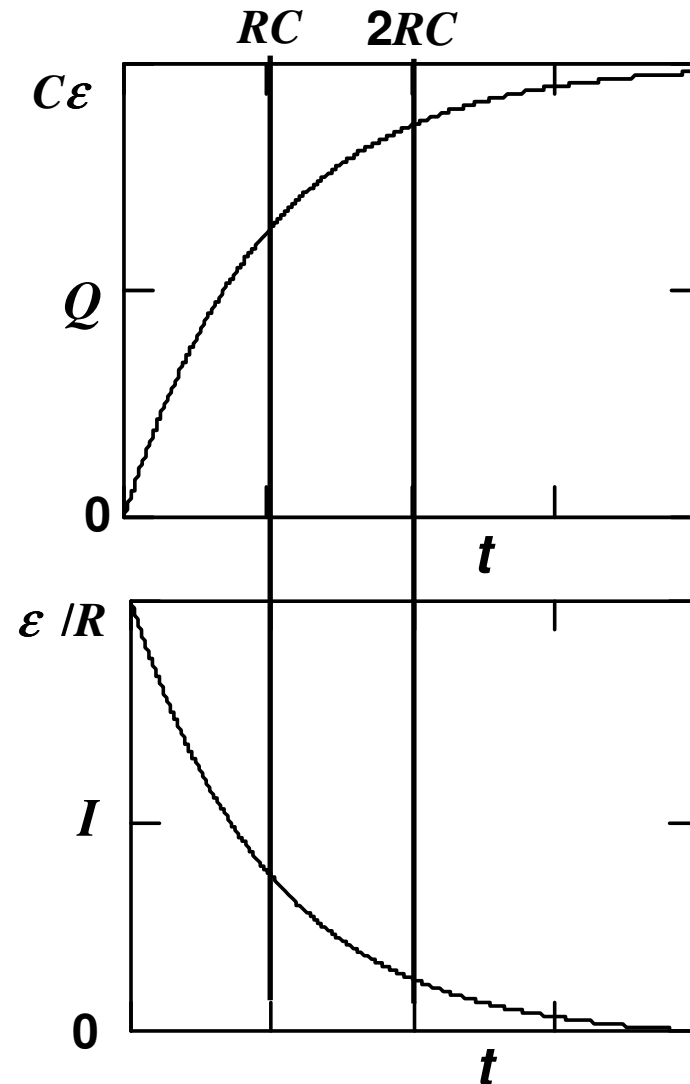

Discharging Capacitor

$$R \frac{dQ}{dt} + \frac{Q}{C} = 0$$


- Guess solution:

$$Q = Q_0 e^{-t/\tau} = C \varepsilon e^{-t/RC}$$

- Check that it is a solution:

$$\frac{dQ}{dt} = C \varepsilon e^{-t/RC} \left(-\frac{1}{RC} \right)$$
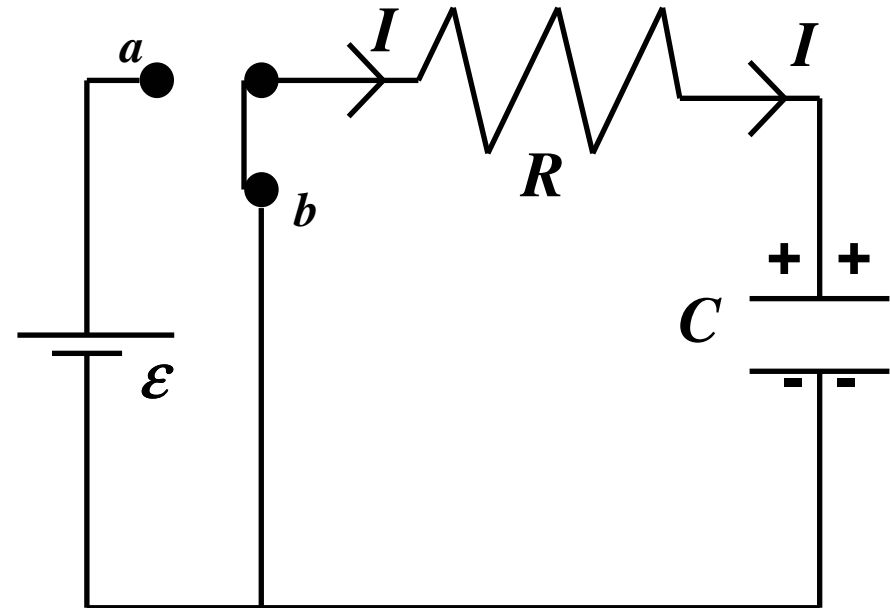
$$\Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = -\varepsilon e^{-t/RC} + \varepsilon e^{-t/RC} = 0 !$$



Note that this “guess” fits the boundary conditions:


$$t = 0 \Rightarrow Q = C \varepsilon$$

$$t = \infty \Rightarrow Q = 0$$

Discharging Capacitor

- Discharge capacitor:
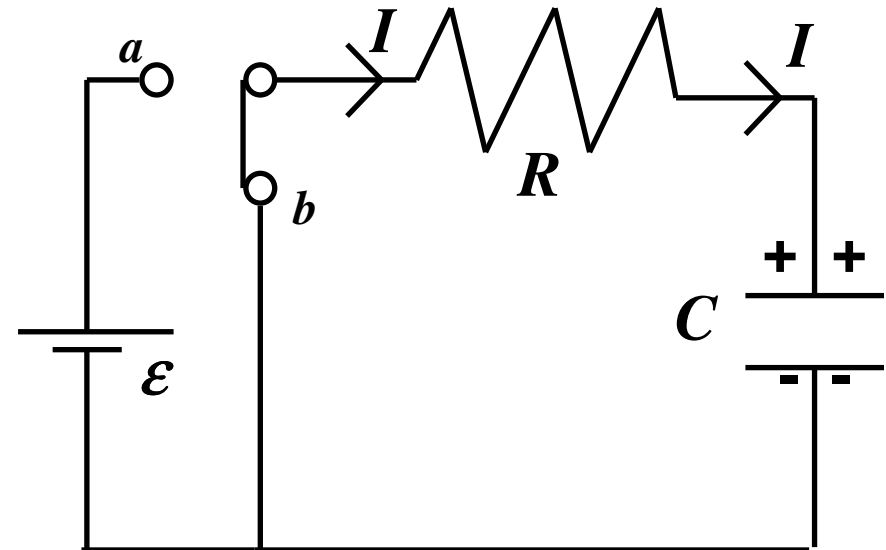
$$Q = Q_0 e^{-t/\tau} = C \epsilon e^{-t/RC}$$




- Current is found from differentiation:

$$I = \frac{dQ}{dt} = -\frac{\epsilon}{R} e^{-t/RC} \Rightarrow$$

Minus sign:
Current is opposite to original definition, i.e., charges flow away from capacitor.

Conclusion:

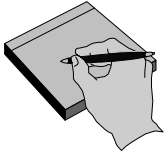- Capacitor discharges exponentially with time constant $\tau = RC$
- Current decays from initial max value ($= -\epsilon/R$) with same time constant



Discharging Capacitor

Charge on C

$$Q = C\varepsilon e^{-t/RC}$$

$$\text{Max} = C\varepsilon$$


$$\text{37\% Max at } t = RC$$

Current

$$I = \frac{dQ}{dt} = -\frac{\varepsilon}{R} e^{-t/RC}$$


$$\text{“Max”} = -\varepsilon/R$$

$$\text{37\% Max at } t = RC$$

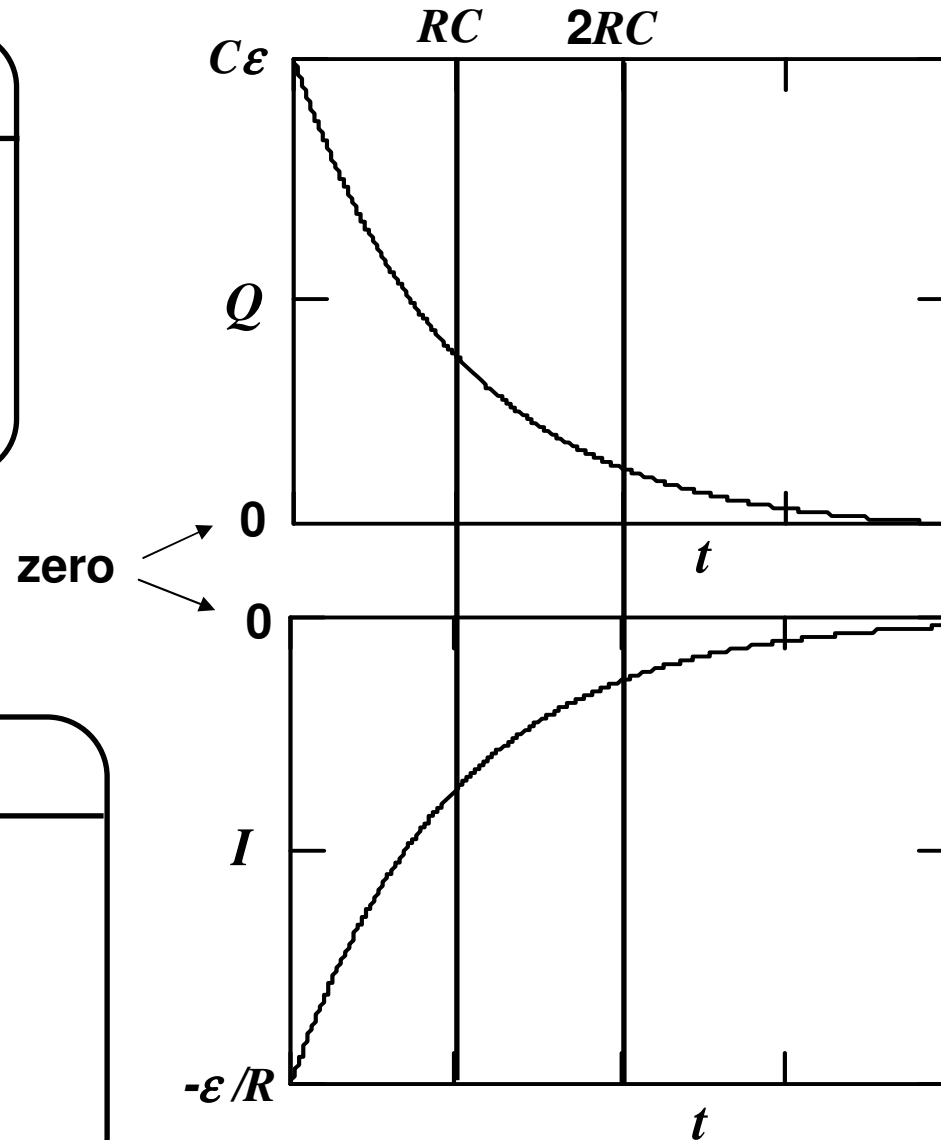

Clicker problem:

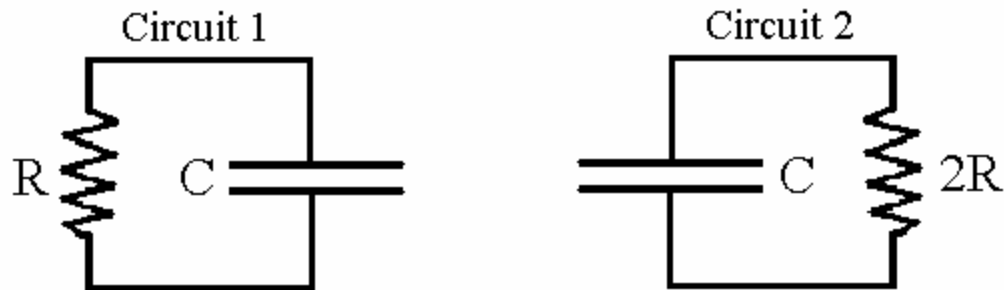The two circuits shown below contain identical fully charged capacitors at $t=0$. Circuit 2 has twice as much resistance as circuit 1.



8) Compare the charge on the two capacitors a short time after $t = 0$

a) $Q_1 > Q_2$


b) $Q_1 = Q_2$

c) $Q_1 < Q_2$

Initially, the charges on the two capacitors are the same. But the two circuits have different time constants: $\tau_1 = RC$ and $\tau_2 = 2RC$. Since $\tau_2 > \tau_1$ it takes circuit 2 longer to discharge its capacitor. Therefore, at any given time, the charge on capacitor 2 is bigger than that on capacitor 1.

Clicker:

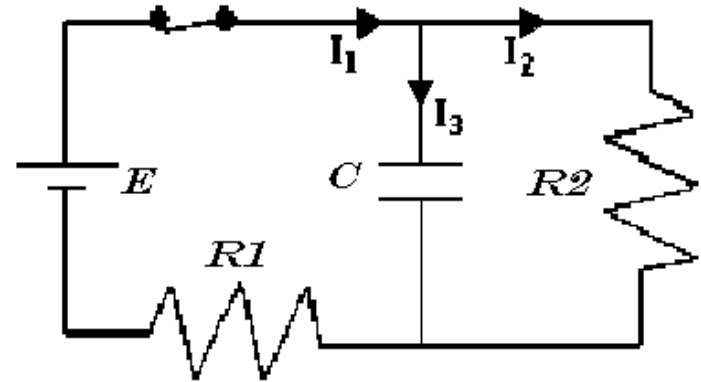The circuit below contains a battery, a switch, a capacitor and two resistors



10) Find the current through R_1 after the switch has been closed for a long time.

a) $I_1 = 0$

b) $I_1 = E/R_1$

c) $I_1 = E/(R_1 + R_2)$



After the switch is closed for a long time

The capacitor will be fully charged, and $I_3 = 0$.



(The capacitor acts like an open switch).

So, $I_1 = I_2$, and we have a one-loop circuit with two resistors in series, hence $I_1 = E/(R_1 + R_2)$

Charging

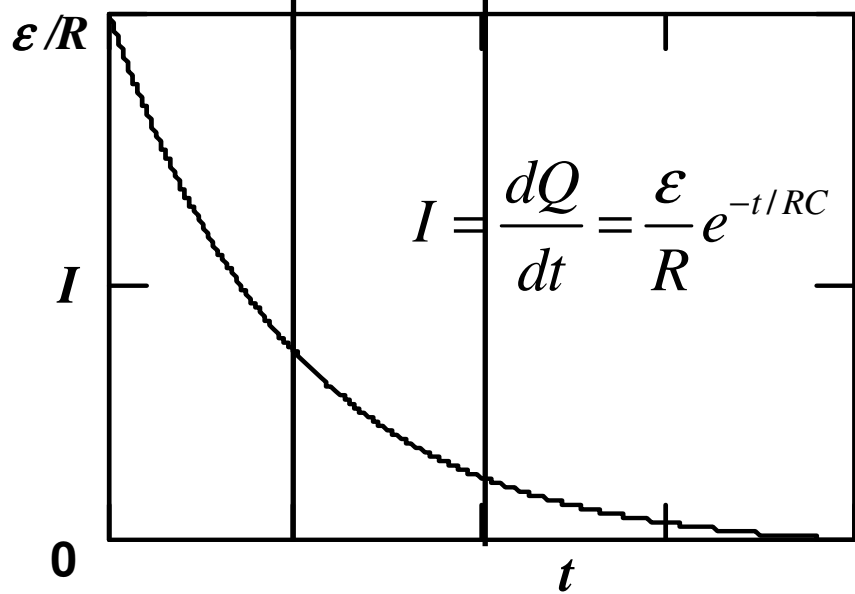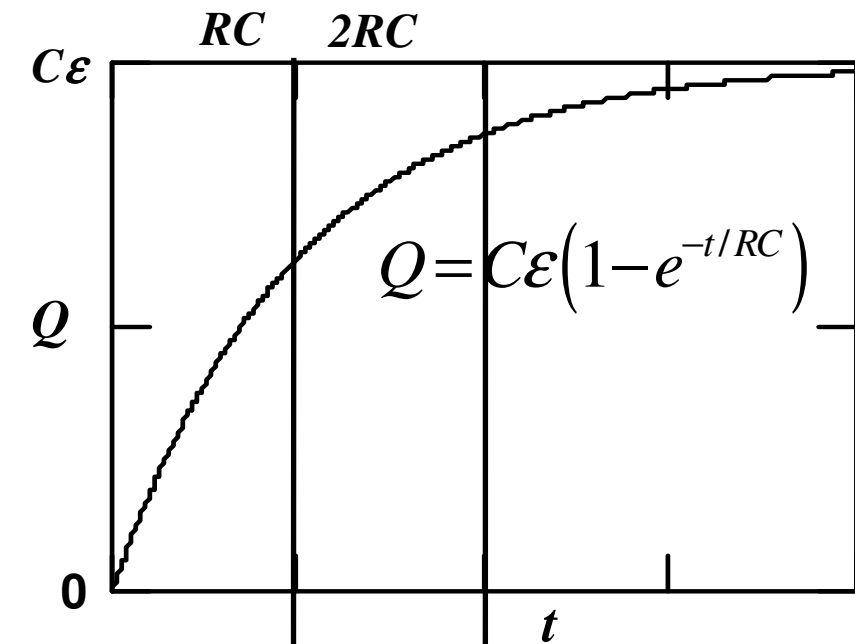

Discharging

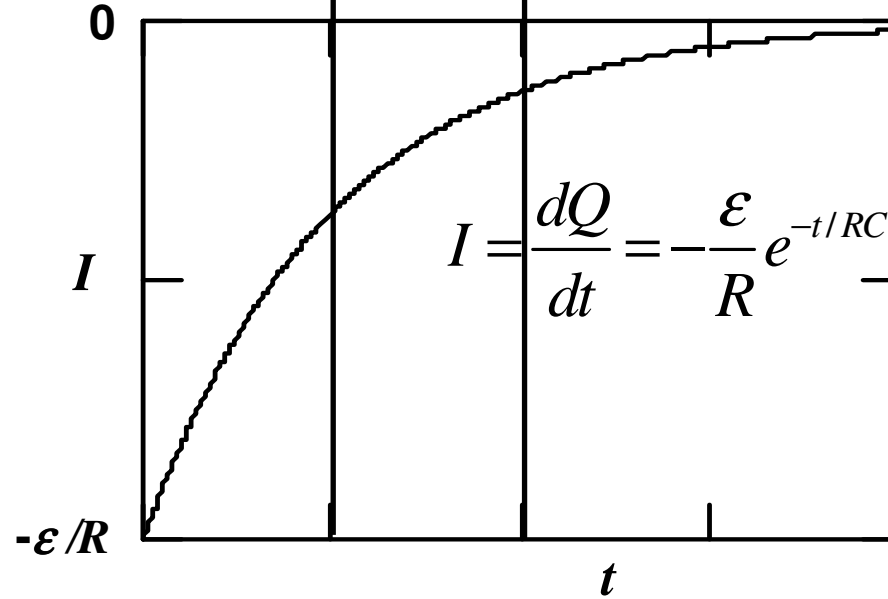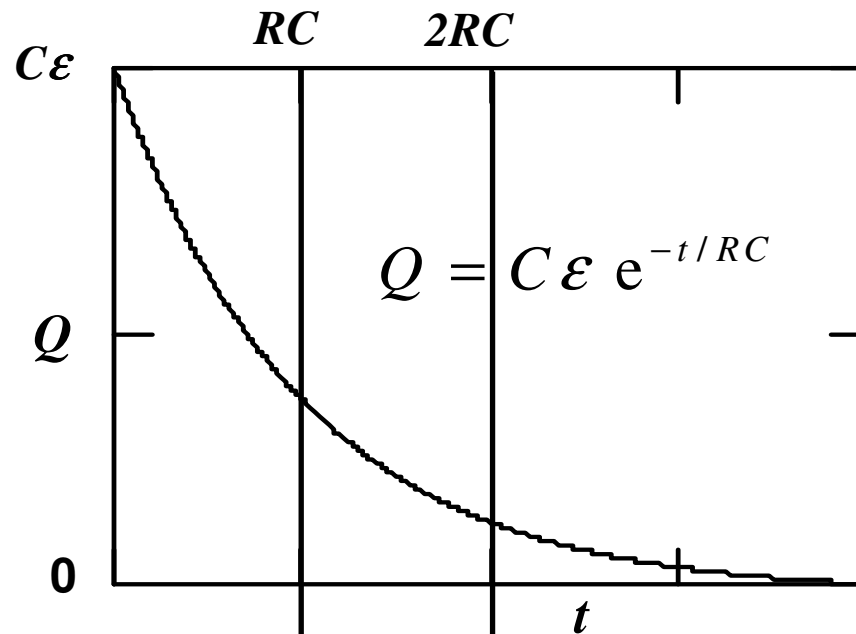


Y&F Problem 26.84 (Not a clicker problem)

A resistor with a resistance of 850Ω is connected to the plates of a charged capacitor with a capacitance of $4.62 \mu\text{F}$. Just before the connection is made, the charge on the capacitor is 8.10 mC .

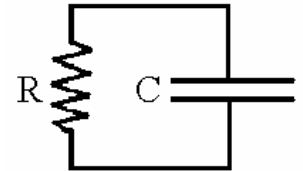A) What is the energy initially stored in the capacitor?

$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(8.1 \times 10^{-3})^2}{4.62 \times 10^{-6}} = 7.1 \text{ J}$$



B) What is the electrical power dissipated in the resistor just after the connection is made ?

$$P = \frac{V^2}{R} = \frac{(Q/C)^2}{R} = \frac{(8.10 \times 10^{-3} / 4.62 \times 10^{-6})^2}{850} = 3600 \text{ W}$$


C) At what time has the energy stored in the capacitor has decreased to half the value calculated in part (A)?

$$U_{1/2} = \frac{1}{2} \frac{Q_{1/2}^2}{C} = \frac{1}{2} U_0 = \frac{1}{2} \left(\frac{1}{2} \frac{Q_0^2}{C} \right) \quad Q_{1/2} = \frac{Q_0}{\sqrt{2}} = Q_0 e^{-t/RC}$$


$$-t/RC = \ln(1/\sqrt{2})$$

$$t = - (850)(4.62 \times 10^{-6}) \ln(1/\sqrt{2}) = 1.36 \times 10^{-3} \text{ s}$$

Power distribution systems

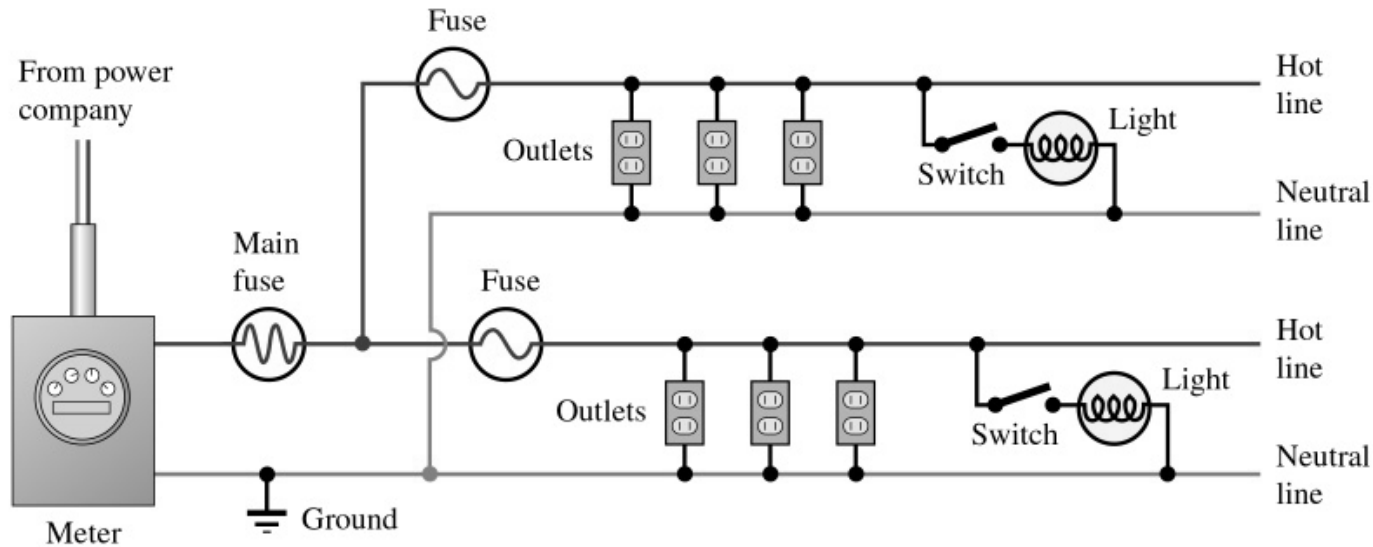

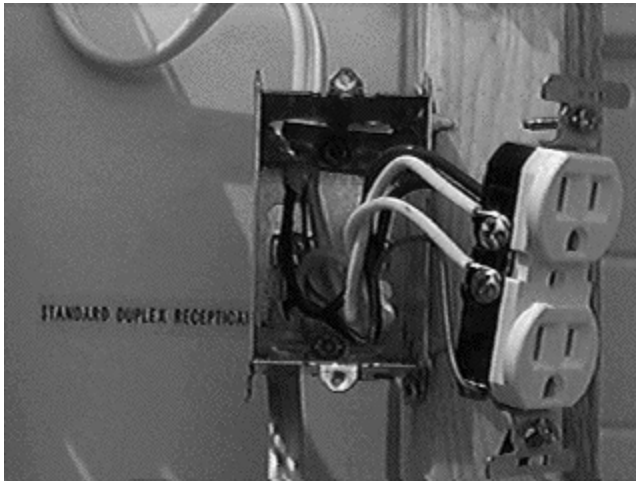Conventional House wiring has 240/120V lines



Which prong is hot??
(Hint: Black is Ground)

Remark; houses typically have two single phase, 120V hot lines

Electricity Costs (\$\$\$\$)

Your electric costs are charged in units of energy, Kilowatt-hours

1 Kilowatt-Hour = 1000 watts x 3600 sec
= 3.6 million joules

Oahu residential charges are about 20 cents per K-H. This can be read on your AC Kilowatt-Hour meter outside your house. Electricity costs in Hawaii are high!



Example

100W light bulb run for 10hrs/day for 30 days uses
 $0.1 \text{ KW} \times 10 \times 30 = 30 \text{ Kilowatt-Hours}$ and costs \$6.00.